

**2005 JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY**

**II B.TECH I SEMESTER SUPPLEMENTARY EXAMINATIONS**  
**ELECTRICAL CIRCUITS-I**  
**(ELECTRICAL & ELECTRONIC ENGINEERING)**

MAY 2005

TIME 3 HOURS  
MARKS: 80

Answer any FIVE Questions  
All Questions carry equal marks

1. (a) State and explain kircho's law.
- (b) For the circuit shown below, calculate the total current, individual currents in each branch . Also, calculate the total power consumed.
- (c) Explain the dot connection used in magnetically coupled circuits.
2. (a) Reduce the following network into a single current source and single resistor network at the terminals 1 and 2. Also, find the voltage across them.
- (b) Define the following:
  - i. R.M.S. value
  - ii. Average value and
  - iii. Form factor of a sinusoidal quantity.
- (c) Two inductors have self inductance of 0.1mH and 0.4 mH and a mutual inductance of 0.15mH. What is the value of the coefficient of coupling between them?
3. (a) In a series RLC circuit, an A.C. voltage of 120 V is applied at a frequency of 400 rad/sec. The input current leads the voltage by 63.5°. Find the value of R if L=25 mH and C=50µF. What are the drops across L and C?
- (b) In the network shown in figure, find I<sub>1</sub>, I<sub>2</sub>, and I when a 200 V A.C., 50Hz voltage is applied at the input.
4. (a) Define the time constant of R-L circuit. Give its significance.
- (b) In the circuit shown in figure, switch S is closed at t=0. Find the value of i, di/dt and d<sup>2</sup>i/dt<sup>2</sup> at t=0+.
5. In the circuit shown below in figure, determine the complete solution for the current when switch K is closed at t=0. Applied voltage is  $v(t)=50 \cos(103t+\pi/3)$ .
6. (a) For the network shown in figure, determine the expression for i(t). The switch is closed at t=0. Take V=1V; R=2; L=1H and C=0.5F.
- (b) Derive the expression for i(t) when R-L series circuit is excited by sinusoidal voltage of  $v(t) = V_m \sin(\omega t + \mu)$ .
7. (a) State and explain initial and final value theorems.
- (b) In the network shown in figure, the switch is closed at t=0 and there is no initial charge on either of the capacitors. Find the current 'i' by Laplace transform method.

8. (a) Define:

i. Quality factor

ii. Selectivity of a series resonant circuit.

(b) A  $5 \mu\text{F}$  capacitor is connected in series with a coil having inductance of  $50 \text{ mH}$ . Determine the frequency of resonance, the resistance of the coil if a  $50\text{V}$  source operating at resonant frequency causes a circuit current of  $10\text{mA}$ . What is the quality factor of the coil?

(c) Derive the resonant frequency of a R-L-C parallel circuit when it is connected across a A.C. supply.

Educationobserver.com