

Roll
No.

--	--	--	--	--	--	--	--	--	--	--

Serial No. of
Q. C. A. B.

ಒಟ್ಟು ಪ್ರಶ್ನೆಗಳ ಸಂಖ್ಯೆ : 9]
Total No. of Questions : 9]

[ಒಟ್ಟು ಮುದ್ರಿತ ಪುಟಗಳ ಸಂಖ್ಯೆ : 16
[Total No. of Printed Pages : 16

ಸಂಕೇತ ಸಂಖ್ಯೆ : **73**

ವಿಷಯ : ಎಲಿಮೆಂಟ್ಸ್ ಆಫ್ ಎಲೆಕ್ಟ್ರಾನಿಕ್ಸ್ ಇಂಜಿನಿಯರಿಂಗ್

Code No. : **73**

Subject : **ELEMENTS OF ELECTRONICS ENGINEERING**

ದಿನಾಂಕ : 03. 04. 2012]

[Date : 03. 04. 2012

ಸಮಯ : ಬೆಳಿಗ್ಗೆ 10-30 ರಿಂದ ಮಧ್ಯಾಹ್ನ-1-45 ರವರೆಗೆ]

[Time : 10-30 A.M. to 1-45 P.M.

ಪರಮಾವಧಿ ಅಂಕಗಳು : 90]

[Max. Marks : 90

FOR OFFICE USE ONLY

Q. No.	Marks	Q. No.	Marks	Q. No.	Marks	Q. No.	Marks	Q. No.	Marks
1.		×		×		×		×	
2.		×		×		×		×	
3.		×		×		×		×	
4.		×		×		×		×	
5.		×		×		×		×	
6.		×		×		×		×	
7.		×		×		×		×	
8.		×		×		×		×	
9.		×		×		×		×	
×		×		×		×		×	
×		×		×		×		×	
×		×		×		×		×	
×		×		×		×		×	
Total Marks									
Total Marks in words							Grand Total		
1. ✓							✓		
2. ✓									
Signature of Evaluators			Registration No.			Signature of the Deputy Chief		Signature of the Room Invigilator	

[Turn over

General Instructions :

- i) The Question-cum-Answer Booklet consists of objective and subjective types of questions having 9 questions.
- ii) Space has been provided against each objective type question. You have to choose the correct choice and write the complete answer in the space provided.
- iii) For subjective type questions enough space for each question has been provided. You have to answer the questions in the space.
- iv) Follow the instructions given against both the objective and subjective types of questions.
- v) Candidate should not write the answer with pencil. Answers written in pencil will not be evaluated. (Except Graphs, Diagrams & Maps)
- vi) In case of Multiple Choice, Fill in the blanks and Matching questions, scratching / rewriting / marking is not permitted, thereby rendering to disqualification for evaluation.
- vii) For reading the questions 15 minutes of extra time has been provided.

Note : Answer all the questions.

1. Fill in the blanks with the appropriate figure/word(s) by selecting from the choices given in the brackets : 10 × 1 = 10

- i) A metal is heated up to a certain temperature. It starts emission of electrons which is called

(photoelectric emission, thermionic emission, secondary emission)

Ans : _____

- ii) The elements essentially required for the manufacture of transistors are.....

(germanium & silicon, germanium & indium, germanium & sulphur)

Ans : _____

iii) The safe inverse voltage is kept lower than that of an ordinary diode which is known as

(*tunnel diode, light emitting diode, Zener diode*)

Ans : _____

iv) LSI circuit has

(*100 gates, less than 100 gates, more than 100 gates*)

Ans : _____

v) The wiring of integrated circuit becomes

(*very simple, complicated, very complicated*)

Ans : _____

vi) Alphanumeric number system is also known as

(*octal system, hexadecimal system, binary system*)

Ans : _____

vii) Op-Amp consumes

(*less power, medium power, more power*)

Ans : _____

viii) A flip-flop is a bistable electronic circuit which has

(four stable states, three stable states, two stable states)

Ans : _____

ix) The first useful microprocessor was developed by Intel and it was named as

(8085, 8080, 8058)

Ans : _____

x) A simple register used to store a binary word temporarily is called (buffer register, shift register, register)

Ans : _____

2. a) What is a semiconductor ? Give two examples.

4

b) List any four differences between intrinsic semiconductor and extrinsic semiconductor. 4

c) What is meant by doping ?

2

3. a) Draw the neat circuit diagrams of forward and reverse biased P.N. junction diodes.

4

- b) What are the materials used in construction of LED ? Name the colours of light they emit. 4

- c) Write the symbols of Zener diode and P-N diode. 2

- 4. a) What is rectifier ? 2

b) Draw a neat circuit diagram of full-wave rectifier.

4

c) Why is the filter circuit necessary in rectifiers ? Name any two types of filter circuits according to input component.

4

5. a) Define an integrated circuit.

2

b) List any four differences between integrated circuit and discrete component circuit.

4

c) How are the ICs classified ?

4

6. a) Draw a neat diagram to show the construction of monolithic IC and name the parts. 4

b) What do you mean by hybrid ? List the two types of hybrid ICs. 4

c) Define SSI and VLSI. 2

7. a) What is an operational amplifier ? 2

b) Draw a neat block diagram of Op-Amp.

4

c) List any four advantages of Op-Amp.

4

8. a) Define binary system.

2

b) Convert 1510 into binary number.

5

c) Convert 110100 into decimal number.

3

9. a) What is a flip-flop ? Draw a neat symbol of flip-flop.

4

b) Name any four types of flip-flops.

4

c) Define a counter.

2
