

2007 COCHIN UNIVERSITY OF SCIENCE & TECHNOLOGY

B.TECH ELECTRONICS & AND COMMUNICATIONS ENGINEERING INDUSTRIAL AND POWER ELECTRONICS

NOVEMBER 2007

TIME: 3 HOUR
MARK: 90

ANSWER ANY SIX QUESTION
ALL QUESTIONS CARRY EQUAL MARKS

MARK [6*15]

- 1 a. Draw and explain the V-I characteristics of an SCR. Also define Latching current and Holding current
- b. What are the various methods to turn on an SCR. Also explain the turn off characteristics of an SCR
- 2 a. Draw the V-I characteristics of a TRIAC and explain its working in each of the four modes using appropriate structures
- b. Explain various voltage ratings of Thyristors
- 3 a. Draw the circuit, waveforms and explain operation of a single phase full converter with RL with voltage source as load
- b. Explain the function of a free-wheeling diode, showing how it is connected in a circuit
- 4 a. Draw the circuit of a 3 phase full wave rectifier with R load and explain its working with suitable waveforms
- b. The speed of a separately excited d.c. motor is to be controlled in either direction. Discuss a suitable thyristor control scheme
- 5 a. Explain with circuit diagrams and waveforms auxiliary commutation scheme for SCRs
- b. Explain the working of a single phase parallel inverter. Bring out its salient features and limitations
- 6 a. With circuit diagram, describe the working of Jone's Chopper
- b. Briefly explain the concept of slip-power recovery scheme in the speed control of induction motors
- 7 a. Explain the working of a buck-boost converter
- b. A boost regulator has an input voltage of $V_{in}=15V$. The average output voltage is $V_{av}=25V$ and average load current $I_{av}=0.5A$. If $L=150 \mu H$ and $C=200 \mu F$ Determine i) duty cycle ii) ripple current in inductor iii) ripple voltage in capacitor. Assume switching frequency as 25 KHz.
- 8 a. Explain online and offline UPS with the help of block diagrams
- b. Explain dv/dt and di/dt protection in thyristors
- 9 a. Give the principle and characteristics of induction heating
- b. Explain with diagrams the various types of resistance welding
- 10 a. Explain the principle and theory of dielectric heating
- b. In non-destructive testing, discuss the use of ultrasonics