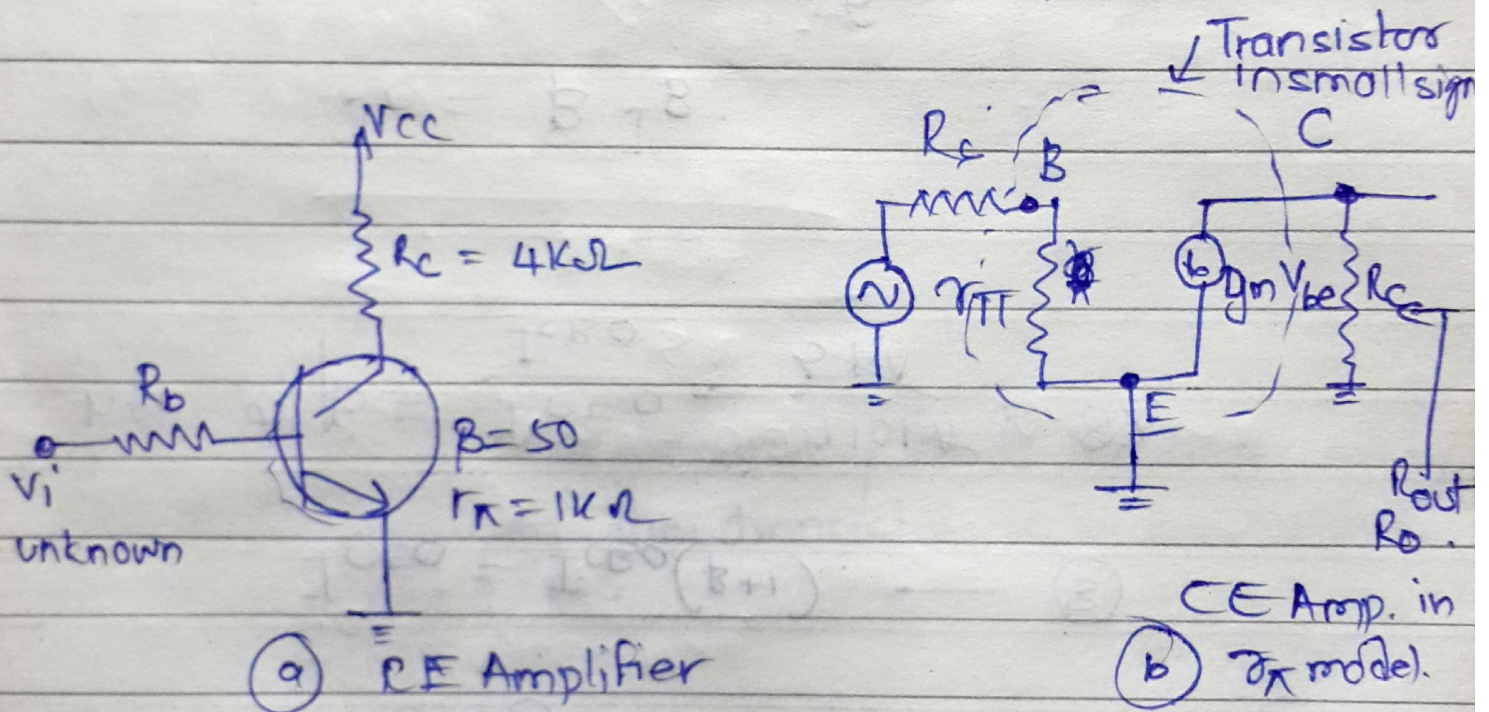


Electronics & Telecommunication

Q21. A CE Amplifier has resistor R_F connected b/t collector & base $R_F = 40K$, $R_C = 4k\Omega$, given $h_{fe} = 50$, $r_{\pi} = 1k\Omega$, output resistance is!

Solution

$R_F = 40K$, $R_C = 4k\Omega$, h_{fe} or $\beta = 50$, $r_{\pi} = 1k\Omega$



Now here

- R_{in} (Does not include source)

$R_{in} = r_{\pi} = 1k\Omega$

- R_{out} or R_o (Does not include load)

so

$R_C = R_o = 4k\Omega$

So Ans! (a) $4k\Omega$

Q22 If $I_{CEO} = 410 \mu A$, $I_{CBO} = 5 \mu A$ & $I_B = 30 \mu A$, then collector current (I_c).

Solⁿ Collector current & current (base) & reverse saturation current.

$$I_c = \beta I_B + I_{CBO}(\beta + 1) \quad \text{--- (1)}$$

$$\therefore I_c = \beta I_B + I_{CEO} \quad \text{--- (2)}$$

from (1) & (2)

$$I_{CEO} = I_{CBO}(\beta + 1). \quad \text{--- (3)}$$

$$h_{fe} \text{ or } \beta = \frac{I_{CEO}}{I_{CBO}} = \frac{410 \mu A}{5 \mu A} = 82$$

$$I_c = \beta I_B$$

$$= 82 \times 30 \times 10^{-6} \text{ A}$$


$$= ~~2460 \mu A~~ \quad 2.46 \text{ mA}$$

$$I_c = 2460 \mu A \text{ or } ~~2.46 \text{ mA}~~$$

There is No such option

24. The transistor as shown in the circuit is operating in

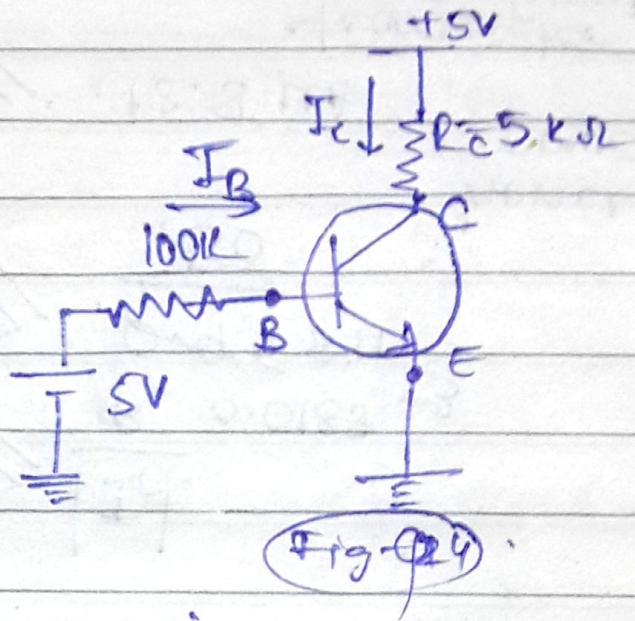- (a) cutoff
- (b) saturation
- (c) Active Region
- (d) Saturation or Active region.



Solution

Test of saturation region:

Test - 1

Determine I_C & I_E separately from the circuit config. under consideration. The transistor is in saturation.

$$iR(I_B) \gg |I_C|/\beta$$

Let us check. Test 1

Given


lets assume

$$V_{BE} = 5V, V_{BE(sat)} = 0.7V, V_{CE(sat)} = 0.3V,$$

$$R_B = 100K, V_{CC} = 5V, \beta = 50 \text{ (Assume)}$$

Base loop (Calculation of I_B)

$$I_C = \frac{V_{BB} - V_{BE}}{R_B}$$

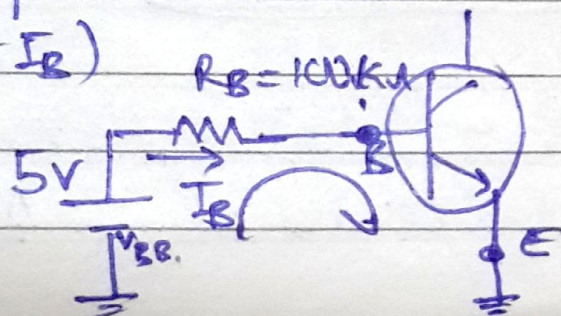

$$I_B = \frac{5V - 0.7V}{100K}$$

$$I_B = \frac{4.3 \text{ A}}{100K} \text{ or } \boxed{I_B = 43 \mu A}$$

~~I_B~~

Calculation of Collector current (I_c).

$$I_c = \frac{V_{cc} - V_{ce}}{R_c}$$

$$I_c = \frac{5V - 0.3V}{5K} = 0.94 \text{ mA}$$

$$\boxed{I_c = 0.94 \text{ mA}}$$

Now check

$$|I_B| \geq \frac{|I_c|}{\beta} \quad 0.0188 \rightarrow 3$$

$$43 \mu A \geq \frac{0.94 \times 10^{-3}}{50}$$

$$\boxed{43 \mu A \geq 18.8 \mu A}$$

hence proved

transistor is in Saturation.

Ans: Saturation Region

Q29 The amplifier A shown in the figure has open loop gain of 100, input impedance Z_i of $1\text{ k}\Omega$ & output impedance Z_o of 100Ω . If negative feedback factors $\beta = 0.99$ is used, the new values of Z_i and Z_{out} are respectively,


Solⁿ

Given


$Z_i = 1\text{ k}\Omega$

$Z_{out} = 100\Omega$

$A = 100, \beta = 0.99$

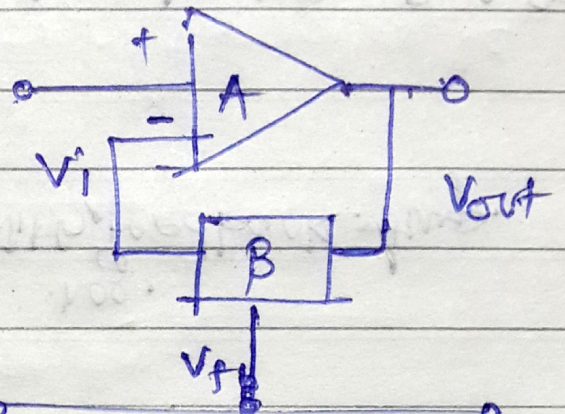

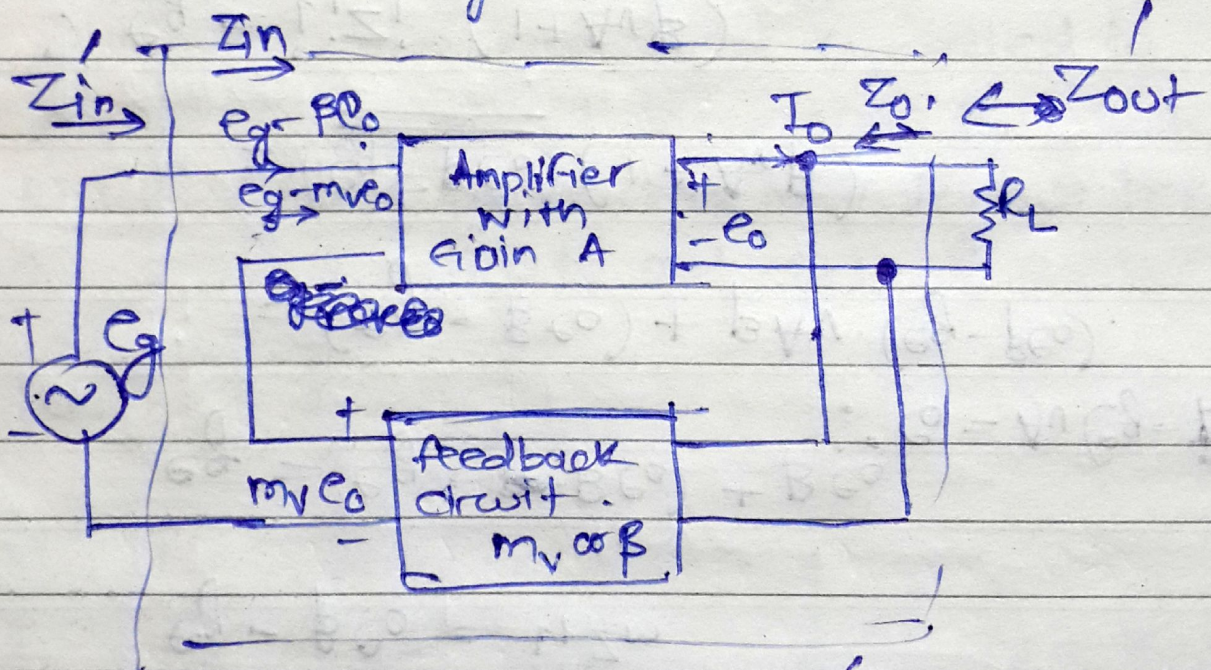Let Z_{in}' & Z_{out}' will be the new impedance of the closed loop negative feedback amplifier,



m_v or β = feedback amplifier. Z_i = New i/p impedance
 E_g = energy generator voltage. Z_o' = New o/p impedance
 e_o = output voltage. i_i = current

From fig

$$e_g - \beta e_o = i_i z_m$$

$$e_g = (e_g - \beta e_o) + \beta e_o$$

$\therefore e_o = A_v (e_g - \beta e_o)$

$$= (e_g - \beta e_o) + \beta A_v (e_g - \beta e_o)$$

$$= \underline{(e_g - \beta e_o)} (1 + A_v \beta)$$

$$\therefore e_g = i_i z_i (1 + A_v \beta)$$

or

$$\left(\frac{e_g}{i_i} \right) = z_i (1 + A_v \beta)$$

New Impedance with ^{neg.} feedback. Amp.

$$z_i' = z_i (1 + A_v \beta)$$

Now given $z_i = 1 \text{ k}\Omega$, $A_v \text{ or } A = 100$, $\beta = 0.99$

$$z_i' = 1 \text{ k}\Omega (1 + 100 \times 0.99)$$


$$z_i' \approx 100 \text{ k}\Omega$$

similary

$$Z_{out}' = \frac{Z_{out}}{(1 + A\beta)}$$

$$Z_{out} = 100 \Omega, \quad A = 100, \quad \beta = 0.99$$
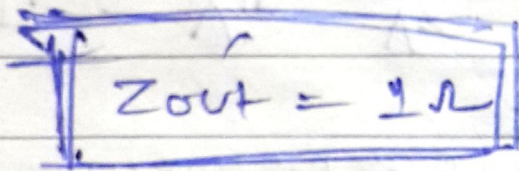
$$Z_{out}' = \frac{100}{(1 + 100 \times 0.99)} = \frac{100}{100} = 1 \Omega$$



Ans (c) $Z_{in}' = 100k\Omega$ & $Z_{out}' = 1\Omega$

Q32 A 5mV, 1kHz sine wave signal is applied to the signal to an OPAMP. Integrator for which $R = 100 \Omega$ (But question it is $100k\Omega$ but I think it was wrong according to options), & $C = 1nF$. The o/p voltage.

