

1. The total resistance of a two similar wire conductors connected in parallel is _____.
- A. resistance of one wire multiplied by 4
 - B. same resistance of one wire
 - C. one half the resistance of one wire
 - D. double the resistance of one wire

ANSWER: C

2. What is the value of a resistor with colors from left: Orange, Blue, Gold, and Silver?
- A. 34 ohms \pm 10%
 - B. 3.6 ohms \pm 10%
 - C. 3.4 ohms \pm 10%
 - D. 36 ohms \pm 10%

ANSWER: B

3. Determine the value of a resistor with colors from left to right; Brown, Green, Gold, and Silver.
- A. 1.5 ohms \pm 10%
 - B. 15 ohms \pm 10%
 - C. 1.5 ohms \pm 20%
 - D. 15 ohms \pm 20%

ANSWER: A

4. Resistors with high value usually have lower wattage ratings because of _____.
- A. varying current
 - B. lower current
 - C. bigger size
 - D. high current

ANSWER: B

5. Smaller resistors usually have _____ resistance value.
- A. small
 - B. high
 - C. low
 - D. very small

ANSWER: B

6. When resistors are connected in series, what happens?
- A. The effective resistance is decreased
 - B. Nothing
 - C. The tolerance is decreased
 - D. The effective resistance is increased

ANSWER: D

7. A 33 kilo ohms resistor is connected in series with a parallel combination made up of a 56 kilo ohm resistor and a 7.8 kilo ohm resistor. What is the total combined resistance of these three resistors?
- A. 63769 ohms
 - B. 49069 ohms
 - C. 95800 ohms
 - D. 39067 ohms

ANSWER: D

8. If you need a 1.25 k Ω resistance and you only have resistors of 5 k Ω , how many of these available resistors you should connect in parallel to get a 1.25 k Ω value?
- A. 2
 - B. 3
 - C. 4
 - D. 5

ANSWER: C

9. Insulating elements or materials has a capability of
- A. allowing electric current to flow
 - B. supporting charge flow
 - C. preventing short circuit between conducting wires
 - D. making electrical circuits to be completed

ANSWER: C

10. _____ is used to store electrical energy in an electrostatic field?
- A. A transformer
 - B. A battery
 - C. A capacitor
 - D. An inductor

ANSWER: C

11. What factors determine the capacitance of a capacitor?
- A. Area of the plates, amount of charge on the plates and the dielectric constant of the material between the plates
 - B. Area of the plates, voltage on the plates and the distance between the plates
 - C. Area of the plates, distance between the plates, and the dielectric constant of the material between the plates
 - D. Area of the plates, voltage on the plates and dielectric constant of the material between the plates

ANSWER: C

12. Factors that determine the capacitance of a capacitor.
- A. area of the plate; directly proportional
 - B. distance between plate; inversely proportional
 - C. dielectric constant; directly proportional
 - D. all of these

ANSWER: D

13. An electronic/electrical component/device used to store electrical energy.
- A. Capacitor
 - B. Inductor
 - C. Resistor
 - D. lightning arrester

ANSWER: A

14. Which of the following describes the action of a capacitor?
- A. Converts ac into dc
 - B. Stores electrical energy
 - C. Opposes change in current flow

D. Creates a dc resistance

ANSWER: B

15. A parallel plate capacitor has the following values: $k=81$; $d=0.025$ inches; $A=6$ square inches. What is the capacitance of the capacitor?

A. 4.372 picofarad

B. 43.72 picofarad

C. 4372 picofarad

D. 437.2 picofarad

ANSWER: C

16. Five picofarad is equivalent to _____.

A. 5×10 to the -12^{th}

B. 50×10 to the -12^{th}

C. 5×10 to the -10^{th}

D. 500×10 to the -10^{th}

ANSWER: A

17. If two micro-farad capacitors are connected in series, what will be the total effective capacitance?

A. 0.125 microfarad

B. 0.0624 microfarad

C. 2.5 microfarad

D. 0.50 microfarad

ANSWER: A

18. A $20 \mu\text{F}$ capacitor is charged by a 12-V battery. What is the stored energy at the capacitor?

A. 2.88×10^{-3} J

B. 1.07×10^{-3} J

C. 1.44×10^{-3} J

D. 2.88×10^{-2} J

ANSWER: C

19. Which of the following characterizes inductance?

A. Tends to oppose dc

B. Tends to oppose changes in voltage

C. Tends to oppose changes in current

D. Opposes all frequencies equally

ANSWER: C

20. A coil of wire wound, with or without a magnetic core designed to have a higher self-inductance than a straight wire.

A. Inductor

B. Solenoid

C. Toroid

D. Inductive relay

ANSWER: A

21. With the same voltage applied, which of the following allows more current?

A. 25 ohms

- B. 250 ohms
 - C. 0.25 ohms
 - D. 2.5 ohms
- ANSWER: C

22. In electrical circuits, current is known as the flow of charged carriers, such as electrons. When can this happen?

- A. when an electrical force (called emf) is applied
 - B. when material used allows electrons to flow
 - C. when there is circuit continuity
 - D. all of the above
- ANSWER: D

23. What utilizes electrical energy in electrical circuits?

- A. supply emf
 - B. load
 - C. the conducting wires
 - D. all of the above
- ANSWER: B

24. An electronic device draws 300 watts from its 24-volt power source. Find effective resistance.

- A. 1.92 ohms
 - B. 19.20 ohms
 - C. 1.25 ohms
 - D. 12.50 ohms
- ANSWER: A

25. A 50Ω resistor is connected in series with a 150Ω resistor and to a supply voltage of 20V. What is the current through the 50Ω resistor?

- A. 0.01 A
 - B. 0.1 A
 - C. 1.0 A
 - D. 10 A
- ANSWER: B

26. Two resistors, 10Ω and 100Ω are connected in parallel, approximately, what is the total resistance?

- A. 10Ω
 - B. 50Ω
 - C. 90Ω
 - D. 100Ω
- ANSWER: A

27. A shunt resistor is used to limit the load current to 0.5 A, if the load resistance is 100Ω and the original current is 1 amp, what should be the value of the shunt resistance?

- A. 25Ω
 - B. 50Ω
 - C. 75Ω
 - D. 100Ω
- ANSWER: D

28. How many $1\text{k}\Omega$ resistors to be connected in parallel are needed in order to get 100Ω ?
- A. 2
 - B. 5
 - C. 10
 - D. 20

ANSWER: C

29. Two resistors, $R_1=100\Omega$ and $R_2=200\Omega$ are connected in series, if the voltage across R_2 is 20V , what is the voltage across R_1 ?
- A. 5V
 - B. 10V
 - C. 15V
 - D. 20V

ANSWER: B

30. Two resistors, $R_1=100\Omega$ and $R_2=200\Omega$ are connected in parallel. If the current through R_1 is 1A , what would be the current on R_2 ?
- A. 0.125A
 - B. 0.25A
 - C. 0.35A
 - D. 0.50A

ANSWER: D

31. A 6A current source drives a load consisting a parallel combination of $R_1 = 50\Omega$ and $R_2 = 25\Omega$. Determine the current I_1 through R_1 .
- A. 1 amp
 - B. 2 amps
 - C. 3 amps
 - D. 4 amps

ANSWER: B

32. A constant voltage source $V_s = 60$ is delivering a power to a series combination of $R_1 = 100\Omega$, $R_2 = 200\Omega$ and $R_3 = 300\Omega$. Calculate the voltage drop across R_2 .
- A. 10V
 - B. 20V
 - C. 30V
 - D. 40V

ANSWER: B

33. If 12V are applied to a circuit that consumes 78W , what is the current flow through the circuit?
- A. 6.5A
 - B. 936A
 - C. 0.15A
 - D. 9.36A

ANSWER: A

34. Find the current that flows through the filament of a 400watts flat iron connected to a 220 Volt power line.
- A. 50 mA

- B. 5 A
 - C. 5 mA
 - D. 500 mA
- ANSWER: D

35. An electrical device has a resistance of 10Ω and is supplied with a 5 ampere constant current source. If the device is rated $100 V_{dc}$, determine its power consumed.

- A. 250 W
 - B. 450 W
 - C. 750 W
 - D. 1000 W
- ANSWER: A

36. The power dissipated by a 10Ω load resistor with a current rating of 5 amperes is _____ if supplied with a 20 volt dc potential.

- A. 40 W
 - B. 80 W
 - C. 160W
 - D. 250 W
- ANSWER: A

37. The power in a circuit consisting of two equal resistors in series is known to be 10 watts. If the two resistors are connected in parallel, what would be the circuit power dissipation?

- A. 2.5 watts
 - B. 5 watts
 - C. 20 watts
 - D. 40 watts
- ANSWER: D

38. How many nodes are needed to completely analyze a circuit according to kirchhoff's current law?

- A. two
 - B. all nodes in the circuit
 - C. one less than the total number of nodes in the circuit
 - D. one
- ANSWER: C

39. Loop currents should be assumed to flow in which direction?

- A. Straight
 - B. Either C or D arbitrarily selected
 - C. Counter-clockwise
 - D. Clockwise
- ANSWER: B

40. What theorem we should use in solving electrical circuits with several voltage sources?

- A. superposition
 - B. Norton
 - C. Thevenin
 - D. Kirchhoff
- ANSWER: A

41. In a mesh, the algebraic sum of all voltages and voltage drops is equal to zero.
- A. superposition theorem
 - B. Norton's law
 - C. Kirchhoff's first law
 - D. Kirchhoff's second law

ANSWER: D

42. The sum of all currents entering a junction is equal to the sum of currents leaving away from that junction.
- A. Kirchhoff's first law
 - B. Kirchhoff's second law
 - C. Norton's theorem
 - D. Thevenin's theorem

ANSWER: A

43. Theorem used to simplify complex circuits wherein, the simplified circuit contains an equivalent open circuit resistance and open circuit voltage.
- A. Norton's
 - B. Thevenin's
 - C. Maxwell's
 - D. Kirchhoff's

ANSWER: B

44. Considered as the reverse of Thevenin's theorem.
- A. Maxwell
 - B. Superposition
 - C. Kirchhoff
 - D. Norton's

ANSWER: D

45. A certain Thevenin equivalent circuit has parameters $R_{TH} = 10 \Omega$ and $V_{TH} = 20 \text{ V}$. If this is converted to Norton's equivalent circuit, R_N and I_N would be
- A. 10Ω and 2A
 - B. 10Ω and 4A
 - C. 0.10 and 2A
 - D. 0.10 and 4A

ANSWER: A

46. R_N and I_N of a Norton's equivalent circuit are known to be 100Ω and 10A , respectively. If a 400Ω load is connected, it will have a load current of
- A. 1 A
 - B. 2 A
 - C. 3 A
 - D. 4 A

ANSWER: B

47. A chosen closed path of current flow in a network. In making this current path there should be no node nor elements that are passed more than once.
- A. node
 - B. junction

- C. mesh
 - D. loop
- ANSWER: C

48. A set of circuit elements that forms a closed path in a network over which signal can circulate.

- A. node
 - B. junction
 - C. mesh
 - D. loop
- ANSWER: D

49. In a network, what do we call a reference point chosen such that more branches in a circuit met.

- A. node
 - B. junction
 - C. ground
 - D. mesh
- ANSWER: A

50. A common connection between circuit elements or conductors from different branches.

- A. node
 - B. junction
 - C. ground
 - D. mesh
- ANSWER: B

51. The return point in a circuit, where all voltage measurements are referred.

- A. node
 - B. junction
 - C. ground
 - D. loop
- ANSWER: C

52. Mesh analysis is best used together with what circuit law?

- A. KVL
 - B. KCL
 - C. VDT
 - D. CDT
- ANSWER: A

53. Nodal analysis is best used together with

- A. KVL
 - B. KCL
 - C. VDT
 - D. CDT
- ANSWER: B

54. Three 100Ω resistors are connected in a tee-form (T) network and is set up between a 100 V supply and a load resistor R_L . If maximum power transfer is desired, what should be the resistance of the load resistor R_L ?

- A. 50 Ω
- B. 75 Ω
- C. 125 Ω
- D. 150 Ω

ANSWER: D

55. Theorem used in simplifying circuit analysis by considering the effect of supply voltages one at a time.
- A. Thevenin's theorem
 - B. Norton's theorem
 - C. Superposition
 - D. KVL

ANSWER: C

56. Three resistors, $R_1 = 60 \Omega$, $R_2 = 80 \Omega$ and $R_3 = 100$ are connected in delta. If the network is to be transformed into star, what would be the value of the resistor opposite of R_2 ?
- A. 25.0 Ω
 - B. 33.3 Ω
 - C. 45.0 Ω
 - D. 56.7 Ω

ANSWER: A

57. The description of two sine waves that are in step with each other going through their maximum and minimum points at the same time and in the same direction
- A. phased sine wave
 - B. sine waves in phase
 - C. sine wave in coordination
 - D. stepped sine waves

ANSWER: B

58. Most ac-supplies are in the form of
- A. sine-wave
 - B. square-wave
 - C. triangular-wave
 - D. rectangular-wave

ANSWER: A

59. Advantage(s) of ac over dc
- A. economically produced
 - B. transmission of ac is more efficient
 - C. ac voltages can be easily changed
 - D. all of the above

ANSWER: D

60. An ac-voltage has an equation $v = 240 \sin 120\pi t$, its frequency is
- A. 60 Hz
 - B. 90 Hz
 - C. 120 Hz
 - D. 240 Hz

ANSWER: A

61. When can an ac-voltage, $v = 120\sin 120\pi t$ reach its first peak?

- A. 4.167 μ s
- B. 8.334 μ s
- C. 4.167 ms
- D. 8.334 ms

ANSWER: C

62. Calculate the period of an alternating current having an equation of $I = 20\sin 120\pi t$.

- A. 4.167 ms
- B. 8.33 ms
- C. 16.67 ms
- D. 33.33 ms

ANSWER: C

63. The time taken by an alternating voltage, $v = 100\sin 240\pi t$ to reach 50V for the first time

- A. 358 μ s
- B. 695 μ s
- C. 358 ms
- D. 695 ms

ANSWER: D

64. An alternating voltage of sine-wave form has a maximum voltage of 311V. What is its value at 225° ?

- A. 110 V
- B. 220 V
- C. -220 V
- D. -110 V

ANSWER: C

65. If an alternating voltage has a magnitude of 10 V at 30° , what is its maximum voltage?

- A. 20 V
- B. 30 V
- C. 40 V
- D. 50 V

ANSWER: A

66. What is the frequency of an alternating current, if it reaches 90° within 4.167 ms?

- A. 20 Hz
- B. 30 Hz
- C. 50 HZ
- D. 60 Hz

ANSWER: D

67. At what angle does an alternating voltage of cosine-waveform reaches its negative peak?

- A. 45°
- B. 90°
- C. 135°
- D. 180°

ANSWER: D

68. When comparing rms voltages and average voltages, which of the following statement is true, assuming sine waves?
- A. Either the rms voltage or the average voltage might be larger
 - B. The rms voltage is always greater than the average voltage
 - C. There will always be a very large difference between the rms voltage and the average voltage
 - D. The average voltage is always greater than the rms voltage

ANSWER: B

69. What is the average voltage of an alternating voltage, $v = 100\sin 120\pi t$?
- A. 31.8 V
 - B. 63.6 V
 - C. 70.71 V
 - D. 0 (zero) V

ANSWER: D

70. Determine the effective voltage of $v = 100\sin 120\pi t$.
- A. 31.80 V
 - B. 35.35 V
 - C. 70.71 V
 - D. 90.00 V

ANSWER: D

71. What do you mean by root-mean-squared (rms) value?
- A. it is the average value
 - B. it is the effective value
 - C. it is the value that causes the same heating effect as a dc-voltage
 - D. B or C

ANSWER: D

72. The power dissipated across the resistance in an AC circuit
- A. real power
 - B. reactive power
 - C. apparent power
 - D. true power

ANSWER: D

73. In AC circuit, resistors will dissipate what power?
- A. reactive
 - B. passive
 - C. inductive
 - D. true

ANSWER: D

74. In an ac-circuit, if the voltage and current are in phase, the circuit is
- A. resistive
 - B. reactive
 - C. capacitive
 - D. inductive

ANSWER: A

75. If the current in an ac-circuit leads the voltage by 90° , the circuit is

- A. resistive
- B. capacitive
- C. inductive
- D. purely inductive

ANSWER: B

76. In a purely inductive circuit the current

- A. leads the voltage by 45°
- B. leads the voltage by 90°
- C. lags the voltage by 90°
- D. lags the voltage by 45°

ANSWER: C

77. If the current and voltage in an ac-circuit has a phase difference, it would mean the load is

- A. resistive
- B. capacitive
- C. inductive
- D. reactive

ANSWER: D

78. A resistive and a capacitive load of equal magnitude is connected in series, determine the phase difference between the voltage and the current.

- A. current leads the voltage by 45°
- B. current lags the voltage by 45°
- C. current leads the voltage by 90°
- D. current lags the voltage by 90°

ANSWER: A

79. The reactance of a 25 mH coil at 500 Hz is which of the following?

- A. 785 ohms
- B. 785,000 ohms
- C. 13 ohms
- D. 0.0013 ohms

ANSWER: A

80. The impedance in the study of electronics is represented by resistance and _____.

- A. inductance and capacitance
- B. inductance
- C. reactance
- D. capacitance

ANSWER: C

81. A series circuit consists of an 80 mH inductor and a $150\mu\text{F}$ capacitor. Calculate the total reactance if it is connected to a 220-volt 60-cycle source.

- A. $12.5\ \Omega$ inductive
- B. $12.5\ \Omega$ capacitive
- C. $47.8\ \Omega$ inductive
- D. $47.8\ \Omega$ capacitive

ANSWER: A

82. Ignoring any inductive effects, what is the impedance of RC series capacitor made up of a 56 kilo ohms resistor and a 0.33 μ F capacitor at a signal frequency of 450 Hz?
- A. 66,730 ohms
 - B. 57,019 ohms
 - C. 45,270 ohms
 - D. 10,730 ohms

ANSWER: B

83. A 220-volt, 60-Hz source is driving a series RL circuit. Determine the current in the circuit if $R = 100 \Omega$ and $X_L = 100 \Omega$.
- A. 1.10 A (lagging)
 - B. 1.55 A (lagging)
 - C. 2.20 A (lagging)
 - D. 4.40 A (lagging)

ANSWER: B

84. How many electrical degrees a current will lead the voltage in a series RC load with $R = 100 \Omega$ and $X_C = 50 \Omega$?
- A. 13.28°
 - B. 26.56°
 - C. 31.72°
 - D. 63.44°

ANSWER: B

85. What will be the current equation in a series RC network if supplied with $v = V_m \sin 120\pi t$ source. The circuit has a power factor $\text{pf} = 0.5$?
- A. $i = I_{\max} \sin(120\pi t + 60)$
 - B. $i = I_{\max} \sin(120\pi t - 60)$
 - C. $i = I_{\max} \sin(120\pi t + 30)$
 - D. $i = I_{\max} \sin(120\pi t - 30)$

ANSWER: A

86. The power factor (pf) of a series LC circuit is
- A. 0
 - B. 0.5
 - C. 0.75
 - D. 1.0

ANSWER: A

87. What is the power factor (pf) of a series RL circuit having $R = 50\Omega$ and $X_L = 20\Omega$?
- A. 0.63
 - B. 0.71
 - C. 0.81
 - D. 0.93

ANSWER: D

88. A 200Ω resistor if connected in series with a capacitive reactance of 100 will give a total circuit impedance of
- A. 173.2Ω

- B. 223.6 Ω
 - C. 250.6 Ω
 - D. 300.0 Ω
- ANSWER: B

89. What will happen when the power factor of a circuit is increased?

- A. reactive power increases
- B. active power increases
- C. both active and reactive powers increases
- D. both active and reactive powers decreases

ANSWER: B

90. A series RL network is supplied with a 200-volt, 60-cycle source. If the voltage across the resistor R is 100 V, what is the voltage across the inductor L?

- A. 0 V
- B. 100 V
- C. 173.2 V
- D. 200 V

ANSWER: C

91. A 6- Ω resistor is connected in series with a capacitive reactance of 8 Ω . If the supply voltage is 200 V, what is the power consumed by the circuit?

- A. 2400 W
- B. 4000 W
- C. 5000 W
- D. 6666.67 W

ANSWER: A

92. A 6- Ω resistor is connected in series with a capacitive reactance of 8 Ω . If the supply voltage is 200 V, what is the circuit current magnitude?

- A. 14.28 A
- B. 20 A
- C. 25 A
- D. 33.33 A

ANSWER: B

93. A 6- Ω resistor is connected in series with a capacitive reactance of 8 Ω . If the supply voltage is 200 V, what is the apparent power of the circuit?

- A. 1200 W
- B. 2400 W
- C. 3200 W
- D. 4000 W

ANSWER: D

94. The apparent power of a series RC network is given to be 4000 W. If $R = 6 \Omega$, and $X_C = 8 \Omega$, calculate the true power of the network.

- A. 1200 W
- B. 2400 W
- C. 3200 W
- D. 4000 W

ANSWER: B

95. A series RC circuit has an apparent power of 4000 W. If $R = 6\Omega$, and $X_C = 8\Omega$, determine the reactive power.

- A. 1200 W
- B. 2400 W
- C. 3200 W
- D. 4000 W

ANSWER: C

96. A network has a true power and a reactive power of 2400 W and 3200 W respectively. What is its apparent power?

- A. 800 W
- B. 1600 W
- C. 4000 W
- D. 5600 W

ANSWER: C

97. What is the total impedance of a series circuit consisting of $R = 6\Omega$, $X_C = 8\Omega$, and $X_L = 16\Omega$?

- A. 10 Ω
- B. 14 Ω
- C. 24.73 Ω
- D. 30 Ω

ANSWER: A

98. What is the significance of connecting loads in parallel?

- A. it makes power consumption less
- B. it provides greater efficiency
- C. it increases the safety factor
- D. it allows independent operations of loads

ANSWER: D

99. A parallel RL circuit with $R = 60\Omega$, and $X_L = 40\Omega$ has a total impedance of

- A. 24.3 Ω
- B. 28.3 Ω
- C. 33.3 Ω
- D. 38.3 Ω

ANSWER: C

100. Calculate the total impedance of a parallel RC circuit if $R = X_C = 50\Omega$.

- A. 25 @ $45^\circ \Omega$
- B. 25 @ $-45^\circ \Omega$
- C. 35.35 @ $45^\circ \Omega$
- D. 35.35 @ $-45^\circ \Omega$

ANSWER: D

101. A 100-volt source is supplying a parallel RC circuit having a total impedance of 35.35 Ω . Calculate the total line current.

- A. 2.83 $\angle 45^\circ$
- B. 2.83 $\angle -45^\circ$
- C. 4.00 $\angle 45^\circ$

D. $4.00 \angle -45^\circ$
ANSWER: A

102. What is the power factor of a circuit if the inductive susceptance and conductance have the same value?

- A. 0.325
- B. 0.525
- C. 0.673
- D. 0.707

ANSWER: D

103. If a circuit has an admittance of $Y = 0.2 + j0.6$, the circuit is

- A. purely inductive
- B. inductive
- C. capacitive
- D. reactive

ANSWER: C

104. The circuit admittance $Y = 0.2 - j0.6$, the circuit is

- A. resistive
- B. inductive
- C. capacitive
- D. reactive

ANSWER: B

105. What is the resonant frequency of a circuit when L is 50 microhenrys and C is 40 picofarads are in parallel?

- A. 7.96 MHz
- B. 79.6 MHz
- C. 3.56 MHz
- D. 1.78 MHz

ANSWER: C

106. If you need an LC circuit to be resonant at 2500 Hz and use a 150 mH coil, what should the capacitance value be?

- A. $0.027 \mu\text{F}$
- B. $0.015 \mu\text{F}$
- C. $0.15 \mu\text{F}$
- D. $27 \mu\text{F}$

ANSWER: A

107. What is the resonant frequency of a circuit when L of 3 microhenry and C of 40 picofarad are in series?

- A. 1.33 MHz
- B. 14.5 MHz
- C. 14.5 kHz
- D. 1.33 kHz

ANSWER: B

108. What is the resonant frequency of a circuit when L of 25 microhenry and C of 10 picofarad are in parallel?

- A. 63.7 MHz
 - B. 10.1 MHz
 - C. 63.7 kHz
 - D. 10.1 kHz
- ANSWER: B

109. A series circuit at resonance would mean, the circuit is
- A. resistive
 - B. inductive
 - C. capacitive
 - D. reactive
- ANSWER: A

110. Characteristics of the current in a series R-L-C circuit at resonance.
- A. It is dc
 - B. It is a minimum
 - C. It is zero
 - D. It is at maximum
- ANSWER: D

111. What is the cause of a minimum Q on a single-tuned LC circuit?
- A. decreased series resistor
 - B. decreased shunt resistor
 - C. increased shunt resistor
 - D. decreased capacitance
- ANSWER: C

112. Find the half-power bandwidth of a parallel resonant circuit, which has a resonant frequency of 3.6 MHz and a Q of 218.
- A. 606 kHz
 - B. 58.7 kHz
 - C. 16.5 kHz
 - D. 47.3 kHz
- ANSWER: C

113. A parallel circuit at resonance would mean, the circuit is
- A. resistive
 - B. inductive
 - C. reactive
 - D. capacitive
- ANSWER: A

114. What will happen to a parallel ac-circuit if its line frequency is more than the resonant frequency?
- A. becomes purely resistive
 - B. becomes purely capacitive
 - C. becomes inductive
 - D. becomes capacitive
- ANSWER: D

115. In a series ac-circuit, if the line frequency is more than the resonant frequency, the circuit behaves as

- A. resistive
- B. inductive
- C. reactive
- D. capacitive

ANSWER: B

116. If the line frequency of a parallel ac-circuit is less than the resonant frequency, the circuit behaves as

- A. resistive
- B. reactive
- C. capacitive
- D. purely inductive

ANSWER: B

117. If an ac-series circuit is supplied with a source whose frequency is less than that of f_r , the circuit becomes

- A. resistive
- B. reactive
- C. inductive
- D. capacitive

ANSWER: D

118. _____ is a parallel LC circuit.

- A. Parallel resisting circuit
- B. Static circuit
- C. Tank circuit
- D. Hartley circuit

ANSWER: C

119. A parallel LC network with $L = 100 \text{ mH}$ and $C = 25 \mu\text{F}$ will resonate at what frequency?

- A. 25 Hz
- B. 45.5 Hz
- C. 75.6 Hz
- D. 100 Hz

ANSWER: D

120. Absolutely, when can we say that the circuit is at resonance?

- A. when $X_L = X_C$
- B. when the current is minimum
- C. when the voltage and current are in-phase
- D. all of the above

ANSWER: C