

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY-2008**II B.TECH SUPPLEMENTARY EXAMINATIONS
PULSE AND DIGITAL CIRCUITS
(BIO-MEDICAL ENGINEERING)****AUG/SEP-2008****MARK-3 HOUR
MARK-80****ANSWER ANY FIVE QUESTIONS. ALL QUESTIONS CARRY EQUAL MARKS.****MARKS [16*5=80]**

1. (a) A symmetrical square wave is applied to a HP circuit having $R = 20 \text{ k}$ and $C = 0.05 \mu \text{ f}$. If the frequency of input signal is 1 kHz and the signal swings $\pm 0.5 \text{ V}$, draw the output wave shape and indicate the voltages.
(b) What happens if the signal frequency of the signal is reduced to 100 Hz ? Show output curve.
2. (a) Explain the response of the clamping circuit when a square wave input is applied under steady state conditions.
(b) Explain the effect of diode characteristics on clamping voltage.
3. Write Short notes on:
 - (a) Diode switching times
 - (b) Switching characteristics of transistors
 - (c) FET as a switch.
4. (a) What are the different types of multivibrators? Name them and sketch their circuits.
(b) Design an astable multi for an o/p amplitude of 15 V and square wave frequency of 500 Hz . Assume $h_{FEmin} = 50$, $I_{Csat} = 5 \text{ mA}$ and $V_{CEsat} = 0$.
5. (a) With the help of a neat circuit diagram and waveforms explain the working of a transistor Miller time base generator.
(b) Find the component values of a bootstrap sweep generator, given $V_{cc} = 18 \text{ V}$, $I_{c(sat)} = 2 \text{ mA}$ and $h_{fe(min)} = 30$.
6. (a) Explain the factors which influence the stability of a relaxation divider with the help of a neat waveforms.
(b) A UJT sweep operates with $V_v = 3 \text{ V}$, $V_p = 16 \text{ V}$ and $\eta = 0.5$. A sinusoidal synchronizing voltage of 2 V peak is applied between bases and the natural frequency of the sweep is 1 kHz , over what range of sync signal frequency will the sweep remain in 1:1 synchronism with the sync signal?
7. (a) What is sampling gate? Explain how it differ from Logic gates?
(b) What is pedestal? How it effects the output of a sampling gates?
(c) What are the drawbacks of two diode sampling gate?
8. (a) Why totem pole is used in DTL? Draw the circuit diagram and explain a DTL gate with this.
(b) Verify the truth table of RTL NOR gate with the circuit diagram of two inputs.