

Solutions of

of

Electrical Engineering

GATE-2016

Session 8 | Set-2



MADE EASY

India's Best Institute for IES, GATE & PSUs

Write us at info@madeeasy.in | Phone: 011-45124612, 9958995830

www.madeeasy.in

Section - I (General Aptitude)

One Mark Questions

Q.1 The chairman requested the aggrieved shareholders to _____ him.

- (a) bare with (b) bore with
(c) bear with (d) bare

Ans. (c)

• • • End of Solution

Q.2 Identify the correct spelling out of the given options:

- (a) Managable (b) Manageable
(c) Mangaible (d) Managible

Ans. (b)

• • • End of Solution

Q.3 Pick the odd one out in the following:

13, 23, 33, 43, 53

- (a) 23 (b) 33
(c) 43 (d) 53

Ans. (b)

13, 23, 43, 53 are all prime numbers.
only 33 is composite 33, (11 × 3)
odd one out is 33.

• • • End of Solution

Q.4 R2D2 is a robot. R2D2 can repair aeroplanes. No other robot can repair aeroplanes. Which of the following can be logically inferred from the above statements?

- (a) R2D2 is a robot which can only repair aeroplanes.
(b) R2D2 is the only robot which can repair aeroplanes.
(c) R2D2 is a robot which can repair only aeroplanes.
(d) Only R2D2 is a robot.

Ans. (b)

• • • End of Solution

Q.5 If $|9y - 6| = 3$, then $y^2 - \frac{4y}{3}$ is_____.

- (a) 0 (b) $+\frac{1}{3}$
(c) $-\frac{1}{3}$ (d) undefined

Ans. (c)

$$|9y - 6| = 3$$

\Rightarrow Either $(9y - 6 = 3)$ or $(9y - 6 = -3)$

$$\Rightarrow [y = 1] \text{ or } \left[y = \frac{1}{3} \right]$$

$$\left[y^2 - \frac{4y}{3} \right]$$

$$\text{put } y = \frac{1}{3}, \left(\frac{1}{3} \right)^2 - \frac{4}{3} \times \frac{1}{3} = -\frac{1}{3}$$


$$\text{or } y^2 - \frac{4y}{3}$$

$$\text{put } y = 1, 1^2 - \frac{4}{3} = -\frac{1}{3}$$

• • • End of Solution

Two Mark Questions

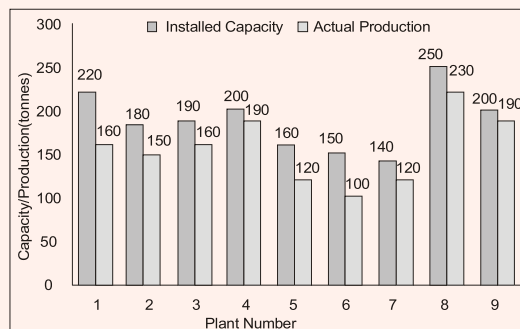Q.6 The following graph represents the installed capacity for cement production (in tonnes) and the actual production (in tonnes) of nine cement plants of a cement company. Capacity utilization of a plant is defined as ratio of actual production of cement to installed capacity. A plant with installed capacity of at least 200 tonnes is called a large plant and a plant with lesser capacity is called a small plant. The difference between total production of large plants and small plants, in tonnes is _____.



Ans. (120)

According to information in Question

Large plants are 1, 4, 8, 9 which are having installed capacity of at least 200 tonnes.

Total production of large plant $[160 + 190 + 230 + 190] = 770$

Remaining plant number 2, 3, 5, 6, 7 all are small plants with capacity less than 200 tonnes.

Total production of small plants = $150 + 160 + 120 + 100 + 120 = 650$

Difference = $750 - 650 = 120$

● ● ● **End of Solution**

Q.7 A poll of students appearing for masters in engineering indicated that 60 % of the students believed that mechanical engineering is a profession unsuitable for women. A research study on women with masters or higher degrees in mechanical engineering found that 99 % of such women were successful in their professions.

Which of the following can be logically inferred from the above paragraph?

- (a) Many students have misconceptions regarding various engineering disciplines.
- (b) Men with advanced degrees in mechanical engineering believe women are well suited to be mechanical engineers.
- (c) Mechanical engineering is a profession well suited for women with masters or higher degrees in mechanical engineering.
- (d) The number of women pursuing higher degrees in mechanical engineering is small.

Ans. (a)

● ● ● **End of Solution**

Q.8 Sourya committee had proposed the establishment of Sourya Institutes of Technology (SITs) in line with Indian Institutes of Technology (IITs) to cater to the technological and industrial needs of a developing country.

Which of the following can be logically inferred from the above sentence?

Based on the proposal,

- (i) In the initial years, SIT students will get degrees from IIT.
 - (ii) SITs will have a distinct national objective.
 - (iii) SIT like institutions can only be established in consultation with IIT.
 - (iv) SITs will serve technological needs of a developing country.
- (a) (iii) and (iv) only. (b) (i) and (iv) only.
(c) (ii) and (iv) only (d) (ii) and (iii) only

Ans. (c)

● ● ● **End of Solution**

Q.9 Shaquille O' Neal is a 60% career free throw shooter, meaning that he successfully makes 60 free throws out of 100 attempts on average. What is the probability that he will successfully make exactly 6 free throws in 10 attempts?

- (a) 0.2508 (b) 0.2816
(c) 0.2934 (d) 0.6000

Ans. (a)

$$\text{Probability of free throw} = \frac{60}{100} = .6$$

$$\text{Probability of NOT free throw} = 1 - .6 = .4$$

So required probability of exactly 6 throws in 10 attempts will be given by

$${}^{10}C_6 (.6)^6 \times (.4)^4 = .2508$$

● ● ● End of Solution

Q.10 The numeral in the units position of $211^{870} + 146^{127} \times 3^{424}$ is_____.

Ans. (7)

$$\text{Unit digit of } 211^{870} + 146^{127} \times 3^{424} \text{ is } 1 + 6 \times 1 = 7$$

● ● ● End of Solution

Section - II (Electrical Engineering)

One Mark Questions

Q.1 The output expression for the Karnaugh map shown below is

BC A	00	01	11	10
0	1	0	0	1
1	1	1	1	1

- (a) $A + \bar{B}$ (b) $A + \bar{C}$
(c) $\bar{A} + \bar{C}$ (d) $\bar{A} + C$

Ans. (b)


BC A	00	01	11	10
0	1	0	0	1
1	1	1	1	1

$$F = A + \bar{C}$$

● ● ● End of Solution

Ans. (10)

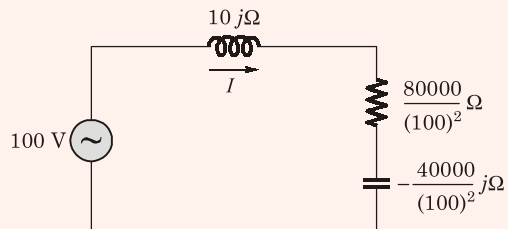The above circuit can be drawn by transferring secondary circuit to primary side.



$$I = \frac{100v}{(8 + 10j - 4j)\Omega}$$

$$= \frac{100V}{(8 + 6j)\Omega}$$

So the rms value of I will be 10 A.

● ● ● **End of Solution**

Q.4 Consider a causal LTI system characterized by differential equation $\frac{dy(t)}{dt} + \frac{1}{6}y(t) = 3x(t)$. The response of the system to the input $x(t) = 3e^{-\frac{t}{3}}u(t)$, where $u(t)$ denotes the unit step function, is

- (a) $9e^{-\frac{t}{3}}u(t)$. (b) $9e^{-\frac{t}{6}}u(t)$.
 (c) $9e^{-\frac{t}{3}}u(t) - 6e^{-\frac{t}{6}}u(t)$. (d) $54e^{-\frac{t}{6}}u(t) - 54e^{-\frac{t}{3}}u(t)$.

Ans. (d)

The differential equation

$$\frac{dy(t)}{dt} + \frac{1}{6}y(t) = 3x(t)$$

So, $sY(s) + \frac{1}{6}Y(s) = 3X(s)$

$$Y(s) = \frac{3X(s)}{\left(s + \frac{1}{6}\right)}$$

$$X(s) = \frac{9}{\left(s + \frac{1}{3}\right)}$$

So,
$$Y(s) = \frac{9}{\left(s + \frac{1}{3}\right)\left(s + \frac{1}{6}\right)} = \frac{54}{\left(s + \frac{1}{6}\right)} - \frac{54}{\left(s + \frac{1}{3}\right)}$$

So,
$$y(t) = (54e^{-1/6t} - 54e^{-1/3t}) u(t)$$

• • • End of Solution

Q.5 Suppose the maximum frequency in a band-limited signal $x(t)$ is 5 kHz. Then, the maximum frequency in $x(t) \cos(2000 \pi t)$, in kHz, is _____.

Ans. (6)

Since $x(t)$ is band limited to 5 kHz then maximum frequency in $x(t) \cos(2000\pi t)$ is 6 kHz.

• • • End of Solution

Q.6 Consider the function $f(z) = z + z^*$ where z is a complex variable and z^* denotes its complex conjugate. Which one of the following is TRUE?

- (a) $f(z)$ is both continuous and analytic
- (b) $f(z)$ is continuous but not analytic
- (c) $f(z)$ is not continuous but is analytic
- (d) $f(z)$ is neither continuous nor analytic

Ans. (b)

$$\begin{aligned} f(z) &= z + z^* \\ f(z) &= 2x && \text{is continuous (polynomial)} \\ u &= 2x & v &= 0 \\ u_x &= 2 & u_y &= 0 \\ v_x &= 0 & v_y &= 0 \end{aligned}$$

C.R. equation not satisfied.
 \therefore No where analytic.

• • • End of Solution

Q.7 A 3×3 matrix P is such that, $P^3 = P$. Then the eigenvalues of P are

- (a) 1, 1, -1
- (b) 1, $0.5 + j0.866$, $0.5 - j0.866$
- (c) 1, $-0.5 + j0.866$, $-0.5 - j0.866$
- (d) 0, 1, -1

Ans. (d)

By Cayley Hamilton theorem

$$\begin{aligned} \lambda^3 &= \lambda \\ \lambda &= 0, 1, -1 \end{aligned}$$

• • • End of Solution

- Q.8** The solution of the differential equation, for $t > 0$, $y''(t) + 2y'(t) + y(t) = 0$ with initial conditions $y(0) = 0$ and $y'(0) = 1$, is ($u(t)$ denotes the unit step function),
 (a) $te^{-t}u(t)$ (b) $(e^{-t} - te^{-t})u(t)$
 (c) $(-e^{-t} + te^{-t})u(t)$ (d) $e^{-t}u(t)$

Ans. (a)

The differential equation is

$$y''(t) + 2y'(t) + y(t) = 0$$

$$\text{So, } (s^2Y(s) - sy(0) - y'(0)) + 2[sY(s) - y(0)] + Y(s) = 0$$

$$\text{So, } Y(s) = \frac{sy(0) + y'(0) + 2y(0)}{(s^2 + 2s + 1)}$$

Given that $y'(0) = 1$, $y(0) = 0$

$$\text{So, } Y(s) = \frac{1}{(s+1)^2}$$

$$\text{So, } y(t) = te^{-t} u(t)$$

● ● ● End of Solution

- Q.9** The value of the line integral

$$\int_C (2xy^2 dx + 2x^2 y dy + dz)$$

along a path joining the origin $(0, 0, 0)$ and the point $(1, 1, 1)$ is

- (a) 0 (b) 2
(c) 4 (d) 6

Ans. (b)

$$\int_C \vec{F} \cdot \vec{dr}$$

where

$$\vec{F} = xy^2\vec{i} + 2x^2y\vec{j} + \vec{k}$$

$$\nabla \times \vec{F} = \vec{O}$$

(\vec{F} is irrotational $\Rightarrow \vec{F}$ is conservative)

$$\vec{F} = \nabla\phi \quad (\phi \text{ is scalar potential function})$$

$$\phi_x = 2xy^2$$

$$\phi_y = 2x^2y$$

$$\phi_z = 1$$

\Rightarrow

$$\phi = x^2y^2 + z + C$$

where, \vec{F} is conservative

$$\int_C \vec{F} \cdot d\vec{r} = \int_{(0,0,0)}^{(1,1,1)} d\phi = [x^2y^2 + z]_{(0,0,0)}^{(1,1,1)}$$

$$= 2$$

• • • End of Solution

Q.10 Let $f(x)$ be a real, periodic function satisfying $f(-x) = -f(x)$. The general form of its Fourier series representation would be

- (a) $f(x) = a_0 + \sum_{k=1}^{\infty} a_k \cos(kx)$ (b) $f(x) = \sum_{k=1}^{\infty} b_k \sin(kx)$
 (c) $f(x) = a_0 + \sum_{k=1}^{\infty} a_{2k} \cos(kx)$ (d) $f(x) = \sum_{k=0}^{\infty} a_{2k+1} \sin(2k+1)x$

Ans. (b)

Given that $f(-x) = -f(x)$


So function is an odd function.

So the Fourier series will have sine term only so

$$f(x) = \sum_{k=1}^{\infty} b_x \sin(kx)$$

• • • End of Solution

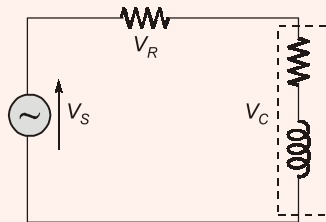Q.11 A resistance and a coil are connected in series and supplied from a single phase, 100 V, 50 Hz ac source as shown in the figure below. The rms values of plausible voltages across the resistance (V_R) and coil (V_C) respectively, in volts, are



- (a) 65, 35 (b) 50, 50
 (c) 60, 90 (d) 60, 80

Ans. (d)

Since $V_s = 100$ V, and the vector sum of V_R and V_C should be equal to V_s i.e.

$$V_s = \sqrt{V_R^2 + V_C^2}$$

From the option we get

$$V_R = 60 \text{ V}$$

$$V_C = 80 \text{ V}$$

• • • End of Solution

Q.12 The voltage (V) and current (A) across a load are as follows.

$$V(t) = 100 \sin(\omega t)$$

$$i(t) = 10 \sin(\omega t - 60^\circ) + 2 \sin(3\omega t) + 5 \sin(5\omega t).$$

The average power consumed by the load, in W , is _____.

Ans. (250)

Method 1:

The average power consumed by the load = $P = V_I I_1 \cos\phi_1$

$$= \frac{100}{\sqrt{2}} \cdot \frac{10}{\sqrt{2}} \cos 60^\circ = 250 \text{ W}$$

Method 2:

$$V(t) = 100 \sin(\omega t)$$

$$i(t) = 10 \sin(\omega t - 60^\circ) + 2 \sin(3\omega t) + 5 \sin(5\omega t)$$

(5 ωt)


$$P = V(t) i(t)$$

$$\begin{aligned} &= 1000 \sin \omega t \cdot \sin(\omega t - 60^\circ) + 200 \sin \omega t \cdot \sin 3\omega t + 500 \sin \omega t \sin 5\omega t \\ &= 500 [\cos(\omega t - \omega t + 60^\circ) - \cos(\omega t + \omega t - 60^\circ)] + 100 [\cos(\omega t - 3\omega t) - \cos(\omega t + 3\omega t)] \\ &+ 250 [\cos(\omega t - 5\omega t) - \cos(\omega t + 5\omega t)] \\ &= 500 [\cos 60^\circ - \cos(2\omega t - 60^\circ)] + 100 (\cos(-2\omega t) - \cos 4\omega t) \\ &+ 250 [\cos(-4\omega t) - \cos(6\omega t)] \\ &= 500 \cos 60^\circ = 250 \text{ W} \end{aligned}$$

average value of $\cos(2\omega t - 60^\circ)$, $\cos(2\omega t)$, $\cos(4\omega t)$, $\cos(6\omega t)$ will be zero.

• • • **End of Solution**

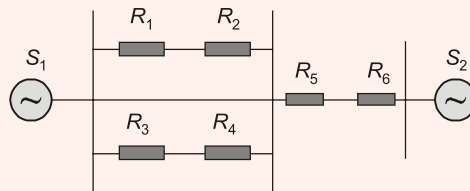Q.13 A power system with two generators is shown in the figure below. The system (generators, buses and transmission lines) is protected by six overcurrent relays R_1 to R_6 . Assuming a mix of directional and nondirectional relays at appropriate locations, the remote backup relays for R_4 are



(a) R_1, R_2

(b) R_2, R_6

(c) R_2, R_5

(d) R_1, R_6

Ans. (d)

• • • **End of Solution**

Q.14 A power system has 100 buses including 10 generator buses. For the load flow analysis using Newton-Raphson method in polar coordinates, the size of the Jacobian is

- (a) 189×189 (b) 100×100
(c) 90×90 (d) 180×180

Ans. (a)

Size of the Jacobian matrix is, $2m - m - 1 \times 2n - m - 1$

Given that 10 generator buses, we need to assume with in the 10 buses one bus as slack bus

then $(2 \times 100 - 10 - 1) \times (2 \times 100 - 10 - 1)$

$$189 \times 189$$

• • • **End of Solution**

Q.15 The inductance and capacitance of a 400 kV, three-phase, 50 Hz lossless transmission line are 1.6 mH/km/phase and 10 nF/km/phase respectively. The sending end voltage is maintained at 400 kV. To maintain a voltage of 400 kV at the receiving end, when the line is delivering 300 MW load, the shunt compensation required is

- (a) capacitive (b) inductive
(c) resistive (d) zero

Ans. (b)

$$Z_n = \sqrt{\frac{L}{C}} = \sqrt{\frac{1.6 \times 10^{-3}}{10 \times 10^{-9}}} = 400 \Omega$$

$$\text{SIL} = \frac{400 \times 400}{400} = 400 \text{ MW}$$

In the second case SIL decreases means Z_n increases.


Z_n increases with increase in inductance 'L'.

So, it is inductive

Load < SIL means, line behaves capacitive to compensate it inductor to be placed.

• • • **End of Solution**

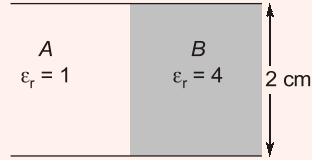- Q.16** A parallel plate capacitor filled with two dielectrics is shown in the figure below. If the electric field in the region A is 4 kV/cm, the electric field in the region B, in kV/cm, is



- (a) 1
(b) 2
(c) 4
(d) 16

Ans. (c)

As voltage is same across both the regions and distance between two plates is also same, then electric field remains same throughout the both region.

As we know
$$E = \frac{V}{d} = \text{constant for both regions.}$$

• • • **End of Solution**

- Q.17** A 50 MVA, 10 kV, 50 Hz, star-connected, unloaded three-phase alternator has a synchronous reactance of 1 p.u. and a sub-transient reactance of 0.2 p.u. If a 3-phase short circuit occurs close to the generator terminals, the ratio of initial and final values of the sinusoidal component of the short circuit current is _____.

Ans. (5.0)

$$I'' = \frac{E_g}{X_d''} ; I = \frac{E_g}{X}$$

$$\frac{I''}{I} = \frac{X}{X_d''} = \frac{1.0}{0.2} = 5.0 \text{ p.u.}$$

• • • **End of Solution**

- Q.18** Consider a linear time-invariant system with transfer function

$$H(s) = \frac{1}{(s+1)}$$

If the input is $\cos(t)$ and the steady state output is $A \cos(t + \alpha)$, then the value of A is _____.

Ans. (0.707)

$$H(s) = \frac{1}{(s+1)}$$

Put $s = j\omega$,

$$H(j\omega) = \frac{1}{j\omega + 1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2 + 1}}$$

\therefore input

$$x(t) = \cos(t)$$

Here $\omega = 1$ rad/sec

and

$$|x(t)| = 1$$

Hence, steady state output

$$y(t) = |x(t)| \times |H(j\omega)|_{\omega=1} \cos [t + \angle H(j\omega)]$$

$$A = |x(t)| \times |H(j\omega)|_{\omega=1}$$

$$A = \frac{1}{\sqrt{2}} = 0.707$$

• • • End of Solution

Q.19 A three-phase diode bridge rectifier is feeding a constant DC current of 100 A to a highly inductive load. If three-phase, 415 V, 50 Hz AC source is supplying to this bridge rectifier then the rms value of the current in each diode, in ampere, is _____.

Ans. (57.7)


In the 3- ϕ diode bridge rectifier each diode conducts for 120° for one complete cycle.

$$I_{D \text{ rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi/3} I_0^2 d\omega t} = I_0 \sqrt{\frac{2\pi}{2\pi \times 3}}$$

$$= \frac{I_0}{\sqrt{3}} = \frac{100}{\sqrt{3}} = 57.7 \text{ A}$$


• • • End of Solution

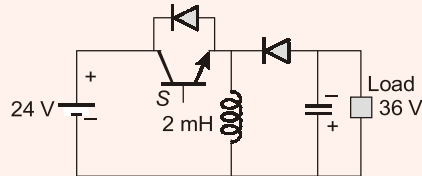- Q.20** A buck-boost DC-DC converter, shown in the figure below, is used to convert 24 V battery voltage to 36 V DC voltage to feed a load of 72 W. It is operated at 20 kHz with an inductor of 2 mH and output capacitor of 1000 μ F. All devices are considered to be ideal. The peak voltage across the solid-state switch (S), in volt, is _____.



Ans. (60)

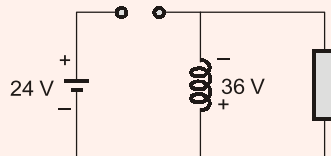
When switch 'S' is off, diode *D* is on then



$$\therefore \text{Peak voltage across switch} = 24 + 36 = 60 \text{ V}$$

• • • **End of Solution**

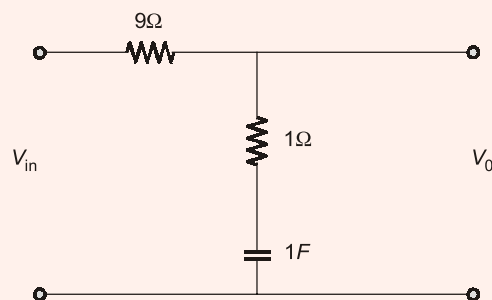- Q.21** For the network shown in the figure below, the frequency (in rad/s) at which the maximum phase lag occurs is, _____.



Ans. (0.316)

\therefore Assuming

Fig.

$$R_1 = 9 \Omega$$

$$R_2 = 1 \Omega$$

We can write,

$$\frac{V_o(s)}{V_{in}(s)} = \frac{R_2 + \frac{1}{sC}}{R_1 + R_2 + \frac{1}{sC}}$$

$$= \frac{1 + R_2.Cs}{1 + (R_1 + R_2)Cs}$$

$$= \frac{1 + R_2.Cs}{1 + \left(\frac{R_1 + R_2}{R_2}\right)R_2Cs}$$

Let $R_2C = T$

$$\frac{R_1 + R_2}{R_2} = \beta$$

Hence $\frac{V_o(s)}{V_{in}(s)} = \frac{1 + Ts}{(1 + \beta Ts)}$

which represent a lag compensator

\therefore here $T = R_2C = 1.1 = 1 \text{ sec}$

$$\beta = \frac{1 + 9}{1} = 10$$

Maximum phase lag occurs at frequency

$$\omega_n = \frac{1}{T\sqrt{\beta}} = \frac{1}{1\sqrt{10}}$$

$$= 0.316 \text{ rad/sec}$$

• • • End of Solution

Q.22 The direction of rotation of a single-phase capacitor run induction motor is reversed by

- (a) interchanging the terminals of the AC supply.
- (b) interchanging the terminals of the capacitor.
- (c) interchanging the terminals of the auxiliary winding.
- (d) interchanging the terminals of both the windings.

Ans. (c)
Inter changing the terminals of the auxiliary winding.

• • • End of Solution



MADE EASY

India's Best Institute for IES, GATE & PSUs

Crack in 1st Attempt

ESE, GATE & PSUs

• Best Faculty • Best Study Material • Best Results

Features of Classroom Courses

- Experienced Faculty
- GATE/ESE Test Series
- Updated Books and Reading References
- Regular classroom tests followed by discussions
- Doubt clearing sessions
- Interview Guidance Program
- Coverage of syllabus before GATE/ESE exams.
- Orientation sessions for GATE/ESE

ADMISSIONS OPEN *for* Session 2016-17

at all centre of MADE EASY

Delhi 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-16; **E-mail** : infodelhi@madeeasy.in **Ph.:** 011-45124612, 09958995830

Noida D-28 Sector-63 Noida, Uttar Pradesh; **E-mail**: infonoida@madeeasy.in **Ph.:** 0120-6524612, 08860378009

Lucknow B1/67, Sector P, Aliganj, Lucknow; **E-mail** : infolucknow@madeeasy.in **Ph.:** 09919111168, 08400029422

Jaipur AB-559, Kings Road, Nirman Nagar, Jaipur, Rajasthan; **E-mail** : infojaipur@madeeasy.in **Ph.:** 0141-4024612, 09166811228

Bhopal Plot No. 46 , Zone - 2 M.P. Nagar, Bhopal (Madhya Pradesh)- 462021; **E-mail** : infobhopal@madeeasy.in **Ph.:** 0755-4004612, 08120035652

Indore Gemini Mall, PU3, Opp. Orbit Mall, A.B. Road, Vijay Nagar, Indore; **E-mail** : infoindore@madeeasy.in **Ph.:** 0731-4029612, 07566669612

Pune II Floor, Business Bay, Plot No. 84, Near R.T.O. Shivaji Nagar, Pune; **E-mail** : infopune@madeeasy.in **Ph.:** 020-26058612, 09168884343

Hyderabad 5-1-744, Bank Street, Koti, Hyderabad-95; **E-mail** : infohyderabad@madeeasy.in **Ph.:** 040-24652324, 09160002324

Bhubaneswar Plot No-1441, CRPF Square, Opposite to IOCL Petrol Pump; **E-mail** : infobhubaneswar@madeeasy.in **Ph.:** 0674-6999888, 9040999888

Kolkata 755, Anandapur Next to Fortis Hospital Off-EM Bypass Kolkata; **E-mail** : infokolkata@madeeasy.in **Ph.:** 033-68888880, 08282888880

Patna Nutan Complex, Near Krrish Hyundai, Main Road, Kankarbagh, Patna; **E-mail** : infopatna@madeeasy.in **Ph.:** 9955991166

Corporate Office : 44-A/1, Kalu Sarai, Sarvapriya Vihar, New Delhi - 110016




011-45124612




www.madeeasy.in

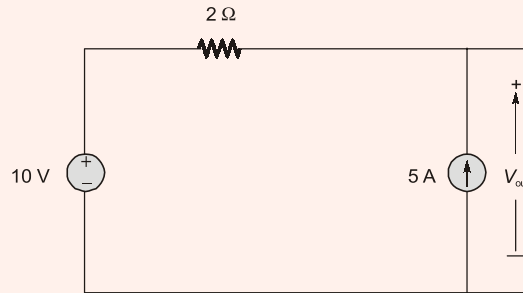Q.23 In the circuit shown below, the voltage and current sources are ideal. The voltage (V_{out}) across the current source, in volts, is



- (a) 0
(b) 5
(c) 10
(d) 20

Ans. (d)

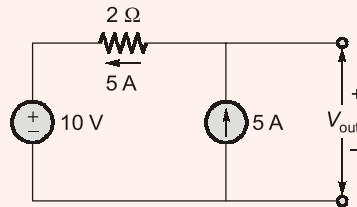

So
$$V_{out} = (5 \times 2) + 10$$
$$= 20 \text{ V}$$

● ● ● **End of Solution**

Q.24 The graph associated with an electrical network has 7 branches and 5 nodes. The number of independent KCL equations and the number of independent KVL equations, respectively, are

- (a) 2 and 5
(b) 5 and 2
(c) 3 and 4
(d) 4 and 3


Ans. (d)

Number of KCL equation = $n - 1 = 5 - 1 = 4$

Number of KVL equation = $b - (n - 1) = 7 - (5 - 1) = 3$


● ● ● **End of Solution**

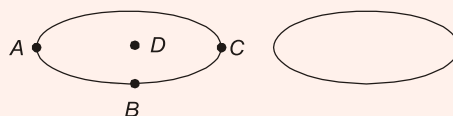Q.25 Two electrodes, whose cross-sectional view is shown in the figure below, are at the same potential. The maximum electric field will be at the point



- (a) A
(b) B
(c) C
(d) D

Ans. (c)

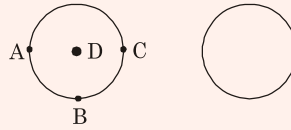

At the point C, \vec{E} (electric field intensity) is maximum being closest to the other plate.

• • • End of Solution

Two Mark Questions

Q.26 The Boolean expression $\overline{(a + \bar{b} + c + \bar{d}) + (b + \bar{c})}$ simplifies is

- (a) 1 (b) $\bar{a} \cdot \bar{b}$
(c) a, b (d) 0

Ans. (d)


$$F = \overline{(a + \bar{b} + c + \bar{d}) + (b + \bar{c})} = \overline{(a + \bar{b} + c + \bar{d})} \cdot \overline{(b + \bar{c})}$$

$$= \bar{a} \cdot b \cdot \bar{c} \cdot d \cdot \bar{b} \cdot c$$

$$F = 0$$


• • • End of Solution

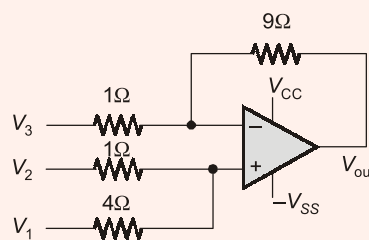Q.27 For the circuit shown below, taking the opamp as ideal, the output voltage V_{out} in terms of the input voltages V_1 , V_2 and V_3 is



- (a) $1.8V_1 + 7.2V_2 - V_3$ (b) $2V_1 + 8V_2 - 9V_3$
(c) $7.2V_1 + 1.8V_2 - V_3$ (d) $8V_1 + 2V_2 - 9V_3$

Ans. (d)

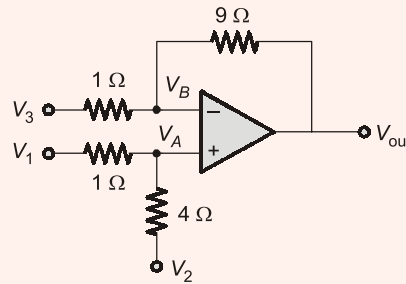


$$V_A = \left(\frac{4}{5} V_1 + \frac{1}{5} V_2 \right)$$

$$V_{out} = -9 V_3 + 10 V_A = -9 V_3 + 8 V_1 + 2 V_2$$

• • • End of Solution

Q.28 Let $x_1(t) \leftrightarrow X_1(\omega)$ and $x_2(t) \leftrightarrow X_2(\omega)$ be two signals whose Fourier Transforms are as shown in the figure below. In the figure, $h(t) = e^{-2|t|}$ denotes the impulse response.

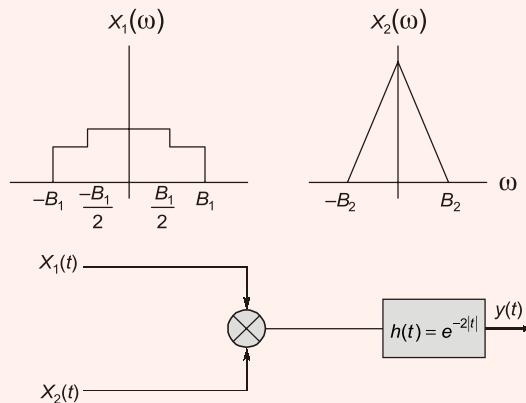

For the system shown above, the minimum sampling rate required to sample $y(t)$, so that $y(t)$ can be uniquely reconstructed from its samples, is

- (a) $2B_1$ (b) $2(B_1 + B_2)$
(c) $4(B_1 + B_2)$ (d) ∞

Ans. (b)

Given that,

$$\text{Bandwidth of } X_1(\omega) = B_1$$

$$\text{Bandwidth of } X_2(\omega) = B_2$$

System has $h(t) = e^{-2|t|}$ and input to the system is $x_1(t) \cdot x_2(t)$

The bandwidth of $x_1(t) \cdot x_2(t)$ is $B_1 + B_2$.