

Section – I

Question number 1-20 carry 1 mark each

- Q-meter works on the principle of
 - series resonance
 - parallel resonance
 - mutual inductance
 - self inductance
- The bridge circuit shown in Fig. Q2-I
 - cannot be balanced
 - can be balanced but the frequency of excitation must be known
 - can be balanced for only one frequency
 - can be balanced at any frequency

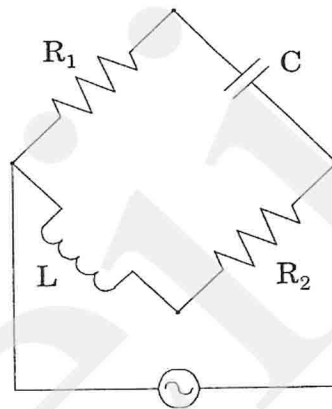


Fig. Q2-I

- Which one of the following statements is TRUE for an 'ideal' power diode?
 - Forward voltage drop is zero and reverse saturation current is non-zero.
 - Reverse recovery time is non-zero and reverse saturation current is zero.
 - Forward voltage drop is zero and reverse recovery time is zero.
 - Forward voltage drop is non-zero and reverse recovery time is zero.
- In a MOSFET, the pinch-off voltage refers to
 - drain-to-source voltage at which drain-to-source current is zero
 - gate-to-source voltage at which gate-to-source current is zero
 - drain-to-source voltage at which gate-to-source current is zero
 - gate-to-source voltage at which drain-to-source current is zero
- Which of the following statements is TRUE for DC switched mode power supply?
 - It cannot provide isolation between input and output as in rectifiers.
 - It cannot remove ripple as in DC switching mode regulators.
 - It has two stage conversions: dc-ac and ac-dc.
 - It is a type of chopper circuit.

6. Which one of the following is a ceramic insulator?
(A) Mica (B) Porcelain
(C) Liquid crystal (D) Synthetic fiber
7. Which one of the following represents a direct band-gap material?
(A) Si (B) Ge (C) GaP (D) GaAs
8. Which one of the following statements is **NOT** true?
(A) Rochelle salt exhibits ferroelectric property.
(B) Spontaneous polarization is a characteristic property of ferroelectric material.
(C) Spontaneous polarization of ferroelectric materials usually vanishes below ferroelectric Curie temperature.
(D) Ferroelectric materials exhibit hysteresis effect.
9. Which one of the following diodes contains a metal-semiconductor junction?
(A) Tunnel diode (B) Zener diode
(C) Schottky diode (D) Gunn diode
10. Which one of the following statements is **NOT** true?
(A) Ferrites can be used in transformer cores only at very low frequencies.
(B) Ferrites are ferrimagnetic material.
(C) Ferrites show spontaneous magnetization below certain temperature.
(D) DC resistivity of ferrites is many orders of ten higher than that of iron.
11. Which one of the following statements is **NOT** true?
(A) In an intrinsic semiconductor, concentration of electrons in the conduction band is same as the concentration of holes in the valance band.
(B) The probability of an energy state at the Fermi level being occupied by an electron is $1/2$.
(C) Mobility of electrons is higher than that of holes.
(D) In an n-type semiconductor, concentration of holes is equal to that of the intrinsic concentration.
12. $ABCD$ parameters of a two-port network is defined as $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$. If the port-2 is terminated by a resistance R_L , the admittance looking into the port-1 is
(A) $\frac{C + D R_L}{A + B R_L}$ (B) $\frac{C R_L + D}{A R_L + B}$ (C) $\frac{C R_L + D}{A + B R_L}$ (D) $\frac{C + D R_L}{A R_L + B}$
13. The phenomenon of injection electro-luminescence is the basis of working of
(A) photodiodes (B) light emitting diodes
(C) phototransistors (D) solar cells

14. A parallel combination of N resistances is connected across an ideal current source of I Amperes. The expression for the current in the k^{th} resistor R_k is

(A) $\left(\frac{R_k}{R_1 + R_2 + \dots + R_N} \right) I$ (B) $\left(\frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} \right) I$

(C) $\left(\frac{R_k}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} \right) I$ (D) $\left(\frac{\frac{1}{R_k}}{R_1 + R_2 + \dots + R_N} \right) I$

15. In the circuit shown in Fig. Q15-I, the voltage across the terminals A-B (in Volt) is

(A) $5 \angle 30^\circ$ (B) $12.5 \angle 30^\circ$ (C) $17 \angle 30^\circ$ (D) $25 \angle 30^\circ$

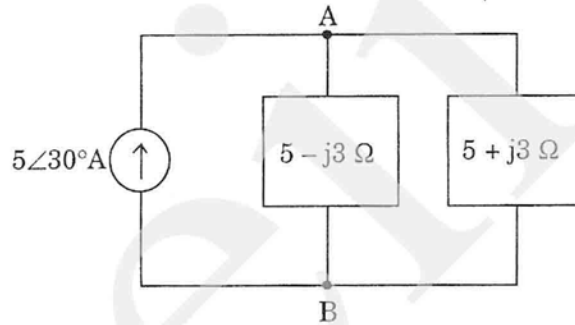


Fig. Q15-I

16. A half wave (i.e., $\lambda/2$) lossless transmission line of characteristic impedance Z_0 is terminated to a load of impedance Z_L as shown in the Fig. Q16-I. The input impedance as seen at the other end is

(A) $\frac{Z_L}{Z_0}$ (B) Z_L (C) $Z_L Z_0$ (D) $\frac{Z_L^2}{Z_0}$

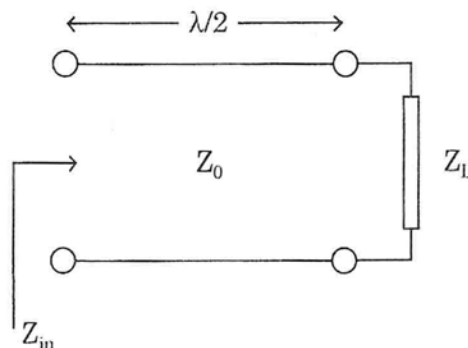


Fig. Q16-I

17. A microstrip line has a strip width W and a grounded dielectric substrate of thickness d and relative permittivity ϵ_r . Which one of the following statements is **NOT** true?
- (A) The effective dielectric constant ϵ_{eff} satisfies $1 < \epsilon_{eff} < \epsilon_r$.
 - (B) The effective dielectric constant ϵ_{eff} is a function of $\frac{W}{d}$.
 - (C) The characteristic impedance of the line is a function of $\frac{W}{d}$.
 - (D) The line can support pure TEM mode of wave propagation.
18. For a rectangular waveguide of internal dimensions a cm \times b cm, $a > b$, the mode of wave propagation with the lowest cut off frequency is
- (A) TE_{01}
 - (B) TE_{10}
 - (C) TE_{11}
 - (D) TM_{11}
19. The most appropriate value (in Ω) of the radiation resistance of a quarter wave monopole antenna is
- (A) 36.5
 - (B) 50
 - (C) 73
 - (D) 120
20. Which one of the following is an active transducer?
- (A) Photo-voltaic cell
 - (B) Strain gauge
 - (C) Photo-emissive cell
 - (D) Synchro

Question number 21-50 carry 2 marks each

21. A 0.1 A ammeter having a resistance of 10Ω is to be converted to a 1 A ammeter by using a shunt resistance. Which one of the followings is the most appropriate shunt resistance?
- (A) 0.1Ω
 - (B) 1.0Ω
 - (C) 1.1Ω
 - (D) 1.2Ω
22. The forward voltage drop of a power diode is $V_D = 1.0$ V at the diode current $I_D = 200$ A. Assuming the emission coefficient $\eta = 2$ and thermal voltage $V_T = 25.7$ mV, the reverse saturation current I_S (approximate) is
- (A) $71.08 \mu\text{A}$
 - (B) $51.20 \mu\text{A}$
 - (C) $21.09 \mu\text{A}$
 - (D) $41.09 \mu\text{A}$

23. In the circuit shown in Fig. Q23-I, the voltage across 25 kΩ resistor is to be measured by using a voltmeter of sensitivity of 1 kΩ/V. The magnitude of percentage error in the measurement is
 (A) 10 (B) 20 (C) 30 (D) 40

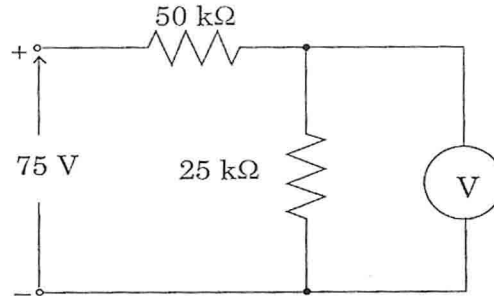


Fig. Q23-I

24. Fig. Q24-I shows some load voltage versus load current plots. Which one of them is **NOT** valid for the classification of dc-dc converters?
 (A) P (B) Q (C) R (D) S

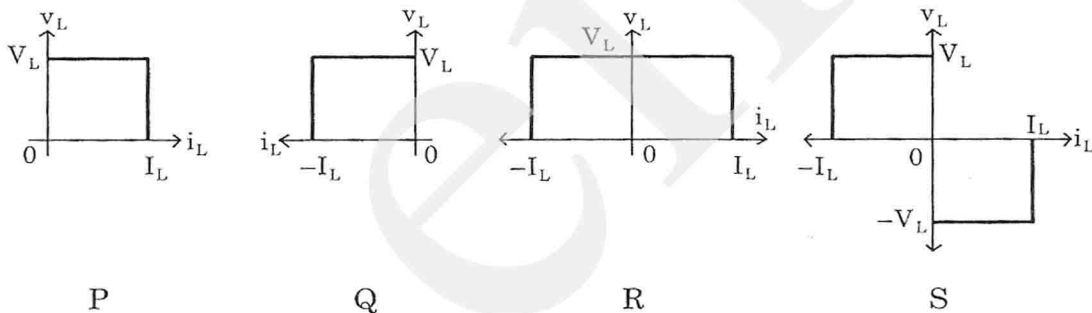


Fig. Q24-I

25. Two single phase inverters, one half-bridge and the other full-bridge, operating with equal inputs delivering power to identical loads. The ratio of, the power delivered, the first harmonic voltage and the total harmonic distortion, for full-bridge inverter to half-bridge inverter, respectively, are
 (A) 4, 2, 1 (B) 4, 2, 2 (C) 4, 1, 1 (D) 2, 1, 1

26. The correct match between Column A and Column B is

<u>Column A</u>	<u>Column B</u>
1. DC Switch	P. Boost Converter
2. Regulated DC-DC	Q. Cycloconverter
3. AC-to-AC	R. Inverter
4. DC-to-AC	S. MOSFET
(A) 1-R, 2-Q, 3-P, 4-S	(B) 1-S, 2-P, 3-Q, 4-R
(C) 1-P, 2-R, 3-Q, 4-S	(D) 1-S, 2-Q, 3-P, 4-R

27. For the power transistor circuit shown in Fig. Q27-I, $V_{CE(sat)} = 1.0 \text{ V}$, $V_{BE(sat)} = 1.5 \text{ V}$ and $\beta = 9$. With an overdrive factor of 2.5, the required resistance R_B for saturation is
- (A) 2.73Ω (B) 6.83Ω (C) 17Ω (D) 22.5Ω

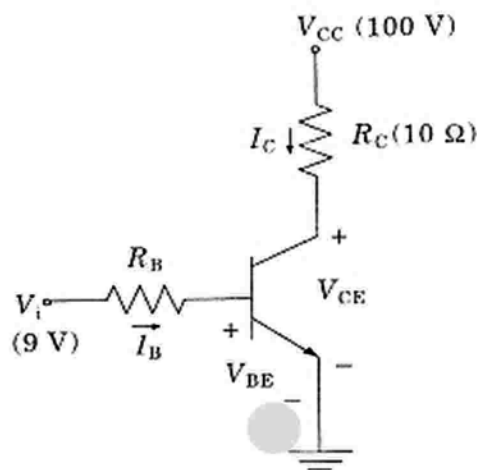


Fig. Q27-I

28. For a lossless air-filled cubical cavity of internal dimension 5 cm on each sides, the resonant frequency for the TE_{101} mode is
- (A) $5\sqrt{2}$ GHz (B) 5 GHz (C) $3\sqrt{2}$ GHz (D) 3 GHz
29. Which one of the following statements is **NOT** true?
- (A) For SCRs to be in the conduction state, the forward anode current must be greater than the latching current.
- (B) For SCRs to be in the forward blocking state, the forward anode current must be lower than the holding current.
- (C) When SCRs are in the conduction state, they can be turned off by applying suitable gate pulses.
- (D) When avalanche breakdown takes place, SCRs enter into the conduction state.
30. Consider two metallic wires W_1 and W_2 . They are made up of same material and each has circular cross section. The diameter of W_2 is twice that of W_1 and the length of W_2 is four times that of W_1 . Which one of the following statements is TRUE?
- (A) Resistance of W_1 is half that of W_2
- (B) Resistance of W_1 is equal to that of W_2
- (C) Resistance of W_1 is twice that of W_2
- (D) Resistance of W_1 is eight times that of W_2

31. A current of 1 A flows through a circular loop of superconducting wire having mean diameter of 1 m, cross section area of 1 mm^2 and self inductance of $4\pi \times 10^{-7} \text{ H}$. The current reduces to 0.99 A after 1 year. The resistivity of the wire is
- (A) $1.275 \times 10^{-26} \Omega\text{m}$ (B) $1.275 \times 10^{-25} \Omega\text{m}$
 (C) $1.275 \times 10^{-24} \Omega\text{m}$ (D) $1.275 \times 10^{-23} \Omega\text{m}$
32. An npn transistor is operating in CE mode and carries a collector current $I_c = 1 \text{ mA}$ when the collector to emitter voltage $V_{CE} = 1 \text{ V}$. If the early voltage for the transistor is 74 V and base to emitter voltage V_{BE} is kept constant, at $V_{CE} = 11 \text{ V}$ the collector current is
- (A) 15/19 mA (B) 1 mA (C) 19/15 mA (D) 19/12 mA

33. Two parallel plate capacitors shown in Fig. Q33-I (a) and Fig. Q33-I (b) have capacitances C_1 and C_2 , respectively. If $C_2 = 2C_1$, which one of the following relations is TRUE? (Neglect fringing effect)

- (A) $x = \frac{L}{4}$ (B) $x = \frac{L}{2}$ (C) $x = \frac{L}{3}$ (D) $x = \frac{2L}{3}$

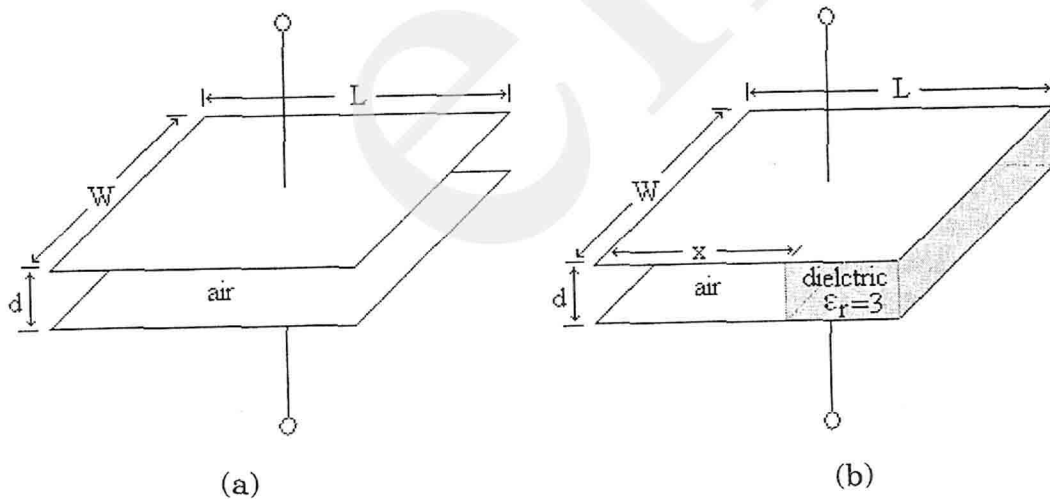


Fig. Q33-I

34. A doped semiconductor specimen has Hall coefficient $3.6 \times 10^{-4} \text{ m}^3 \text{ C}^{-1}$ and the resistivity $9 \times 10^{-3} \Omega\text{m}$. Assuming single carrier conduction, the mobility and density of carriers in the specimen, respectively, are (approximately)
- (A) $0.04 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ and $1.74 \times 10^{22} \text{ m}^{-3}$
 (B) $0.4 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ and $1.74 \times 10^{22} \text{ m}^{-3}$
 (C) $0.04 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ and $1.74 \times 10^{18} \text{ m}^{-3}$
 (D) $4.0 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ and $1.74 \times 10^{18} \text{ m}^{-3}$

35. If n , n_i , μ_n and μ_p , respectively denote electron concentration, intrinsic concentration, mobility of electrons and mobility of holes, the minimum conductivity of a semiconductor sample occurs at

- (A) $n = n_i \sqrt{\frac{\mu_p}{\mu_n}}$ (B) $n = n_i \sqrt{\frac{\mu_n}{\mu_p}}$
 (C) $n = n_i \sqrt{\mu_n \mu_p}$ (D) $n = n_i \sqrt{\mu_n + \mu_p}$

36. GaAs has bandgap energy of 1.42 eV. The material would produce photon output at a wavelength of (Planck's constant = 6.625×10^{-34} J-s, $q = 1.6 \times 10^{-19}$ C)

- (A) 0.553 μm (B) 0.653 μm (C) 0.875 μm (D) 0.953 μm

37. At a frequency of 1 GHz, the equivalent inductance between the terminals of a $\lambda/8$ (λ represents wavelength) short-circuited lossless 50Ω line is

- (A) $5/\pi$ nH (B) $15/\pi$ nH (C) $25/\pi$ nH (D) $50/\pi$ nH

38. For the circuit shown in Fig. Q38-I, the transistor parameters are $V_{BE} = 0.7$ V, $\beta = 99$. If V_C is to be set at 7.5 V, the required value (in k Ω) of R_B is

- (A) 172 (B) 136 (C) 100 (D) 82

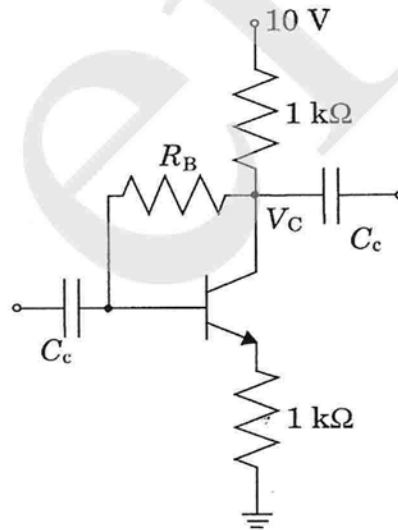


Fig. Q38-I

39. A quarter wave matching transformer is used to match a 30 Ω load to a line having characteristic impedance 120 Ω . The characteristic impedance of the quarter wave matching section is

- (A) 50 Ω (B) 60 Ω (C) 120 Ω (D) 150 Ω

40. If the average power delivered to a load terminated to a lossless transmission line is 75% of that of the incident power, the VSWR on the line is

- (A) 1/3 (B) 1 (C) 2 (D) 3

41. For the circuit shown in Fig. Q41-I, a value of R (in Ω), to which the voltage source would deliver 50% of the maximum deliverable power, is
 (A) 1 (B) 0.5 (C) 0.25 (D) $3 - \sqrt{8}$

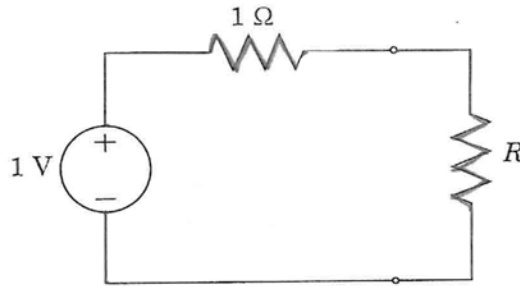


Fig. Q41-I

42. In the circuit shown in Fig. Q42-I (a), the current $I_1 = 2$ A. The current I_2 in Fig. Q42-I (b) is
 (A) -6 A (B) -4 A (C) 4 A (D) 6 A

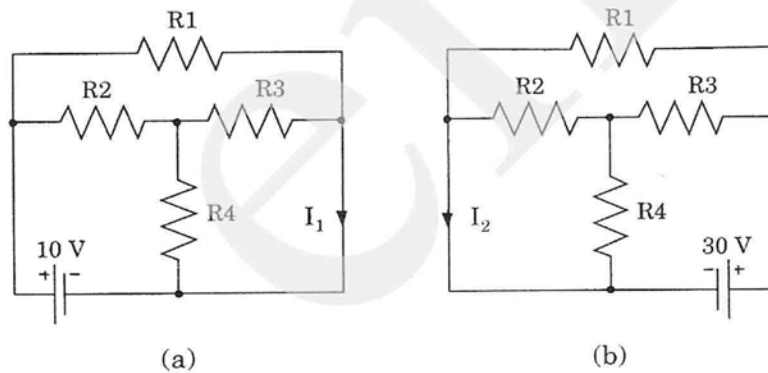


Fig. Q42-I

43. In the circuit shown in Fig. Q43-I, the current I through 2Ω resistor is
 (A) -94.34 mA (B) -70.34 mA (C) 70.34 mA (D) 94.34 mA

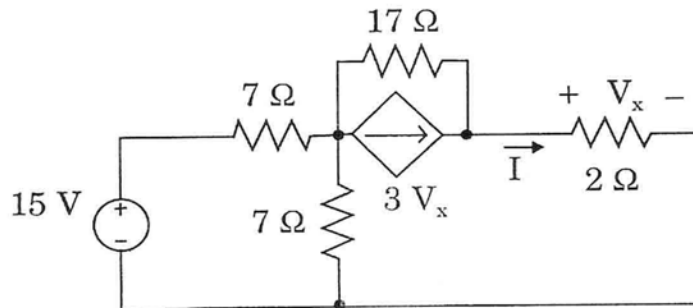


Fig. Q43-I

44. For the circuit shown in Fig. Q44-I, the Thevenin's voltage and resistance at terminals A and B, respectively, are

- (A) 8 V and 5 k Ω (B) 8 V and 10 k Ω
 (C) 4 V and 5 k Ω (D) 4 V and 10 k Ω

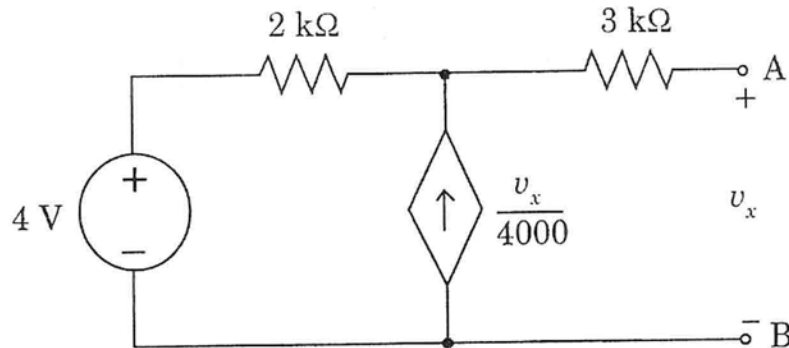


Fig. Q44-I

45. In the circuit shown in Fig. Q45-I, the switch closes at $t = 0$. Assuming steady state condition for $t = 0^-$, the current i_L at $t = 0.15$ sec is (approximately)

- (A) 0.04 A (B) 0.5 A (C) 0.76 A (D) 1.60 A

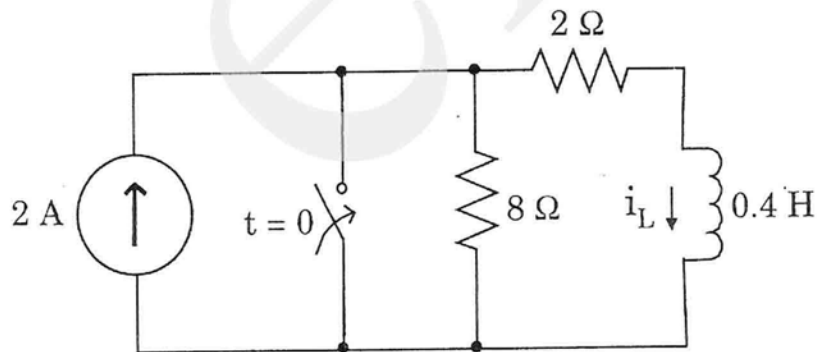


Fig. Q45-I

46. A PMMC instrument has a coil of dimensions 10 mm \times 10 mm and the flux density in the air gap is 2 mW/m². The coil has 100 turns. If a current of 5 mA produces an angular deflection of 90°, the spring constant of the instrument is

- (A) $\frac{2}{\pi} \times 10^{-8}$ N-m/rad (B) $\frac{\pi}{2} \times 10^{-8}$ N-m/rad
 (C) $\pi \times 10^{-8}$ N-m/rad (D) $\frac{1}{\pi} \times 10^{-8}$ N-m/rad

47. In the circuit shown in Fig. Q47-I, assume the diodes are ideal and the ammeter is an average indicating meter with zero internal resistance. The ammeter reading is

- (A) $\frac{0.4}{\pi}$ mA (B) $\frac{0.8}{\pi}$ mA (C) $\frac{0.4}{\sqrt{2}}$ mA (D) $\frac{0.8}{\sqrt{2}}$ mA

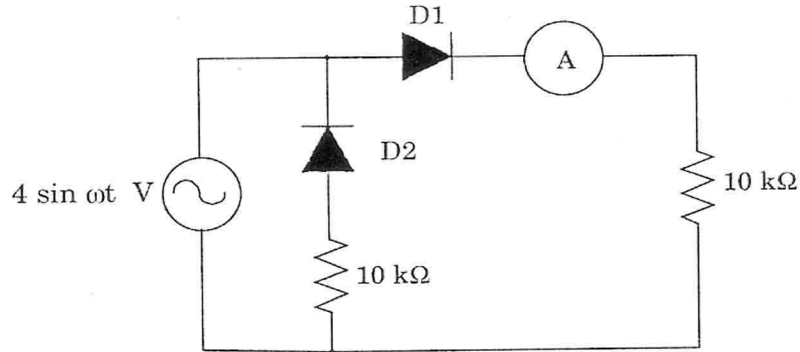


Fig. Q47-I

48. A capacitive transducer uses two quartz diaphragms of area 550 mm^2 each separated by a distance of 3.7 mm. A pressure of 750 kN/m^2 applied to the top diaphragm produces a displacement of 0.7 mm. The capacity is 390 pF when no pressure is applied to the diaphragm. The value of the capacitance after the application of pressure of 750 kN/m^2 is

- (A) 400 pF (B) 451 pF (C) 481 pF (D) 500 pF

49. A thermistor has a resistance of 500Ω at 30°C and has a temperature coefficient of $-5 \Omega/^\circ\text{C}$. This thermistor is used to measure the temperature of a system by the arrangement shown in Fig. Q49-I. If the system temperature falls to 20°C , the V_{AB} measured by the voltmeter is

- (A) $-10/29 \text{ V}$ (B) $-15/29 \text{ V}$ (C) $10/29 \text{ V}$ (D) $15/29 \text{ V}$

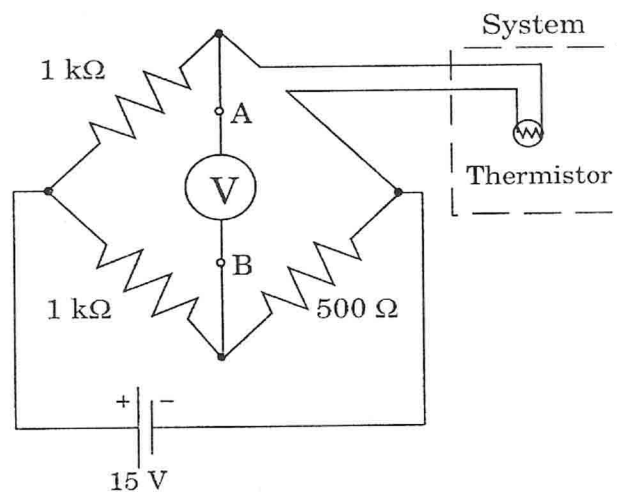


Fig. Q49-I

50. For the circuit shown in Fig. Q50-I, if the current $I = 3\text{ A}$, then the voltage V_2 is
(A) 2.5 V (B) 5 V (C) 8 V (D) 10 V

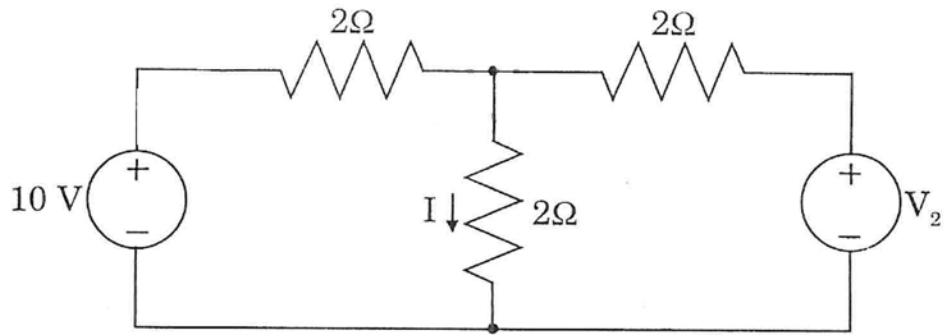


Fig. Q50-I



Section - II

Question number 1-20 carry 1 mark each

- Which one of the following statements is **NOT** true for a TWT?
 - The interaction region usually consists of a slow wave helix structure.
 - A static axial magnetic field keeps the electron beam focused.
 - Continued interaction takes place between the waves on a traveling wave structure and the electron beam.
 - TWT amplifiers are suitable only for narrowband microwave communication systems.
- The minimized form of the Boolean expression $F(A, B, C) = \Pi(0, 2, 3)$ is
 - $A + \overline{B}C$
 - $A + B\overline{C}$
 - $\overline{A}\overline{C} + B$
 - $\overline{A}\overline{B}\overline{C} + \overline{A}B$
- Number of address lines required to address 8 k bytes of memory is
 - 13
 - 14
 - 15
 - 16
- The standard binary code for alpha numeric characters is
 - ASCII
 - GRAY
 - BCD
 - Excess-3
- The 2's complement of the binary number 1101100 in BCD is
 - 12
 - 13
 - 14
 - 15
- In the op-amp circuit shown in Fig. Q6-II, the voltage ratio V_o/V_i is
 - 2
 - 1
 - 0.5
 - 0.5

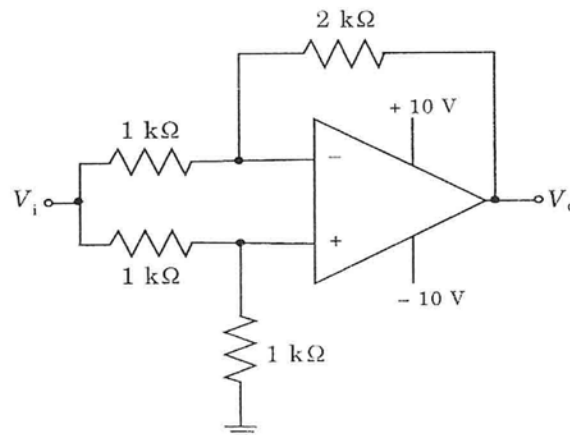


Fig. Q6-II

7. For the Schmitt trigger circuit shown in Fig. Q7-II, assuming diodes and op-amp are ideal, the values of lower and upper threshold points of voltage transfer characteristics, respectively, are
 (A) $-8\text{ V}, +5\text{ V}$ (B) $-5\text{ V}, +5\text{ V}$ (C) $-5\text{ V}, +8\text{ V}$ (D) $-8\text{ V}, +8\text{ V}$

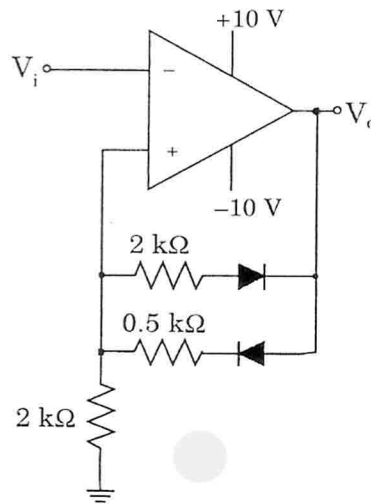


Fig. Q7-II

8. Which one of the following Boolean expressions is **NOT** correct?
 (A) $\overline{x + y} = \overline{x} \overline{y}$ (B) $\overline{\overline{x + y}} = \overline{\overline{x} \overline{y}}$
 (C) $\overline{\overline{\overline{x} \overline{y}}} = \overline{\overline{x} + \overline{y}}$ (D) $\overline{\overline{\overline{x + y}}} = \overline{\overline{x} \overline{y}}$
9. A Boolean function can be expressed
 (A) as sum of maxterms or product of minterms
 (B) as product of maxterms or sum of minterms
 (C) partly as product of maxterms and partly as sum of minterms
 (D) partly as sum of maxterms and partly as product of minterms
10. Among the following logic families, the one having the lowest power dissipation and highest noise margin is
 (A) Schottky TTL (B) TTL
 (C) ECL (D) CMOS
11. The characteristic equation of a level triggered T flip-flop, with T as input and Q as output is
 (A) $Q(n + 1) = T \overline{Q} + \overline{T} Q$ (B) $Q(n + 1) = \overline{T}$
 (C) $Q(n + 1) = Q$ (D) $Q(n + 1) = TQ + \overline{T} \overline{Q}$

12. The Nyquist plot of $G(j\omega)H(j\omega)$ of a closed loop control system encloses the point $(-1, j0)$ in GH -plane. The gain margin of the system in dB, is
- (A) greater than zero (B) less than zero
(C) zero (D) infinite
13. For the LTI system described by $2 \frac{d^2 y(t)}{dt^2} + 3 \frac{dy(t)}{dt} + 4y(t) = r(t) + 2r(t-1)$ and having zero initial conditions, the transfer function $\frac{Y(s)}{R(s)}$ is
- (A) $\frac{1+2e^s}{2s^2+3s+4}$ (B) $\frac{2s^2+3s+4}{1+2e^s}$ (C) $\frac{1+2e^{-s}}{2s^2+3s+4}$ (D) $\frac{2s^2+3s+4}{1+2e^{-s}}$
14. An amplitude modulated double sideband suppressed carrier signal is given by $[1 + a_m \cos 2\pi f_a t] \cos 2\pi f_m t \cos 2\pi f_c t$, where f_c is the frequency of the carrier signal. The modulating signal is
- (A) $a_m \cos 2\pi f_a t$ (B) $a_m \cos 2\pi f_a t \cos 2\pi f_m t$
(C) $[1 + a_m \cos 2\pi f_a t] \cos 2\pi f_m t$ (D) $1 + a_m \cos 2\pi f_a t$
15. Which one of the following expressions represents a frequency modulated signal?
- (A) $A_c \cos 2\pi [f_c t + m(t)]$ (B) $\left[1 + \int_0^t m(\tau) d\tau\right] \cos 2\pi f_c t$
(C) $A_c m(t) \cos 2\pi f_c t$ (D) $A_c \cos 2\pi \left[f_c t + \int_0^t m(\tau) d\tau\right]$
16. A binary pulse communication system transmits a normalized pulse $p(t)$ over bit duration T_b . If the pulse $p(t)$ has Fourier transform $P(f)$, the condition for zero intersymbol interference in the absence of noise is
- (A) $\sum_{n=-\infty}^{\infty} P\left(f - \frac{n}{T_b}\right) = 1$ (B) $\sum_{n=-\infty}^{\infty} P\left(f - \frac{n}{T_b}\right) = T_b$
(C) $\sum_{n=-\infty}^{\infty} P\left(f - \frac{n}{T_b}\right) = \frac{1}{T_b}$ (D) $\sum_{n=0}^{\infty} P\left(f - \frac{n}{T_b}\right) = T_b$
17. The magnitude response of an ideal equalizer for rectifying a distortion characterized by $T \operatorname{sinc}(fT) e^{-j\pi fT}$ is
- (A) $|T \operatorname{sinc}(fT)|$ (B) $T / \operatorname{sinc}(fT)$
(C) $\pi f / \sin(\pi fT)$ (D) $\sin(\pi fT) / T$

18. If the minimum sampling frequency required to reconstruct a band limited analog signal from its samples is 8 kHz, the maximum frequency present in the signal is
(A) 16 kHz (B) ≥ 16 kHz (C) 4 kHz (D) > 4 kHz
19. Which one of the following statements is **NOT** true?
(A) The two cavity klystron tube is used as an amplifier.
(B) A reflex klystron uses only a single cavity and operates as an oscillator.
(C) In klystron tubes, the bunching of electrons is caused by velocity modulation.
(D) Klystrons belong to the category of crossed-field tubes.
20. In a microprocessor, the program counter points to the address location from where the
(A) current byte is to be fetched
(B) next byte is to be fetched
(C) next byte is to be stored
(D) current byte is to be added

Question number 21-50 carry 2 marks each

21. A microwave link operates under free space conditions at a frequency of 1 GHz and uses identical antennas at the transmitter and the receiver ends. The transmitter and the receiver are separated by a distance of 30 km. If -30 dBm power is to be received when the transmitted power is 1 W, the antenna gain should be
(A) 100π (B) 200π (C) 300π (D) 400π
22. In connection with memory mapped I/O which one of the following statements is **NOT** true?
(A) The processor treats an interface register as a part of the memory system.
(B) It reduces the memory space available.
(C) The processor cannot manipulate I/O data residing in interface registers with the same instructions that are used to manipulate memory location.
(D) Arithmetic or logical operation can be directly performed with I/O data.

23. After execution of the following C program, the value of the sum printed is

```
main ()
{
    int i, n;
    float x, dx, sum;
    sum = 0;
    x = 2;
    for (i = 1; i <= 100; i++)
    {
        dx = x *(i - 1);
        sum = sum + dx;
        x = 2 * x;
        if (sum > x)
            break;
    }
    printf("%f", sum);
    end;
}
```

- (A) 68 (B) 20 (C) 16 (D) 4
24. If selection sort takes 3 ms to run an array of 200 elements, for a similar array of 4000 elements the selection sort is expected to take
- (A) 1.2 s (B) 600 ms
(C) 300 ms (D) 60 ms
25. In a stack based processor organization, postfix notation is used for evaluating arithmetic expressions. The postfix expression $ABC*/D-EF/+$ for $A = 6$, $B = 2$, $C = 3$, $D = 3$, $E = 4$ and $F = 2$ evaluates to
- (A) 0 (B) 1 (C) 2 (D) 3
26. In a 8085 microprocessor system, the active low chip select (\overline{CS}) signal is generated by passing address lines A_{15}, \dots, A_{10} through a 6 inputs NAND gate. For selecting the address range $CC00$ to $CFFF$, the inputs to the NAND gate are
- (A) $A_{10}, A_{11}, \overline{A}_{12}, \overline{A}_{13}, A_{14}, A_{15}$ (B) $\overline{A}_{10}, \overline{A}_{11}, A_{12}, A_{13}, \overline{A}_{14}, \overline{A}_{15}$
(C) $A_{10}, A_{11}, \overline{A}_{12}, A_{13}, A_{14}, A_{15}$ (D) $A_{10}, A_{11}, A_{12}, A_{13}, A_{14}, A_{15}$

27. In the context of 8085 microprocessor, the correct matching combination between Column A and Column B is

<u>Column A</u>	<u>Column B</u>
P. ALE	1. Rotate accumulator left
Q. PSW	2. Compare with accumulator
R. CMA	3. Program status word
S. RLC	4. Address latch enable
	5. Program stack word
	6. Arithmetic logic enabled
	7. Complement accumulator
	8. Rotate accumulator left through carry

(A) P-6, Q-5, R-2, S-8

(B) P-4, Q-3, R-2, S-8

(C) P-4, Q-3, R-7, S-1

(D) P-6, Q-5, R-7, S-1

28. The content of the memory location 2070 H after the execution of the following 8085 program is

```
LXIB 2070H
MVI A, 8FH
MVI C, 68H
SUB C
ANI 0FH
STAX B
HLT
```

(A) 04 H

(B) 07 H

(C) 09 H

(D) 0F H

29. A 8085 microprocessor program uses all available Jump instructions, each only once. For this program, the total memory (in Bytes) occupied by the Jump instructions is

(A) 30

(B) 27

(C) 24

(D) 18

30. The circuit shown in Fig. Q30-II oscillates at an angular frequency of ω at a particular R. The values of ω (in rad/sec) and R (in $k\Omega$), respectively, are
- (A) 10^5 and 20 (B) 2×10^5 and 20
 (C) 2×10^5 and 10 (D) 10^5 and 10

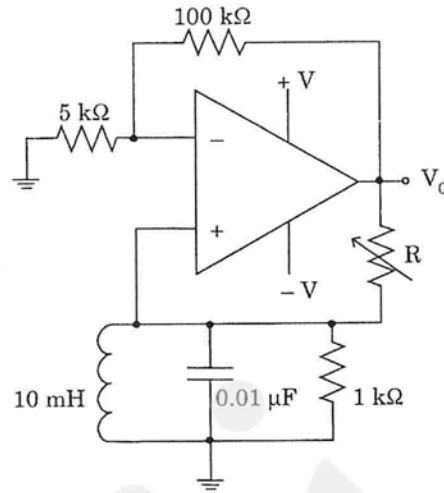


Fig. Q30-II

31. A combinational circuit accepts a 2 bit binary number and outputs its square in binary. To design this circuit using a ROM, the minimum size of ROM required is
- (A) 2×2 (B) 4×2 (C) 4×4 (D) 8×4
32. In the op-amp circuit shown in Fig. Q32-II, assume the diode current follows the equation $I = I_s e^{V/V_T}$. If $V_0 = V_{0_1}$ for $V_i = 2$ V and $V_0 = V_{0_2}$ for $V_i = 4$ V, the relation between V_{0_1} and V_{0_2} is
- (A) $V_{0_2} = V_{0_1} \sqrt{2}$ (B) $V_{0_2} = V_{0_1} e^2$
 (C) $V_{0_2} = V_{0_1} \ln 2$ (D) $V_{0_2} = V_{0_1} + V_T \ln 2$

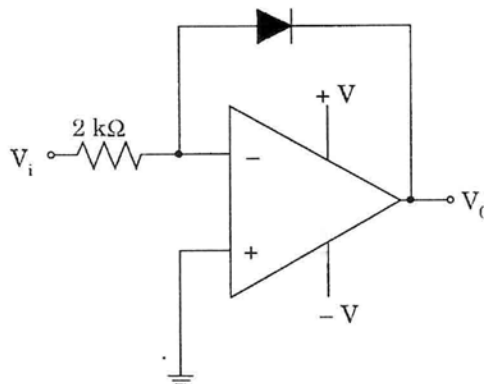


Fig. Q32-II

33. In the 2-stage amplifier circuit shown in Fig. Q33-II, if the transconductances of transistor Q_1 and transistor Q_2 are g_{m1} and g_{m2} , respectively, the overall transconductance $g_{mo} = i_o/v_i$ of the amplifier is

- (A) $g_{mo} \approx g_{m1}$ (B) $g_{mo} \approx g_{m2}$
 (C) $g_{mo} = g_{m1} + g_{m2}$ (D) $g_{mo} = g_{m1} - g_{m2}$

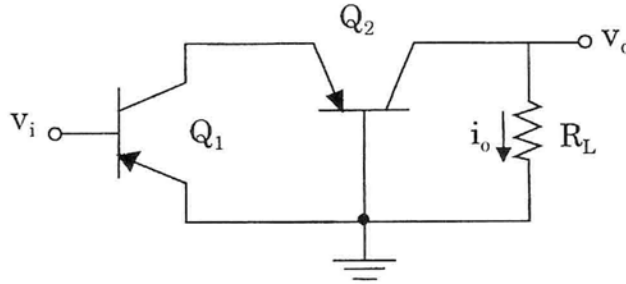


Fig. Q33-II

34. For the system with $G(s)H(s) = \frac{K(s + 4)}{s(s + 1)}$, the breakaway points in the root-loci plot approximately are

- (A) $-7.46, -1$ (B) $-0.54, -1$
 (C) $-7.46, -0.54$ (D) $7.46, 0.54$

35. For the circuit shown in Fig. Q35-II, the p-channel JFET transistor parameters are $I_{DSS} = 6 \text{ mA}$ and $V_p = 4 \text{ V}$. The source-to-drain voltage V_{SD} and the region of operation of the transistor, respectively, are

- (A) 2.09 V and active region (B) 2.09 V and saturation region
 (C) 2.47 V and active region (D) 2.47 V and saturation region

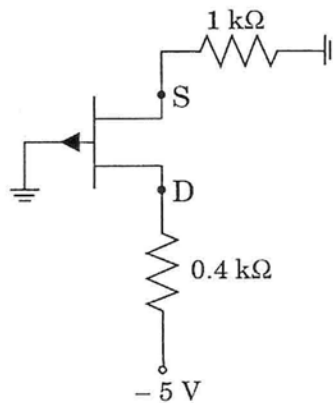


Fig. Q35-II

36. For the truth table given in Fig. Q36-II, the minimized Boolean expression is

- (A) $p = xyz + \bar{x}y\bar{z} + x\bar{y}\bar{z} + \bar{x}\bar{y}z$
- (B) $p = \overline{x \oplus y \oplus z}$
- (C) $p = x \overline{(y \oplus z)} + \bar{x}(y \oplus z)$
- (D) $p = x \oplus \bar{y} \oplus z$

Input			Output
x	y	z	p
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Fig. Q36-II

37. For a linear system having the characteristic equation $s^4 + s^3 + 2s^2 + 2s + 3 = 0$, the number of roots in the right-half of s-plane is

- (A) 4
- (B) 3
- (C) 2
- (D) 1

38. The Boolean function $F(A, B, C) = \prod(0, 2, 4, 7)$ is to be implemented using a 4×1 multiplexer shown in Fig. Q38-II. Which one of the following choices of inputs to multiplexer will realize the Boolean function?

- (A) $(I_0, I_1, I_2, I_3, s_1, s_0) = (1, 0, \bar{A}, A, C, B)$
- (B) $(I_0, I_1, I_2, I_3, s_1, s_0) = (1, 0, \bar{A}, A, B, C)$
- (C) $(I_0, I_1, I_2, I_3, s_1, s_0) = (0, 1, \bar{A}, A, C, B)$
- (D) $(I_0, I_1, I_2, I_3, s_1, s_0) = (0, 1, A, \bar{A}, B, C)$

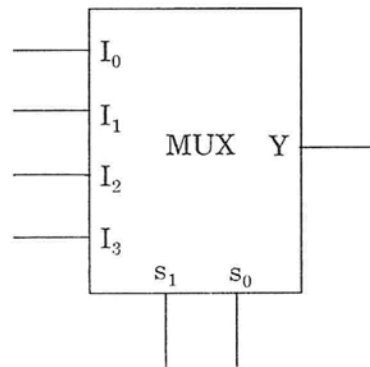


Fig. Q38-II

39. An edge triggered synchronous binary counter is provided with a clock (CLK) and control inputs: active low clear (\overline{CLR}), active high load (L) and active high count (C). The correct matching combination between Column A and Column B is

Column A

Column B

- | | |
|--|----------------------------|
| 1. $(CLK, \overline{CLR}, L, C) = (\uparrow, 1, 1, X)$ | P. No change |
| 2. $(CLK, \overline{CLR}, L, C) = (\uparrow, 1, 0, 1)$ | Q. Load inputs |
| 3. $(CLK, \overline{CLR}, L, C) = (X, 0, X, X)$ | R. Count next binary state |
| 4. $(CLK, \overline{CLR}, L, C) = (X, 1, 0, 0)$ | S. Clear outputs |

where $X = \text{don't care}$.

- | | |
|------------------------|------------------------|
| (A) 1-Q, 2-R, 3-S, 4-P | (B) 1-P, 2-Q, 3-R, 4-S |
| (C) 1-Q, 2-R, 3-P, 4-S | (D) 1-P, 2-Q, 3-S, 4-R |

40. A 5-bit serial adder is implemented using two 5-bit shift registers, a full adder and a D flip-flop. The two binary words to be added are 11011 and 11011. The sum of the two numbers is stored in one of the shift registers and the carry in the D flip-flop. Assuming that the D flip-flop is set initially, the content of the sum shift register and the D flip-flop, respectively, are

- | | |
|-----------------|-----------------|
| (A) 10111 and 0 | (B) 11011 and 1 |
| (C) 11101 and 0 | (D) 10111 and 1 |

41. For the flow diagram shown in Fig. Q41-II, the transfer function $\frac{Y(s)}{R(s)}$ is

- | | | | |
|-------------------------------|------------------------------|------------------------------|--------------------------------|
| (A) $\frac{3}{s^2 + 6s + 11}$ | (B) $\frac{3}{s^2 + 5s + 4}$ | (C) $\frac{3}{s^2 + 6s + 8}$ | (D) $\frac{-3}{s^2 + 6s + 11}$ |
|-------------------------------|------------------------------|------------------------------|--------------------------------|

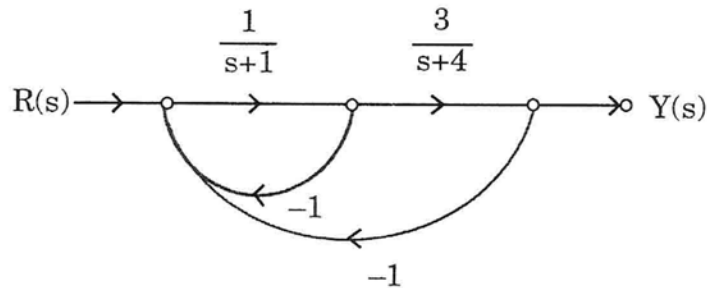


Fig. Q41-II

42. The compensated system shown in Fig. Q42-II, has a phase margin of 60° at the crossover frequency of 1 rad/sec. The value of K is
 (A) 0.366 (B) 0.732 (C) 1.366 (D) 2.732

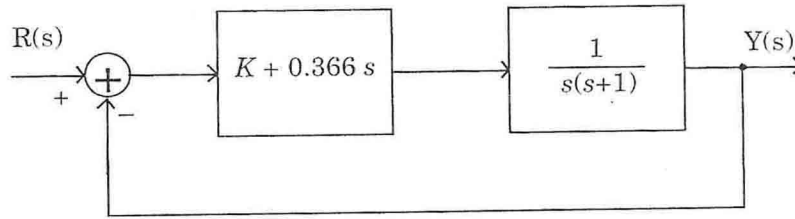


Fig. Q42-II

43. A time division multiplex system samples 96 voice channels at a rate of 8 kHz and encodes into 8 bits per sample. If one synchronization bit per frame is added, the transmitted data rate (Mbps) is
 (A) 6.208 (B) 6.152 (C) 6.144 (D) 0.768
44. A geostationary satellite located at 36,000 km from the surface of the earth. The uplink free space loss is 1.583 dB higher than the downlink free space loss. If the downlink frequency is 10 GHz, the uplink free space loss (in dB) is
 (A) 10.25 (B) 20.5 (C) 102.5 (D) 205
45. In a uniform quantizer, the quantization noise is
 (A) independent of the number of levels of the quantizer
 (B) proportional to square of the peak-to-peak voltage range of the quantizer
 (C) independent of the peak-to-peak voltage range of the quantizer
 (D) proportional to square of the number of levels of the quantizer
46. In a digital communication system, the transmitted pulse is shown in Fig. Q46-II. The matched filter output at the sampling instant (i.e., $t = 1$ sec) is
 (A) $\frac{\sqrt{3}}{2}$ (B) 1 (C) $\frac{1}{2}$ (D) $\frac{1}{6}$

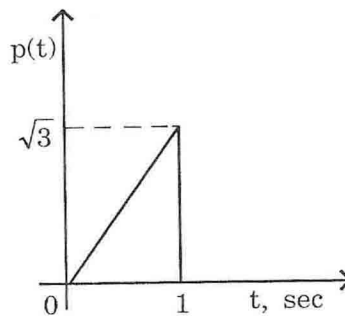


Fig. Q46-II

47. An optical link uses a fiber having a power loss of 1 dB/km. A typical photo detector has responsivity 0.5 A/W. If the link is 3 km long and the detector is required to produce a current of 25 μ A, the required transmitted power is
 (A) 0 dBm (B) -10 dBm (C) -30 dBm (D) -50 dBm
48. For the directional coupler shown in Fig. Q48-II, the coupling is 20 dB and the directivity is 30 dB. If 10 W power is incident in port-1, power out of port-4 is
 (A) 0.1 mW (B) 1 mW (C) 0.01 W (D) 0.1 W

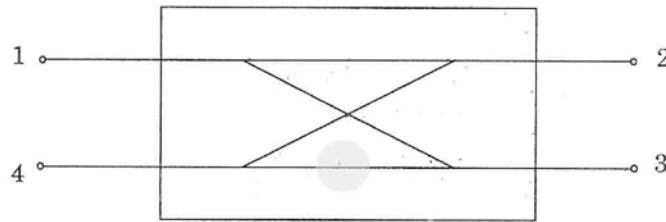


Fig. Q48-II

49. In a microwave measurement with slotted rectangular waveguides, the distance between successive minima is found to be 2.5 cm. If the measurement has been carried out at a frequency of 10 GHz and the guide operates in TE_{10} mode, the cut off frequency $f_{c_{10}}$ for the guide is
 (A) 6 GHz (B) 8 GHz (C) 10 GHz (D) 12 GHz
50. An antenna having a directivity of 2 at a frequency of 300 MHz will have a maximum effective aperture of
 (A) $\frac{1}{8\pi}$ m² (B) $\frac{1}{4\pi}$ m²
 (C) $\frac{1}{2\pi}$ m² (D) $\frac{1}{\pi}$ m²

Section – III

All questions carry 1 mark each

1. Chandrayaan-I, India's first mission to the moon, has 11 scientific instruments that are being released on the surface of the moon. These instruments are together known as
(A) Moon Impact Probes (B) Terrain Mapping Cameras
(C) Scientific Payloads (D) Spectrometers
2. The World Wide Web was invented by
(A) Tim Berners-Lee (B) Narayanmurthy
(C) Sabeer Bhatia (D) Charles Babbage
3. How many diagonals does a quadrilateral have?
(A) one (B) two (C) four (D) eight
4. ISO 14000 standards deal with
(A) quality management (B) production management
(C) human resource management (D) environmental management
5. Which Indian politician's autobiography is titled *The Story of My Life*?
(A) Morarji Desai (B) Mahatma Gandhi
(C) Lal Krishna Advani (D) Atal Behari Vajpayee
6. The phrase 'through thick and thin' means
(A) big and small (B) thin and fat
(C) large object (D) under all conditions
7. Picturesque means
(A) photogenic (B) simple (C) stimulating (D) ugly
8. Diligent means
(A) intelligent (B) energetic (C) modest (D) industrious
9. The opposite of miserly is
(A) spendthrift (B) generous (C) liberal (D) charitable
10. The opposite of ingratitude is
(A) sympathy (B) reward
(C) thankfulness (D) stimulation

11. The appropriate missing word in the blank space in the sentence “I prefer coffee _____ tea.” is
(A) than (B) over (C) for (D) to
12. The appropriate missing word in the blank space in the sentence “Many relatives attended _____ him during his illness.”
(A) of (B) on (C) for (D) with
13. The article required before the word “one-eyed” in the sentence “There was _____ one-eyed beggar by the multiplex.” is
(A) the (B) a (C) an (D) nil
14. The article required before the word University in the sentence “She met Professor Shah at _____ University.” is
(A) a (B) an (C) the (D) nil
15. Which one is the correct sentence amongst the following sentences?
(A) Mr. Gupta, accompanied by his friends, were assembled on the lawns.
(B) Mr. Gupta, accompanied by his friends, are assembled on the lawns.
(C) Mr. Gupta, accompanied by his friends, assembled on the lawns.
(D) Mr. Gupta, accompanied by his friends, have assembled on the lawns.
16. Who was the first woman to be elected as the President of the Indian National Congress?
(A) Sarojini Naidu (B) Sonia Gandhi
(C) Indira Gandhi (D) Annie Besant
17. Which political leader delivered the famous ‘I have a dream’ speech?
(A) Jawaharlal Nehru (B) Winston Churchill
(C) Martin Luther King (D) Rabindranath Tagore
18. Who established the organization ‘Khudai Khidmatgar’?
(A) Hyder Ali (B) Gopal Krishna Gokhale
(C) Maulana Abul Kalam Azad (D) Khan Abdul Ghaffar Khan
19. Analgesics are drugs used to prevent or relieve
(A) aches and pain (B) fever and high body temperature
(C) hormone deficiency (D) stress and anxiety
20. The abbreviation CD stands for
(A) Circular Disc (B) Computer Device
(C) Compact Disc (D) Code-Demodulator