

2005-PUNJAB UNIVERSITY
B.TECH IV SEMESTER DEGREE EXAMINATION
ANALOG ELECTRONICS
(ELECTRONICS AND COMMUNICATION ENGINEERING)

TIME-3HOUR
MARKS-100

PART A [10*2=20 MARKS]

1. Draw the high frequency equivalent circuit of CE transition.
2. Why does RC coupling give constant gain over mid-frequency range?
3. Explain the difference between a voltage and power amplifier.
4. What is crossover distortion? Explain in brief.
5. Show that maximum collector efficiency of class a transformer coupled power amplifier is 50%.
6. Why is negative feedback employed in high gain amplifiers?
7. What are practical applications of emitter follower?
8. Why is crystal oscillator used in radio transmitter?
9. Why is -ve feedback provided in Wein-bridge oscillator?
10. How does zener diode maintain constant voltage across load in the breakdown region?

PART B [10*8=80 MARKS]

2. Explain hybrid pi CE transistor model in detail.
3. Explain the push-pull amplifier circuit in detail with a neat diagram.
4. The gain and distortion of an amplifier are 150 and 5% respectively without feedback. If the stage has 10% of its output voltage applied as negative feedback, find the distortion of the amplifier with feedback.
5. A transformer coupling is used in the final stage of a multistage amplifier. If the output impedance of transistor is 1 k Ω , find the turn ratio of the transformer so that maximum power is transferred to the load.
6. Explain a current shunt feedback circuit and perform a suitable analysis.
7. What do you understand by class A, Class B and class C power amplifier? Define and explain the following terms as applied to power amplifiers:
 - (a) Collector efficiency
 - (b) Distortion
 - (c) Power dissipation capability
- 8 (a) A zener regulator has $V_z=15V$. The input voltage may vary from 22 V to 40 V and load current from 20 to 100 mA. To hold load voltage constant under all conditions, what should be the value of series resistance?
 - (b) Explain the working of a Colpitts oscillator with a neat diagram.

9. (a) Derive an expression for the gain of negative voltage feedback amplifier.

(b) A multistage amplifier consists of three stages. The voltage gain of stages are 60, 100 and 160 Calculate the overall

Educationobserver.com