

2008-PUNJAB TECHNICAL UNIVERSITY
B.TECH I SEMESTER REGULAR EXAMINATION
SWITCHING THEORY AND LOGIC DESIGN
(ELECTRICAL AND ELECTRONICS ENGINEERING)

TIME-3HOUR
MARKS-80

ANSWER ANY FIVE QUESTIONS ALL QUESTIONS CARRY EQUAL MARKS

MARKS [16*5=80]

1. (a) Perform the following using BCD arithmetic.

- i. $712910 + 771110$
- ii. $812410 + 812710$

(b) Convert the following.

- i. $AB_{16} = ()_{10}$
- ii. $12348 = ()_{10}$
- iii. $101100112 = ()_{10}$
- iv. $77210 = ()_{16}$

2. (a) Convert the following expressions in to sum of products and product of sums

- i. $(AB+C)(B+C'D)$
- ii. $x' + x(x+y)(y+z')$

(b) Obtain the Dual of the following Boolean expressions.

- i. $(AB'+AC')(BC+BC')(ABC)$
- ii. $AB'C+A'BC+ABC$
- iii. $(ABC)'(A+B+C)'$
- iv. $A+B'C(A+B+C)$

3. (a) What is meant by a prime implicant, an essential prime implicant, and a secondary essential prime implicant?

(b) Minimize following function using Map method $F(A, B, C, D) = \sum m(2, 3, 8, 12, 13) + d(10, 14)$

4. (a) Implement the following multiple output combinational logic using a 4 line to 16 line Decoder.

$$Y1 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD$$
$$Y2 = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + A\bar{B}C\bar{D} + ABC\bar{D}$$
$$Y3 = \bar{A}BCD + ABC\bar{D} + ABCD.$$

(b) Explain the terms Multiplexing and Demultiplexing.

5. (a) Specify the size of a ROM (number of words and numbers bits per word) that will accommodate the truth table of a BCD to seven segment decoder with an enable input.

(b) Write a brief note on programmable logic devices.

6. (a) Find a modulo-6 gray code using k-Map & design the corresponding counter.

(b) Compare synchronous & Asynchronous.

7. A clocked sequential circuit is provided with a single input x and single output Z . Whenever the input produce a string of pulses 1 1 1 or 0 0 0 and at the end of the sequence it produce an output $Z = 1$ and overlapping is also allowed.

(a) Obtain State - Diagram.

(b) Also obtain state - Table.

(c) Find equivalence classes using partition method & design the circuit using D flip-flops.

8. For the ASM chart

(a) Draw the state diagram.

(b) Design the control unit using D flip-flops and a decoder.

Educationobserver.com