

NOTE: SECTION A IS COMPULSORY. ATTEMPT ANY FOUR QUESTIONS FROM SECTION B AND TWO FROM SECTION C

SECTION A MARKS 2 EACH

- 1 (a) What four bit number is equal to its 2's complement ?
- (b) Discuss the significance of Boolean Logic.
- (c) What are the low and high levels at the input and output sides of a TTL logic?
- (d) Explain the term tri-state.
- (e) Discuss the racing condition. How is it avoided?
- (f) What are the functions of the counter?
- (g) Justify the need of bus technology.
- (h) Compare the level triggering and edge triggering.
- (i) What is the difference between accuracy and resolution for A-D convertors?
- (j) List the merits and applications of CAD tools.

SECTION B MARKS 5 EACH

2. Minimise the following logic function and realize using NAND gates:
 $f(A,B,C,D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$
3. Compare the features of various logic families.
4. Describe the salient features of VLSI design.
5. Explain with an example the parallel comparator type A-D convertor.
6. Compare the features of ROM, RAM, EEPROM, PLA and PAL..

SECTION C MARKS 10 EACH

7. Design a mod Counter. Completely show the timing waveforms indicating counting and division of frequency.
8. Write short notes on any three of the following:
 - (a) Transmission line effects.
 - (b) programmable logic devices.
 - (c) Astable multivibrator
 - (d) Computer aids in synthesis.
9. A sequential circuit is to have two level inputs x_1 and x_2 and one clock. An output pulse Z is to be coincident with a clock pulse occurring with $x_1x_2 = 01$ immediately following two or more consecutive clock pulses with $x_1x_2 = 10$ and $x_1x_2 = 00$. $x_1x_2 = 11$ can never occur. draw the stable state diagram and design the circuit using minimum number of J-K flip-flops.