

2007-COCHIN UNIVERSITY OF SCIENCE AND TECHNOLOGY

B.TECH DEGREE EXAMINATION

ELECTRONIC DEVICES & CIRCUITS

(ELECTRICAL AND ELECTRONICS ENGINEERING)

TIME- 3HOUR
MARKS-60

ANSWER ALL QUESTIONS

SECTION A [4*5=20]

1. Explain the dc power supply with block diagram.
2. Explain the principle & operation of Photodiode, PIN diode& Phototransistor.
3. Explain the pulse characteristics.
4. Explain the positive& negative clippers with neat ckt diagram.

SECTION B [4*10=40]

5. a) Explain voltage multipliers.
b) An ac supply of 230 v is applied to a half wave rectifier ckt through a T/F of turns ratio 10:1 .Determine
 1. I_m, I_{dc} & I_{rms}
 2. dc power o/p.
 3. ac power o/p.
 4. efficiency of rectification.
 5. dc o/p voltage.
 6. Peak inverse voltage
Assume that the crystal diode has a forward resistance of 20 ohm& the load resistance is 1 Kilo ohm
6. a) Explain the working of T/F as a switch.
b) A bridge rectifier is supplying a load of 200mA at 30V. It uses a pi-section filter with a choke of 0.5 H & 2 capacitors each of 80 microF. Assume the supply frequency of 50 Hz. Find
 - (i) the i/p rms voltage of the secondary of the T/F.
 - (ii) the percentage ripple in o/p.
7. a) Explain the Breeder resistor& voltage regulation.
b) Explain astable, monostable& bistable multivibrators using BJT's.
8. a) Explain zener& avalanche diode.
b) A full wave rectifier has a peak o/p voltage of 25 V at 50Hz.& feeds a resistive load of 1Kohm. The filter used is shunt capacitor one with $C=20$ microfarad. Determine (i) dc load current(ii) dc o/p voltage(iii) ripple voltage(iv) ripple factor.