

FIRST YEAR HIGHER SECONDARY EXAMINATION MARCH 2018

SUBJECT: ELECTRONICS SYSTEMS

CODE. NO: 124

| Qn No | Sub Qns | Answer Key/Value Points  | Score                   | Total  |
|-------|---------|--|-------------------------|--------|
| 1.    |         | Doping   | 1                       |        |
| 2     |         | 7815   | 1                       |        |
| 3     |         | Voltage divider biasing  | 1                       | 5      |
| 4     |         | NAND   | 1                       |        |
| 5     |         | CRO  | 1                       |        |
| 6     |         | Any two advantages   | 2                       | 2      |
| 7     |         | Energy band diagram of Si ( $E_g = 1.12\text{eV}$ ) and Ge ( $0.72\text{eV}$ ) | 2                       | 2      |
| 8     |         | Circuit diagram of voltage divider biasing                                     | 2                       | 2      |
| 9.    |         | Short notes on TDM   | 2                       | 2      |
| 10    |         | Circuit diagram of Common Source FET amplifier                                 | 2                       | 2      |
| 11    |         | Avalanche break down, Zener break down<br>Difference                           | $\frac{1}{2}$ each<br>1 | 1<br>1 |
| 12    |         | Symbol of phototransistor, thermistor  | 1 each                  | 2      |
| 13    |         | SCR - Speed control<br>Varactor diode - Frequency selection                    | $4 \times \frac{1}{2}$  | 2      |

| Qn No | Sub Qns | Answer Key/Value Points   | Score          | Total |
|-------|---------|---|----------------|-------|
|       |         | LED - Seven segment display<br>Photodiode - burglar alarm   |                |       |
| 14    |         | $V_{max} = \sqrt{2} \times V_{rms} = \sqrt{2} \times 6 = 8.49V$<br>$Frequency = \frac{1}{T} = \frac{1}{10msec} = 100Hz$           | 1 1/2<br>1 1/2 | 3     |
| 15    |         | Any three points  | 3              | 3     |
| 16    |         | Sketch the 3 waveforms  | 3 x 1          | 3     |
| 17    |         | Circuit diagram of Half wave rectifier with capacitor filter<br>Working   | 1 1/2<br>1 1/2 | 3     |
| 18    | a       | Truth Table of EX-OR  | 1              |       |
|       | b       | Truth Table of Half adder<br>Circuit diagram of Half adder  | 1<br>1         | 3     |
| 19    |         | $R_1 = 100\Omega \pm 5\%$ , $R_2 = 270\Omega \pm 5\%$ , $R_3 = 3.3K\Omega \pm 5\%$<br>$R_{eff} = 3373\Omega [(R_1    R_2) + R_3]$ | 1<br>3         | 4     |
| 20    | a)      | Forward characteristics<br>mark knee voltage  | 1<br>1         | 4     |
|       | b)      | Dynamic resistance  | 2              |       |
| 21    |         | K mapping<br>Grouping<br>Equation   | 2<br>1<br>1    | 4     |

| Qn No | Sub Qns | Answer Key/Value Points                                 | Score  | Total |
|-------|---------|---|--------|-------|
| 22    |         | Circuit diagram<br>Explanation                          | 2<br>2 | 4     |
| 23    |         | Symbol<br>Structure                                     | 1<br>3 | 4     |
| 24    | a)      | Potential difference                                    | 1      |       |
|       | b)      | $R_{eff} = 7.4 \Omega$                                  | 1      |       |
|       |         | $I_{TOT} = 1.89 A$                                      | 1      | 5     |
|       |         | $I_1 = 1.13 A$  | 1      |       |
|       |         | $I_2 = 0.76 A$  | 1      |       |
| 25    |         | Comparison of CE, CB & CC<br>(Compare any 4 parameters) | 5      | 5     |
| 26    | a)      | Working principle of galvanometer                       | 2      |       |
|       | b)      | Conversion to ammeter                                   | 1/2    | 5     |
|       |         | Conversion to voltmeter                                 | 1/2    |       |
| 27    |         | Block diagram   | 3      |       |
|       |         | waveforms   | 2      | 5     |

Ueena. U  
20

Public  
AMBIL.K.

[Signature]  
Nathana. M.A.