



IES MASTER

Institute for Engineers (IES/GATE/PSUs)

**GATE
2019**

**ELECTRICAL
ENGINEERING**

Detailed Solution

EXAM DATE: 09-02-2019

AFTERNOON SESSION (02:30 PM-05:30 PM)

Office Address

DELHI: F-126, Katwaria Sarai, New Delhi - 110 016

Ph: 011-41013406, **Mobile:** 8130909220, 9711853908

NOIDA: B-23 A, 5th Floor, Gaurav Deep Heights, Near Fortis Hospital
Sector 62, Noida- 201305 **Ph:** 0120 415 1100

Web: www.iesmaster.org | E-mail: info@iesmaster.org



SECTION: GENERAL APTITUDE

1. The missing number in the given sequence 343, 1331, _____, 4913 is
 (a) 2744 (b) 2197
 (c) 3375 (d) 4096

Ans. (b)

343, 1331, _____, 4913
 $7^3, 11^3, \underline{13^3}, 17^3$
 $\Rightarrow 13^3 = 2197$

here, the given series is the cube of prime numbers.

2. The passengers were angry _____ the airline staff about the delay.
 (a) with (b) on
 (c) about (d) towards

Ans. (a)

3. I am not sure if the bus that has been booked will be able to _____ all the students.
 (a) fill (b) accommodate
 (c) deteriorate (d) sit

Ans. (b)

4. Newspapers are a constant source of delight and recreation for me. The _____ trouble is that I read _____ many of them.
 (a) even, too (b) only, quite
 (c) even, quite (d) only, too

Ans. (d)

5. It takes two hours for a person X to mow the lawn. Y can mow the same lawn in four hours. How long (in minutes) will it take X and Y, if they work together to mow the lawn?
 (a) 120 (b) 60
 (c) 90 (d) 80

Ans. (d)

$$\text{Rate of work of X persons} = \frac{\text{work}}{120}$$

$$\text{Rate of work of Y persons} = \frac{\text{work}}{240}$$

$$\Rightarrow \left(\frac{\text{work}}{120} + \frac{\text{work}}{240} \right) t = \text{work}$$

$$\Rightarrow t = 80 \text{ minute}$$

6. Given two sets $X = \{1, 2, 3\}$ and $Y = \{2, 3, 4\}$, we construct a set Z of all possible fractions where the numerators belong to set X and the denominators belong to set Y. The product of elements having minimum and maximum values in the set Z is _____.
 (a) 1/8 (b) 1/6
 (c) 3/8 (d) 1/12

Ans. (c)

$$x = \{1, 2, 3\} \quad y = \{2, 3, 4\}$$

$$z = \left\{ \frac{\text{Numerator (from x)}}{\text{denominator (from y)}} \right\}$$

$$z = \left\{ \frac{1}{4} \dots \frac{3}{2} \right\}$$

min max

$$\Rightarrow \frac{1}{4} \times \frac{3}{2} = \frac{3}{8}$$

7. The ratio of the number of boys and girls who participated in an examination is 4.3. The total percentage of candidates who passed the examination is 80 and the percentage of girls who passed is 90. The percentage of boys who passed is _____.
 (a) 90.00 (b) 55.50
 (c) 72.50 (d) 80.50

Ans. (c)

$$\text{Participated } \frac{\text{Boys}}{\text{Girls}} = \frac{4}{3}$$

$$\text{Pass \%} = 80\%$$

$$\text{Let total students be } x.$$

$$\text{Passed students} = 0.8x$$

$$\text{Boys} = \frac{4}{7}x$$



$$\text{Girls} = \frac{3}{7}x$$

$$\text{Passed girls} = 0.9 \times \frac{3}{7}x$$

$$\text{Let passed boys} = y$$

$$\Rightarrow \frac{0.9 \times \frac{3}{7}x + y}{x} = 0.8$$

$$\Rightarrow y = 0.8x - \frac{2.7}{7}x = \frac{2.9x}{7}$$

$$\% \text{ Boys passed} = \frac{\frac{2.9x}{7}}{\frac{4}{7}x} \times 100 = 72.5\%$$

8. How many integers are there between 100 and 1000 all of whose digits are even ?

- (a) 60 (b) 80
(c) 100 (d) 90

Ans. (c)

No. of integers whole all digits are even

$$\boxed{4} \boxed{4} \boxed{5}$$

$$\Rightarrow 4 \times 5 \times 5 = 100$$

9. An award winning study by a group of researchers suggests that men are as prone to buying on impulse as women but women feel more guilty about shopping.

- (a) Many men and women indulge in buying on impulse
(b) All men and women indulge in buying on impulse
(c) Few men and women indulge in buying on impulse
(d) Some men and women indulge in buying on impulse

Ans. (d)

10. Consider five people -Mita, Ganga, Rekha, Lakshmi and Sana. Ganga is the taller than

both Rekha and Lakshmi. Lakshmi is taller than Sana. Mita is taller than Ganga.

1. Lakshmi is taller than Rekha
 2. Rekha is shorter than Mita
 3. Rekha is taller than Sana
 4. Sana is shorter than Ganga
- (a) 3 only (b) 1 and 3
(c) 1 only (d) 2 and 4

Ans. (d)

SECTION: ELECTRICAL ENGINEERING

1. The output response of a system is denoted as $y(t)$, and its Laplace transform is given by

$$Y(s) = \frac{10}{s(s^2 + s + 100\sqrt{2})}$$

The steady state value of $y(t)$ is

- (a) $\frac{1}{10\sqrt{2}}$ (b) $10\sqrt{2}$
(c) $100\sqrt{2}$ (d) $\frac{1}{100\sqrt{2}}$

Ans. (a)

Sol: Given transfer function

$$y(s) = \frac{10}{s(s^2 + s + 100\sqrt{2})}$$

The steady-state value of $y(t) = \lim_{t \rightarrow \infty} y(t)$

According to final value theorem.

$$\lim_{t \rightarrow \infty} y(t) = \lim_{s \rightarrow 0} sY(s)$$

$$= \lim_{s \rightarrow 0} s \left[\frac{10}{s(s^2 + s + 100\sqrt{2})} \right]$$

$$= \frac{10}{100\sqrt{2}} = \frac{1}{10\sqrt{2}}$$

$$\left| \lim_{t \rightarrow \infty} y(t) = \frac{1}{10\sqrt{2}} \right|$$

Hence, the steady-state value of $y(t)$ is $\frac{1}{10\sqrt{2}}$.

2. A coaxial cylindrical capacitor shown in Figure (i) has dielectric with relative permittivity $\epsilon_{r1} = 2$. When one-fourth portion of the dielectric is replaced with another dielectric of relative permittivity ϵ_{r2} , as shown in Figure (ii), the capacitance is doubled. The value of ϵ_{r2} is _____.

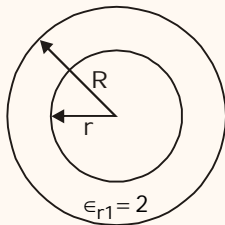


Figure (i)


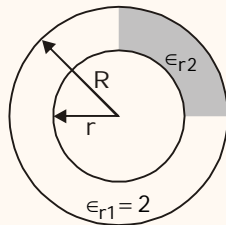


Figure (ii)

Ans. (10)

Sol:

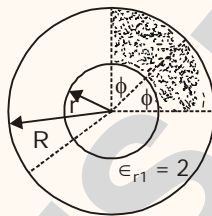

The capacitance for region (ϵ_{r1})

$$C_1 = \frac{2\epsilon_{r1}}{\ln \frac{R}{r}} (\pi - \phi)$$

and the capacitance for region (ϵ_{r2})

$$C_2 = \frac{2\epsilon_{r2}}{\ln \frac{R}{r}} \phi$$

here, $\phi = \frac{90^\circ}{2} = 45^\circ = \frac{\pi}{4}$

$$\Rightarrow C_1 = \frac{2\epsilon_{r1}}{\ln \frac{R}{r}} \times \frac{3\pi}{4}$$

$$\text{and } C_2 = \frac{2\epsilon_{r2}}{\ln \frac{R}{r}} \times \frac{\pi}{4}$$

As, C_1 and C_2 are in parallel

$$C_{eq} = C_1 + C_2 = \frac{2\epsilon_{r1}}{\ln \frac{R}{r}} \times \frac{3\pi}{4} + \frac{2\epsilon_{r2}}{\ln \frac{R}{r}} \times \frac{\pi}{4}$$

$$= \frac{\pi}{2 \ln \frac{R}{r}} (3\epsilon_{r1} + \epsilon_{r2})$$

For figure (i),

$$C = \frac{2\pi\epsilon_{r1}}{\ln \frac{R}{r}}$$

Given that,

$$C_{eq} = 2C$$

$$\Rightarrow \frac{\pi}{2 \ln \frac{R}{r}} (3\epsilon_{r1} + \epsilon_{r2}) = 2 \times \frac{2\pi\epsilon_{r1}}{\ln \frac{R}{r}}$$

$$\Rightarrow 3\epsilon_{r1} + \epsilon_{r2} = 8\epsilon_{r1}$$

$$\Rightarrow \epsilon_{r2} = 5\epsilon_{r1}$$

$$\Rightarrow \epsilon_{r2} = 5 \times 2 = 10$$

$$\Rightarrow \boxed{\epsilon_{r2} = 10}$$

3. A current controlled current source (CCCS) has an input impedance of 10Ω and output impedance of $100k\Omega$. When the CCCS is used in a negative feedback closed loop with a loop gain of 9, the closed loop output impedance is

- (a) 100 kΩ (b) 1000 kΩ
(c) 100 Ω (d) 10 Ω

Ans. (b)


Sol.

Current controlled current source (CCCS)

$$Z_{in} = 10 \Omega$$

$$Z_{o/p} = 100 \text{ k}\Omega$$

$$A\beta = 9$$

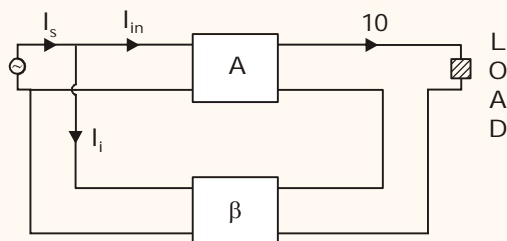

Output is series connection

$$Z_{o/p} = Z_o(1 + A\beta) = 100(1 + 9) \text{ k}\Omega$$

$$Z_{o/p} = 1000 \text{ k}\Omega$$

4. A 5kVA, 50 V/100V, single-phase transformer has a secondary terminal voltage of 95V when loaded. The regulation of the transformer is

- (a) 9% (b) 5%
(c) 1% (d) 4.5%

Ans. (b)

Sol: Voltage regulation = $\frac{V_{2nl} - V_{2fl}}{V_{2fl}} \times 100\%$

Hence, VR = $\frac{100 - 95}{100} \times 100\% = 5\%$

[Note: For transformers, the voltage drop from no load to full load is given with respect to no load voltage as it is fixed by the power supply.

Whereas, for alternators and transmission lines, the reference voltage is taken as full

load voltage.]

5. The output voltage of a single-phase full bridge voltage source inverter is controlled by unipolar PWM with one pulse per half cycle. For the fundamental rms component of output voltage to be 75% of DC voltage, the required pulse width in degrees (round off up to one decimal place) is ____.

Ans. (112.88°)

Sol: Single phase full bridge VSI with PWM

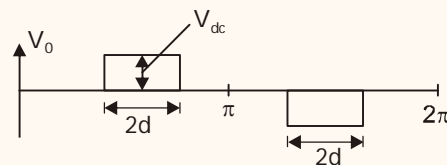


Fig. (a) Output voltage waveform of PWM control (one pulse per half cycle)

$$V_{on} = \sum_{n=6k \pm 1} \frac{4V_{dc}}{n\pi} \sin nd \cdot \sin \frac{n\pi}{2} \cdot \sin n\omega t$$

V_{01rms} = Fundamental rms output voltage

$$V_{01rms} = \frac{2\sqrt{2}}{\pi} V_{dc} \sin d \cdot \sin \frac{\pi}{2}$$

\Rightarrow Given $\frac{V_{01rms}}{V_{dc}} = 0.75$

$\Rightarrow 0.75 = \sin d \left(\frac{2\sqrt{2}}{\pi} \right)$

$\Rightarrow d = \sin^{-1} \left[\frac{0.75}{0.9} \right] = 56.44$

Hence, pulse width $2d = 2 \times 56.44 = 112.88^\circ$

6. The open loop transfer function of a unity feedback system is given by

$$G(s) = \frac{\pi e^{-0.25s}}{s}$$

In $G(s)$ plane, the Nyquist plot of $G(s)$ passes through the negative real axis at the point.

- (a) $(-0.75, j0)$ (b) $(-1.5, j0)$
(c) $(-1.25, j0)$ (d) $(-0.5, j0)$



IES MASTER .org

Institute for Engineers (IES/GATE/PSUs)

Take Your Preparation for
ESE | GATE | PSUs
to the Next Level

ME

CE

EE

ECE

ADMISSIONS OPEN for SESSION 2019-20

Announcing **Regular** and **Weekend Batches**

Batches starting from

DELHI

NOIDA

Regular Batch

Weekend Batch

Weekend Batch

15th Feb (Morning)

16th Feb

16th Feb

18th Feb (Evening)

Register Now

F-126

**Katwaria Sarai
New Delhi-110016**

80100 09955

B-23 A


**Behind Fortis Hospital
Sector 62, Noida- 201305**

0120 415 1100

Sol: Nyquist-plot cut the negative real axis at $\omega = \omega_{pc}$ (Phase cross-over frequency)

$$G(j\omega) = \frac{\pi e^{-0.25(j\omega)}}{j\omega}$$
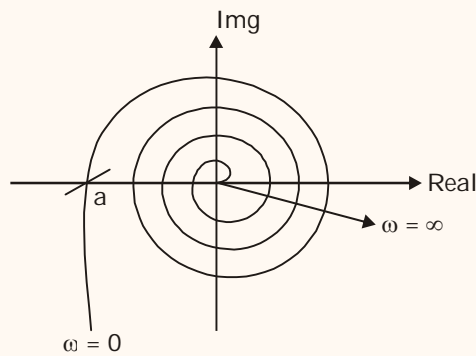
$$\phi = -90^\circ - 0.25\omega \times \frac{180^\circ}{\pi}$$



$$\phi \Big|_{\omega=\omega_{pc}} = -180^\circ = -90^\circ - \frac{\omega}{\pi} (45^\circ)$$

$$\Rightarrow 90^\circ = \omega_{pc} \left(\frac{45^\circ}{\pi} \right)$$

$$\Rightarrow \boxed{\omega_{pc} = 2\pi}$$

Magnitude at cutting point

$$a = |GH|_{\omega=\omega_{pc}}$$

$$a = \frac{\pi}{\omega_{pc}} = \frac{\pi}{2\pi}$$

$$\boxed{a = \frac{1}{2}}$$

Hence Nyquist-plot of $G(s)$ passes through the negative real axis at the point $(-0.5, j0)$

7. The mean square of a zero mean random process is kT/C , where k is Boltzman's constant. T is the absolute temperature, and C is capacitance. The standard deviation of the random.

(a) $\frac{C}{kT}$

(b) $\sqrt{\frac{kT}{C}}$

(c) $\frac{kT}{C}$

(d) $\frac{\sqrt{kT}}{C}$

Ans. (b)

Sol: Given that,

$$\sigma^2 = \frac{kT}{C} \quad (\because \text{Mean} = 0)$$

Hence, standard deviation

$$\sigma = \sqrt{\frac{kT}{C}}$$

8. If $f = 2x^3 + 3y^2 + 4z$, the value of line integral $\int_C \text{grad } f \cdot dr$ evaluated over contour C formed by the segments $(-3, -3, 2) \rightarrow (2, -3, 2) \rightarrow (2, 6, 2) \rightarrow (2, 6, -1)$ is _____.

Ans. (139)

Sol: $\int_C \text{grad } f \cdot dr = ?$

$$dr = dx\hat{i} + dy\hat{j} + dz\hat{k}$$

and $\text{grad } f = \frac{d}{dx}(2x^3 + 3y^2 + 4z)\hat{i}$

$$+ \frac{d}{dy}(2x^3 + 3y^2 + 4z)\hat{j} + \frac{d}{dz}(2x^3 + 3y^2 + 4z)\hat{k}$$

$$\text{grad } f = (6x^2)\hat{i} + (6y)\hat{j} + (4)\hat{k}$$

So, $\text{grad } f \cdot dr = 6x^2 dx + 6y dy + 4 dz$

$$\int_C \text{grad } f \cdot dr = \int 6x^2 dx + \int 6y dy + \int 4 dz$$

Applying the limits

$$\int_C \text{grad } f \cdot dr = \left[\int_{-3}^2 6x^2 dx + \int_{-3}^{-3} 6y dy + \int_2^2 4 dz \right]$$

$$+ \left[\int_2^2 6x^2 dx + \int_{-3}^6 6y dy + \int_2^2 4 dz \right] +$$

$$\left[\int_2^2 6x^2 dx + \int_6^6 6y dy + \int_2^{-1} 4 dz \right]$$

$$\int_c \text{grad} \cdot \text{fdr} = \left[(2x^3)^2_{-3} + 0 + 0 \right] +$$

$$\left[(3y^2)^6_{-3} + 0 + 0 \right] + \left[0 + 0 + (4z)^{-1}_2 \right]$$

$$\int_c \text{grad} f \cdot \text{dr} = [2(8+27)] + [3 \times (36-9)] + 4[-1-2]$$


$$= 70 + 81 - 12 = 139$$

9. A six-pulse thyristor bridge rectifier is connected to a balanced three-phase, 50 Hz AC source. Assuming that the DC output current of the rectifier is constant, the lowest harmonic component in the AC input current is

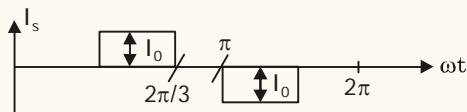- (a) 100 Hz (b) 150 Hz
(c) 300 Hz (d) 250 Hz

Ans. (d)

Sol: Supply current as AC input current of 6 pulse thyristor bridge rectifier is quasi-square waveform.



$$I_{sn} = \sum \frac{4I_0}{n\pi} \sin \frac{n\pi}{3} \sin n\omega t$$

$$n = 6k \pm 1$$

Note: Due to symmetric waveform, even harmonic does not present.


Harmonic present $n = 6k \pm 1$

For lowest component, $k = 1, n = 5, 7$

So, the lowest harmonic component in the AC input current is $n f_{in}$

$$= 50 \times 5 = 250 \text{ Hz}$$

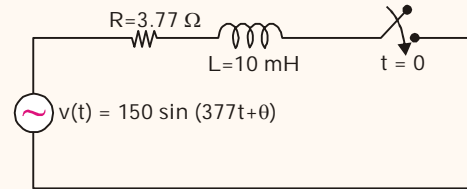
10. In the circuit shown below, the switch is closed at $t = 0$. The value of θ in degrees which will give the maximum value of DC offset of the current at the time of switching is



- (a) -30 (b) -45
(c) 60 (d) 90

Ans. (b)

Sol:

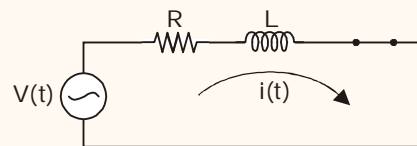

By applying KVL in the loop, we get

$$i(t) \cdot R + L \frac{di(t)}{dt} = V(t)$$

Solving this differential equation

$$i(t) = \left(\text{Complimentary} \right) + \left(\text{Particular} \right)$$

$$i(t) = \left(\text{Integral} \right) + \left(\text{Integral} \right)$$

For complimentary integral

$$i(t) R + L \frac{di(t)}{dt} = 0$$

so, we get $i(t) = A \cdot e^{-Rt/L} \Rightarrow$ DC offset.

For particular integral

$$i(t) = \frac{V_m}{Z} \sin(\omega t + \theta - \phi)$$

where $\omega = 377 \text{ rad/sec}$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$i(t) = A \cdot e^{-Rt/L} + \frac{V_m}{Z} \sin(\omega t + \theta - \phi)$$

Applying boundary conditions

at $t = 0, i(t) = 0$

$$0 = A \cdot e^{-0} + \frac{V_m}{Z} \sin(\omega(0) + \theta - \phi)$$

$$A + \frac{V_m}{Z} \sin(\theta - \phi) = 0$$

$$A = -\frac{V_m}{Z} \sin(\theta - \phi)$$

For maximum value of DC offset "A"

$$\theta - \phi = -90^\circ$$

$$\theta - \tan^{-1}\left(\frac{\omega L}{R}\right) = -90^\circ$$

$$\theta - \tan^{-1}\left(\frac{377 \times 10 \times 10^{-3}}{3.77}\right) = -90^\circ$$

$$\theta - 45^\circ = -90^\circ$$

$$\theta = -45^\circ$$

11. A three-phase synchronous motor draws 200A from the line at unity power factor at rated load. Considering the same line voltage and load., the line current at a power factor of 0.5 leading is

- (a) 400 A (b) 300 A
(c) 200 A (d) 100 A

Ans. (a)

Sol: Considering in per-unit system

Initially,

$$V = V_{\text{rated}} = 1 \text{ pu}$$

$$I = I_{\text{rated}} = 1 \text{ pu} \quad \left(\begin{array}{l} \text{given } I = 200 \text{ A} \\ \text{consider as } I_{\text{base}} \end{array} \right)$$

$$\text{p.f} = 1 \text{ (unity)}$$

So, $P = VI \cos \phi$

$$P = 1 \times 1 \times 1$$

$$P = 1 \text{ pu}$$

Now, $V = V_{\text{rated}} = 1 \text{ pu}$

$$I = ?$$

$$\text{pf} = 0.5$$

and $P = 1 \text{ pu}$

Since, $P = VI \cos \phi$

$$1 = 1 \times I \times 0.5$$

$$I = 2 \text{ pu}$$

So, line current in ampere is $I = 2 \times 200 = 400 \text{ A}$.

12. The partial differential equation

$$\frac{\partial^2 u}{\partial t^2} - C^2 \left(\frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2} \right) = 0 ; \text{ where } c \neq 0 \text{ is known}$$

as

- (a) wave equation
(b) Laplace equation
(c) heat equation
(d) Poisson's equation

Ans. (a)

Sol: (i) Wave equation

$$\frac{\partial^2 u}{\partial t^2} = C^2 \left(\frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2} \right)$$

(ii) Laplace equation

$$\nabla^2 u = \frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2} = 0$$

(iii) Poisson's equation

$$\nabla^2 u = f$$

(iv) Heat equation


$$\frac{\partial u}{\partial t} - \alpha \left(\frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2} + \frac{\partial^2 u}{\partial z^2} \right) = 0$$

13. The parameter of an equivalent circuit of a three-phase induction motor affected by reducing the rms value of the supply voltage at the rated frequency is

- (a) magnetizing reactance
(b) rotor leakage reactance
(c) rotor resistance
(d) stator resistance

Ans. (a)

Sol.

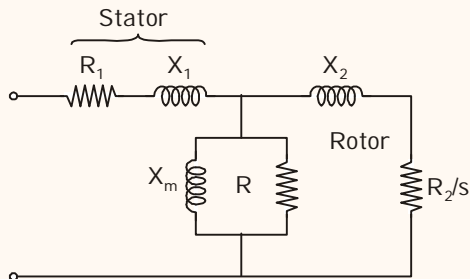

$$\frac{V_1}{f} \propto \phi_m \propto I_m \quad I_m \propto \frac{V}{X_m}$$

$$\frac{V}{f (= \text{const.})} \downarrow \propto \phi_m \downarrow$$

By reducing the rms value of the supply voltage at rated frequency, magnetising current changes which changes the magnetizing reactance.

So, option (1).

14. The symbols, α and T , represent positive quantities, and $u(t)$ is the unit step function. Which one of the following impulse responses is NOT the output of a causal linear time-invariant system?

- (a) $1 + e^{-at}u(t)$ (b) $e^{-a(t-T)}u(t)$
(c) $e^{+at}u(t)$ (d) $e^{-a(t+T)}u(t)$

Ans. (a)

Sol.

$$1 + e^{-at} u(t)$$

Due to presence of 1, Given impulse response is non-causal.

15. Which one of the following function is analytic in the region $|z| \leq 1$?

- (a) $\frac{z^2 - 1}{z}$ (b) $\frac{z^2 - 1}{z + j0.5}$
(c) $\frac{z^2 - 1}{z - 0.5}$ (d) $\frac{z^2 - 1}{z + 2}$

Ans. (d)

Sol. In option 1, 2 and 3 singularities lying inside the contour but in option 4 singularity $z = -2$ lying outside the contour $z = 1$.

So, the function given in option 4 is analytic in the region $|z| \leq 1$.

16. The inverse Laplace transform of $H(s) = \frac{s+3}{s^2+2s+1}$ for $t \geq 0$ is

- (a) $4te^{-t} + e^{-t}$ (b) $2te^{-t} + e^{-t}$
(c) $3te^{-t} + e^{-t}$ (d) $3e^{-t}$

Ans. (b)

Sol: Given from function

$$H(s) = \frac{s+3}{s^2+2s+1} \quad t \geq 0$$

By using partial fraction

$$H(s) = \frac{s+3}{(s+1)^2} = \frac{A}{s+1} + \frac{B}{(s+1)^2}$$

$$s+3 = A(s+1) + B$$

$$\Rightarrow s+3 = As + A + B$$

Equating coefficients, we get

$$\Rightarrow \boxed{A=1}$$

and $\boxed{B=2}$

$$H(s) = \frac{A}{s+1} + \frac{B}{(s+1)^2}$$

$$H(s) = \frac{1}{s+1} + \frac{2}{(s+1)^2}$$

By taking Inverse Laplace, we get

$$h(t) = e^{-t} + (2e^{-t})t$$

$$\boxed{h(t) = 2te^{-t} + e^{-t}}$$



IES MASTER .org

Institute for Engineers (IES/GATE/PSUs)



MASTER TALENT REWARD EXAM (MTRE) A National Level Online Scholarship Test

MTRE-02
Scholarship

Get up to

100% Scholarship

*Write Online
from Anywhere*

Exam Date
3rd March, 2019

Registration Closes on
28th February, 2019

For **ESE & GATE** Aspirants

Session 2019-20

- Opportunity to get up to 100% off on tuition fee
- Chance to study with the best engineering minds
- Learn in a stress-free environment
- Know your ranking at national level

**Registrations
Open**

To get the most out of the MTRE, visit iesmaster.org/master-talent-reward-exam

Email: mtre@iesmaster.org

F-126, Katwaria Sarai, **New Delhi** - 110016 | Call 80100 09955, 011 4101 3406

Email info@iesmaster.org

17. The rank of the matrix, $M = \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$ is _____.

Ans. (3)

Sol: Given data,

$$M = \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}_{3 \times 3}$$

Determinant of M

$$\begin{aligned} |M| &= \begin{vmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{vmatrix} \\ &= 0(0 - 1) - 1(0 - 1) + 1(1 - 0) \\ &= 1 + 1 = 2 \end{aligned}$$

$$\therefore |M| \neq 0$$


Hence, rank of the matrix is '3'.

18. Given, V_{gs} is the gate-source voltage, V_{ds} is the drain source voltage, and V_{th} is the threshold voltage of an enhancement type NMOS transistor, the conditions for transistor to be biased in saturation are :

- (a) $V_{gs} > V_{th}; V_{ds} \leq V_{gs} - V_{th}$
- (b) $V_{gs} > V_{th}; V_{ds} \geq V_{gs} - V_{th}$
- (c) $V_{gs} < V_{th}; V_{ds} \geq V_{gs} - V_{th}$
- (d) $V_{gs} < V_{th}; V_{ds} \leq V_{gs} - V_{th}$

Ans. (b)

Sol.

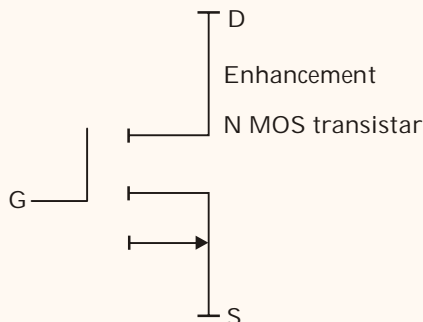


Condition for Transistor in saturation

$$V_{GS} > V_{th}$$

and

$$V_{DS} > V_{ov}$$


$$V_{DS} > V_{GS} - V_{th}$$

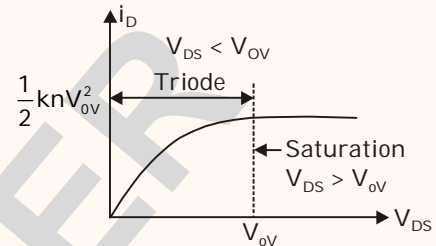

19. The total impedance of the secondary winding, leads, and burden of a 5 A CT is 0.01Ω . If the fault current is 20 times the rated primary current of the CT, the VA output of the CT is _____.

Ans. (100)

Sol:

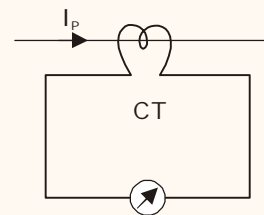

Secondary rated current of CT = 5A

Secondary impedance = 0.01Ω

$$\text{CT Ratio} = \frac{\text{Primary current}}{\text{Secondary current}}$$

Since, fault current is 20 times the rated primary current.

Hence, secondary current of CT will also be 20 times the rated secondary current.

Now, when fault occurs, the secondary current will be

$$\begin{aligned} I_s &= 20 \times \text{Rated secondary current of CT} \\ &= 20 \times 5\text{A} \\ &= 100\text{A} \end{aligned}$$

Hence, VA output of the CT

$$\begin{aligned}
 &= EI \\
 &= (IZ) \times I \\
 &= (100 \times 0.01) \times 100 \\
 &= 100 \text{ VA}
 \end{aligned}$$

20. The characteristic equation of a linear time-invariant (LTI) system is given by

$$\Delta(s) = s^4 + 3s^3 + 3s^2 + s + k = 0$$

The system is BIBO stable if

- (a) $k > 6$ (b) $0 < k < \frac{8}{9}$
 (c) $0 < k < \frac{12}{9}$ (d) $k > 3$

Ans. (b)

Sol: R-H criteria

S^4	1	3	k
S^3	3	1	0
S^2	$\frac{8}{3}$	k	
S^1	$\frac{8/3 - 3k}{8/3}$	0	
S^0	k		

For BIBO stable, all elements of first column have same sign,

$$k > 0 \text{ and } \frac{\frac{8}{3} - 3k}{\frac{8}{3}} > 0$$


$$\Rightarrow k < \frac{8}{9}$$

$$\text{Hence, } 0 < k < \frac{8}{9}$$


21. Five alternators each rated 5 MVA, 13.2 kVA with 25% of reactance on its own base are connected in parallel to a busbar. The short-circuit level in MVA at the busbar is _____.

Ans. (100)

Sol: According to the given condition.

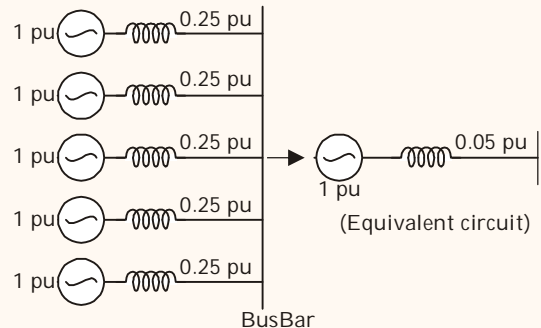

For short circuit current (I_f)

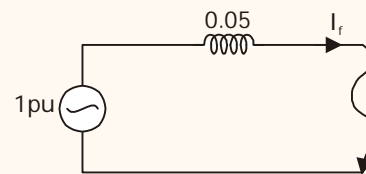

$$I_f = \frac{V_{pu}}{X_{pu}} = \frac{1}{0.05}$$

$$I_f = 20pu$$

So, short circuit level in MVA is (I_f) × (MVA rating of alternator)

$$\text{S.C (MVA) level} = 20 \times 5 \text{ (MVA)} = 100 \text{ MVA}$$

22. A system transfer function is $H(s) = \frac{a_1s^2 + b_1s + c_1}{a_2s^2 + b_2s + c_2}$. If $a_1 = b_1 = 0$, and all other coefficients are positive, the transfer function represents a

- (a) high pass filter (b) notch filter
 (c) low pass filter (d) band pass filter

Ans. (c)

Sol.

$$H(s)|_{a_1=b_1=0} = \frac{c_1}{a_2s^2 + b_2s + c_2}$$

$$H(j\omega) = \frac{c_1}{j\omega b_2 - a_2(\omega)^2 + c_2}$$

at $\omega = 0$


$$H(j\omega) = c_1/c_2 = K$$

at $\omega = \infty$

$$H(j\omega) = 0$$


So, given filter is a low pass filter.

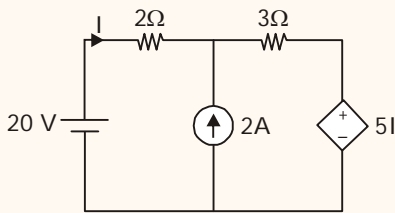23. The current I flowing in the circuit shown below in amperes (round off to one decimal place) is _____.



Ans. (1.4 amp)

Sol.

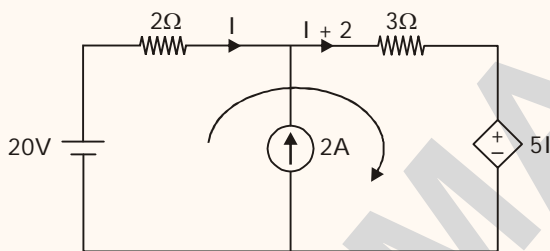

Current distribution is shown in the above diagram.

Applying KVL in the loop

$$20 - 2I - 3(I + 2) - 5I = 0$$

$$20 - 10I - 6 = 0$$

$$10I = 14$$

$$I = 1.4 \text{ Ampere}$$

24. M is a 2×2 matrix with eigenvalues 4 and 9. The eigenvalues of M^2 are

- (a) -2 and -3 (b) 2 and 3
(c) 4 and 9 (d) 16 and 81

Ans. (d)

Sol: When M is required, the eigen vectors remain unchanged whereas, the eigen values are squared.

Hence, eigen values of M^2 are 16 and 81.

Proof: Let λ be the eigen value of A^2 , then

$$|A^2 - \lambda I| = 0$$

$$\text{or } (A - \sqrt{\lambda}I)(A + \sqrt{\lambda}I) = 0$$

$$\text{hence, either } |A - \sqrt{\lambda}I| = 0$$

$$\text{or } |A + \sqrt{\lambda}I| = 0$$

Eigen values of A are $\sqrt{\lambda}$ or $-\sqrt{\lambda}$.


25. The Y_{bus} matrix of a two-bus power system having two identical parallel lines connected between them in pu is given as

$$Y_{bus} = \begin{bmatrix} -j8 & j20 \\ j20 & -j8 \end{bmatrix}$$

The magnitude of the series reactance of each line in pu (round off to one decimal place) is _____.

Ans. (0.1)

Sol:

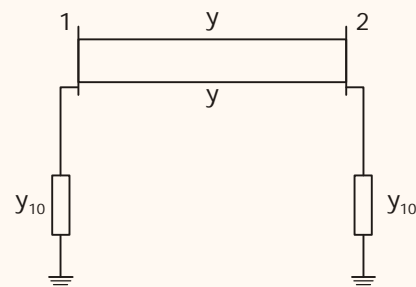

Let, y be the admittance of identical lines and, y_{10} and y_{20} is the shunt admittance connected at bus-1 and bus-2 respectively.

Then, by using direct inspection method, Y_{BUS} is given as,

$$Y_{BUS} = \begin{bmatrix} y_{10} + 2y & -2y \\ -2y & y_{20} + 2y \end{bmatrix}$$



IES MASTER

Institute for Engineers (IES/GATE/PSUs)

CONVENTIONAL QUESTION PRACTICE PROGRAM for ESE - 2019 Mains Exam

COMPLETE PACKAGE

Classroom Program

includes
Subject-wise tests



Conventional Test Series

includes
11 Mixed Topic-wise & 6 Full-length tests



RANK
Prize

1st

₹3000/-

2nd

₹2500/-

3rd

₹2000/-

4th

₹1500/-

5th

₹1000/-

6-10th

₹500/-

Classroom Program

18th Feb | Monday to Saturday

250-300 hrs

8:30 am to 2:30 pm

- Subject wise Practice, Discussion and Test
- Practice Booklets with Solution Outlines
- How to Write Answer- Test & Counselling Session
- Discussion and Practice Session of 250-300 hrs
- Under Guidance of Mr. Kanchan Kr. Thakur

Conventional Test Series

17th March | Every Sunday

a) New Topics b) Revision Topics

- Classroom Solutions + Discussion
- Improve Question Selection Ability
- Cover all Concepts in Various Topics
- Improve Time Management
- Under Simulated Classroom Exam Env.
- Unique Approach : Test on New Topics + Revision Topics

Course	Branch	Fees (₹)
Complete Package (Classroom Program + Conventional Test Series) for Non IES Master Students	CE	18000/-
Complete Package (Classroom Program + Conventional Test Series) for Ex- IES Master Students	CE	15000/-
Conventional Classroom Program (For Non IES Master Students)	CE	15000/-
Conventional Classroom Program (For Ex- IES Master Students)	CE	12000/-
Conventional Classroom Program (For Current year IES Master Classroom Program Students)	CE	10000/-
Conventional Offline Test Series (For Non IES Master Students)	CE, ME, EE, ECE	5000/-
Conventional Offline Test Series (For Ex- IES Master Students)	CE, ME, EE, ECE	4000/-
Conventional Offline Test Series (For Current year IES Master Classroom Program Students)	CE, ME, EE, ECE	Free
Conventional Online Test Series (For All Students)	CE, ME, EE, ECE	3000/-



Students can also
pay online

HOW TO APPLY

Students can register by making payments
in person with Cash/DD at our office located at

F-126, Katwaria Sarai, New Delhi - 110016
from 9 am to 8:30 pm

For Query

8010009955

9711853908

Comparing this matrix with given by y_{BUS} ,

$$y_{10} + 2y = -j8$$

$$y_{20} + 2y = -j8$$

$$2y = -j20$$

$$\Rightarrow y = -j10$$

Hence, series reactance = $\frac{1}{10} = 0.10$

26. The closed loop line integral

$$\oint_{|z|=5} \frac{z^3 + z^2 + 8}{z + 2} dz$$

evaluated counterclockwise, is

(a) $-4j\pi$ (b) $+8j\pi$

(c) $-8j\pi$ (d) $+4j\pi$

Ans. (b)

Sol: According to **Cauchy's integral formula**

$$f(a) = \frac{1}{2\pi j} \int_C \frac{f(z)}{(z-a)} dz$$

(if $f(z)$ is analytic within and on the closed curve C)

Hence,

$$\int_C \frac{f(z)}{(z+2)} \{ \text{where, } f(z) = z^3 + z^2 + 8 \}$$

$$= 2\pi j f(-2) \quad \{ \because a = -2 \}$$

$$= 2\pi j (-8 + 4 + 8)$$

$$= +j8\pi$$

27. A DC-DC buck converter operates in continuous conduction mode. It has 48 V input voltage, and it feeds a resistive load of 24Ω . The switching frequency of the converter is 250 Hz. If switch-on duration is 1 ms, the load power is

(a) 48 W

(b) 24 W

(c) 12 W

(d) 6 W

Ans. (d)

Sol. Given,


$$V_{dc} = 48 \text{ V}$$

$$R = 24\Omega$$

$$f_s = 250 \text{ Hz}$$

$$T_{on} = 1 \text{ msec}$$

$$P_{load} = ?$$

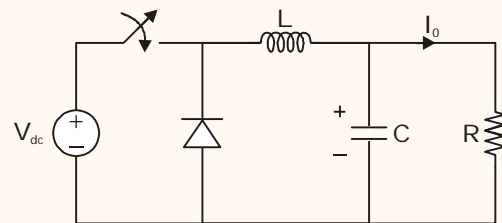


(Buck converter)

So, $D = \frac{T_{ON}}{T} = T_{on} f$

$$D = (1 \times 10^{-3})(250)$$

$$\boxed{D = 0.25}$$

Waveform

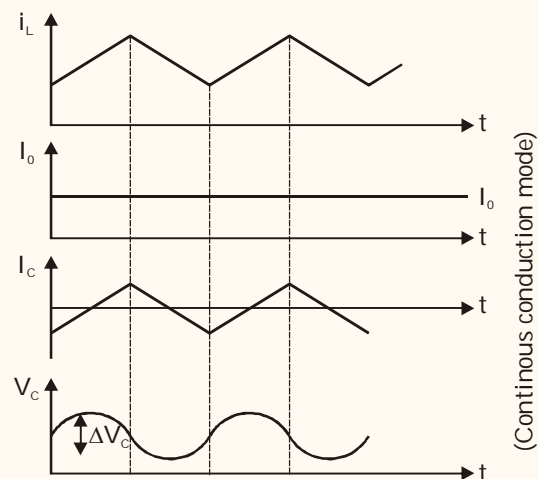

Current I_o is ripple free due to high value of inductor present in Buck converter. But V_c have some ripple.

Considering fourier transform of I_o and V_c

$$I_o = I_{0avg}$$

$$\text{Power} = (V_{0avg} \times I_{0avg}) + (\text{harmonics power})$$

\therefore Harmonics power = 0; (Because no harmonics in current I_o)

$$P = (V_{0avg}) \left(\frac{V_{0avg}}{R} \right)$$

$$= \frac{(V_{0avg})^2}{R}$$

$$V_{0avg} = \alpha V_s = 0.25 \times 48 = 12 \text{ V}$$

$$P = \frac{(12)^2}{24}$$

$$\boxed{P = 6 \text{ W}}$$

28. The voltage across and the current through a load are expressed as follows

$$v(t) = -170 \sin \left(377t - \frac{\pi}{6} \right) \text{ V}$$

$$i(t) = 8 \cos \left(377t + \frac{\pi}{6} \right) \text{ A}$$

The average power in watts (round off to one decimal place) consumed by the load is _____

Ans. (588.9)

Sol: Given data,

$$v(t) = -170 \sin \left(377t - \frac{\pi}{6} \right) \text{ V}$$

$$= 170 \cos \left(377t + \frac{\pi}{3} \right) \text{ V}$$

and $i(t) = 8 \cos \left(377t + \frac{\pi}{6} \right) \text{ A}$

The average power is given as,

$$P = VI \cos \phi$$

where, V and I are the rms values and ϕ is the phase angle difference or power factor angle between $v(t)$ and $i(t)$.

$$\text{So, that, } V = \frac{170}{\sqrt{2}} \text{ V, } I = \frac{8}{\sqrt{2}}, \phi = \frac{\pi}{6}$$


$$\Rightarrow P = \frac{170}{\sqrt{2}} \times \frac{8}{\sqrt{2}} \times \cos \frac{\pi}{6} = 588.9 \text{ Watts}$$

29. A fully-controlled three-phase bridge converter is working from a 415 V, 50 Hz AC supply. It is supplying constant current of 100 A at 40 V to a DC load. Assume large inductive smoothing and neglect overlap. The rms value of the AC line current in amperes (round off to two decimal places) is _____.

Ans. (81.649A)

Sol. For 3 phase 6 pulse AC to DC converter, source current is quasi square waveform.

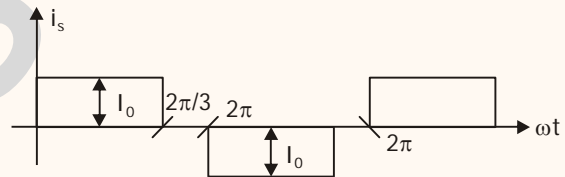SCR conducts for $(2\pi/3)$ in 2π period.



$$\Rightarrow I_{Sr} = I_o \sqrt{\frac{2\pi/3}{\pi}} = I_o \sqrt{\frac{2}{3}}$$

$$\Rightarrow I_{Sr} = 100 \times \sqrt{\frac{2}{3}} = 81.649 \text{ A}$$


30. A 220 V (line), three-phase, Y-connected, synchronous motor has a synchronous impedance of $(0.25 + j2.5) \Omega/\text{phase}$. The motor draws the rated current of 10A at a 0.8 pf leading. The rms value of line-to-line internal voltage in volts (round off to two decimal places) is _____.

Ans. (245.34 volts)

Sol.

$$z_s = (0.25 + j2.5) \Omega/\text{ph}$$
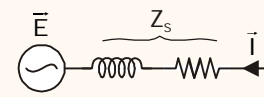
$$I = 10 \text{ A, } 0.8 \text{ pf leading}$$



$$\vec{V} = \frac{220}{\sqrt{3}} \angle 0^\circ$$

$$\vec{E} = \vec{V} - \vec{I} \vec{Z}_s$$

$$\bar{E} = \frac{220}{\sqrt{3}} \angle 0^\circ - (10 \angle \cos^{-1}(0.8))(0.25 + j2.5)$$

$$\bar{E} = 127.01 + 13 - 21.5j$$

$$\bar{E} = 140.01 - 21.5j$$

$$\bar{E} = 141.65 \angle -8.736^\circ \text{ volts (per phase)}$$

$$|E_{L-L}| = \sqrt{3} \times 141.65$$

$$|E_{L-L}| = 245.345 \text{ volts}$$

31. The probability of a resistor being defective is 0.02. There are 50 such resistors in a circuit. The probability of two or more defective resistors in the circuit (round off to two decimal places) is ____.

Ans. (0.26)

Sol. Probability of a resistor being defective

$$p(\text{def}) = 0.02$$

Numbers of resistors = 50

Approximated Poisson distribution will have mean = $\mu = np$

$$\Rightarrow \mu = 50 \times 0.02 = 1$$

Poisson distribution,

$$f(x) = \frac{e^{-\mu} \mu^x}{x!}$$


$$p(0 \text{ defective}) = \frac{e^{-\mu} \mu^0}{0!} = e^{-1}$$

$$p(1 \text{ defective}) = \frac{e^{-\mu} \mu^1}{1!} = e^{-1}$$

$$p(2 \text{ or more defective}) = 1 - p(0 \text{ defective}) - p(1 \text{ defective})$$

$$\begin{aligned} \Rightarrow p(2 \text{ or more defective}) &= 1 - e^{-1} - e^{-1} = 1 - 2e^{-1} \\ &= 0.26 \end{aligned}$$

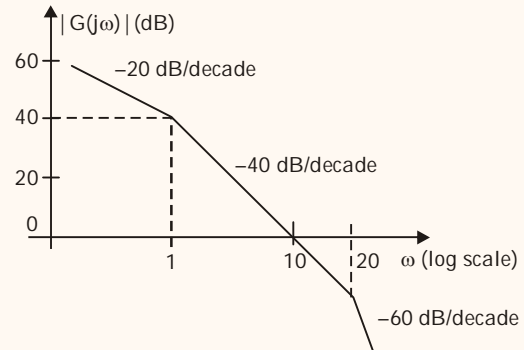32. The asymptotic Bode magnitude plot of a minimum phase transfer function $G(s)$ is shown



Consider the following two statements.

Statement I : Transfer function $G(s)$ has three poles and one zero

Statement II : At very high frequency ($\omega \rightarrow \infty$),


the phase angle $\angle G(j\omega) = -\frac{3\pi}{2}$

Which of the following options is correct ?

- (a) Statement I is true and statement II is false.
(b) Both the statements are true
(c) Both the statements are false
(d) Statement I is false and statement II is true.

Ans. (d)

Sol.

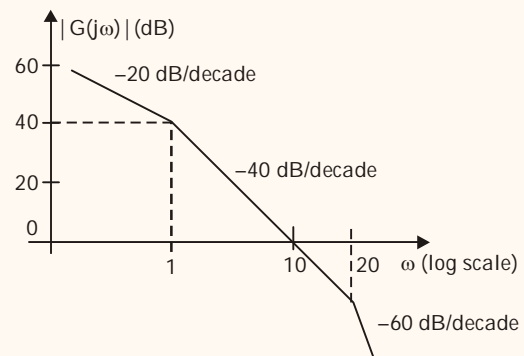

Transfer function of given Bode plot is

$$\begin{aligned} &= \frac{K}{s \left(1 + \frac{s}{1}\right) \left(1 + \frac{s}{20}\right)} \\ G(s) &= \frac{K(20)}{s(s+1)(s+20)} \end{aligned}$$



IES MASTER

Institute for Engineers (IES/GATE/PSUs)

ESE-2019 Conventional Test Schedule, Electrical Engineering

Date	Topic
17th Mar 2019	N.T. : ECF-1, MC-1, MC-2, ADE-2
	R.T. :
24th Mar 2019	N.T. : ECF-2, MI-1, CS-1, CS-2
	R.T. : ECF-1, MC-1, MC-2, ADE-2
31st Mar 2019	N.T. : ECF-3, MI-2, MC-3, MC-4
	R.T. : ECF-2, MI-1, CS-1, CS-2
07th Apr 2019	N.T. : BEX-1, ADE-1, ADE-3
	R.T. : ECF-3, MI-2, MC-3, MC-4
14th Apr 2019	N.T. : EM-1, MATH-1, PS-1, SSP-1
	R.T. : BEX-1, ADE-1, ADE-3
21st Apr 2019	N.T. : CF-1, MATH-2, PS-2, PE-1
	R.T. : EM-1, MATH-1, PS-1, SSP-1
28th Apr 2019	N.T. : BEX-2, MI-3, CS-3, SSP-2
	R.T. : CF-1, MATH-2, PS-2, PE-1
05th May 2019	N.T. : EM-2, PS-3
	R.T. : BEX-2, MI-1, MI-3, CS-3, SSP-2, ADE-3, MC-1, MC-2
12th May 2019	N.T. : CF-2, PE-2
	R.T. : EM-2, ECF-1, ECF-3, MI-2, PS-2, PS-3, ADE-2, CS-2
19th May 2019	N.T. : CF-3, MATH-3
	R.T. : CF-2, ECF-2, MI-1, BEX-1, EM-1, CS-1, MI-3, CS-3, ADE-3, PE-2, SSP-1
26th May 2019	N.T. :
	R.T. : MATH-1, MATH-3, EM-1, EM-2, ECF-1, BEX-2, CF-3, ADE-2, CS-2, PS-1, PS-3, PE-1, SSP-2
02nd Jun 2019	Full Length-1 (Test Paper-1 + Test Paper-2)
09th Jun 2019	Full Length-2 (Test Paper-1 + Test Paper-2)
16th Jun 2019	Full Length-3 (Test Paper-1 + Test Paper-2)

Test Type

Timing

Day

Conventional Test	10:00 A.M. to 1:00 P.M.	Sunday
Conventional Full Length Test Paper-1	10:00 A.M. to 1:00 P.M.	Sunday
Conventional Full Length Test Paper-2	02:00 P.M. to 5:00 P.M.	Sunday

Note : The timing of the test may change on certain dates. Prior information will be given in this regard.

*N.T. : New Topic. *R.T. : Revision Topic

Call us : 8010009955, 011-41013406 or Mail us : info@iesmaster.org

Subject Code Details

Engineering Mathematics (MATH)	MATH-1	MATH-2		MATH-3
	◆ Linear Algebra ◆ Complex Variables ◆ Transform Theory	◆ Calculus ◆ Differential Equations		◆ Probability and Statistics ◆ Numerical Methods
Electrical Materials (EM)	EM-1		EM-2	
	◆ Crystal Structures & Solid State ◆ Band Theory ◆ Dielectrics ◆ Magnetic materials		◆ Conductive materials ◆ Photo conductivity ◆ Nano materials ◆ Superconductors	
Electric Circuits & Fields (ECF)	ECF-1	ECF-2		ECF-3
	◆ Circuit Elements ◆ 3-phase Circuits ◆ Network Graphs ◆ Transient and steady state Response	◆ Magnetically Coupled Circuits ◆ Network Theorems ◆ Two-port networks ◆ Resonance ◆ Basic Filters		◆ Electrostatics and Magneto statics ◆ Time varying fields & Maxwell's Equations
Electrical & Electronic Measurements	MI-1	MI-2		MI-3
	◆ Errors, Units, Dimensions & standards ◆ Galvanometers ◆ Types of Instruments ◆ Measurement of Power	◆ Measurement of Energy ◆ Measurement of resistance ◆ Potentiometers ◆ AC bridges ◆ CRO ◆ Q-meter		◆ Electronic Instrumentation ◆ Data Acquisition System ◆ Transducers
Computer Fundamentals (CF)	CF-1	CF-2		CF-3
	◆ Architecture, CPU, I/O, Memory, Peripheral devices ◆ Boolean algebra ◆ Number system arithmetic functions	◆ Basic of OS, Virtual memory ◆ File system ◆ Networking		◆ Data Representation and Programming, Programming languages
Basic Electronics Engineering (BEX)	BEX-1		BEX-2	
	◆ Basics of diodes, BJT, FET, MOSFET		◆ Transistor amplifiers – equivalent circuits & frequency response ◆ Oscillators, Feedback amplifiers	
Analog Digital Electronics (ADE)	ADE-1	ADE-2		ADE-3
	◆ OPAMP ◆ Multivibrator, Sample and Hold circuits ◆ Filters	◆ Digital Electronics ◆ Microprocessors		◆ Communications
Systems and Signal Processing (SSP)	SSP-1		SSP-2	
	◆ Continuous & discrete-time signals ◆ Shifting and scaling ◆ Linear, time-invariant and causal system ◆ Laplace & Z-transform		◆ Fourier series ◆ Discrete Fourier Transform ◆ FFT ◆ FIR and IIR Filters ◆ Bilinear Transformation	
Control System (CS)	CS-1		CS-2	
	◆ Basics ◆ Block diagram Algebra ◆ Signal flow ◆ Mathematical Modeling		◆ Time Response Analysis ◆ Stability ◆ Root Locus	
Electrical Machines (MC)	MC-1	MC-2		MC-3
	◆ Transformers ◆ Basic concepts of Rotating Machines	◆ Polyphase Induction Machines ◆ Single Phase motors		◆ DC Machines
Power System (PS)	PS-1		PS-2	
	◆ Electric Power Sources-Thermal, Hydro Nuclear, Wind & Solar ◆ Performance of lines & cables ◆ HVDC & Corona ◆ Smart Grid; Environment Implications		◆ Symmetrical Components & Fault Analysis ◆ Power System stability & dynamics ◆ Load flow; Matrix Representation	
Power Electronics and Drivers (PE)	PE-1		PE-2	
	◆ Power Semiconductor Devices ◆ High Frequency Inductors & transformers ◆ Diode Rectifiers ◆ Phase Controlled Rectifiers		◆ Choppers; DC-DC switched mode converters ◆ Inverters; DC-AC switched mode converters ◆ AC Voltage Controllers ◆ Cycloconverters ◆ Electric Drives ◆ Resonant Converters	

$$\phi(j\omega) = -90^\circ - \tan^{-1} \omega - \tan^{-1} \left(\frac{\omega}{20} \right)$$

Transfer function G(s) has only three Poles.

So, statement I is false.

$$\begin{aligned} \text{and } \phi(j\omega) \Big|_{\omega \rightarrow \infty} &= -90 - 90 - 90 = -270 \\ &= -\frac{3\pi}{2} \end{aligned}$$

So, statement II is true.

Option (d)

33. Consider a 2×2 matrix $M = [v_1 \ v_2]$ where, v_1 and v_2 are the column vectors. Suppose

$M^{-1} = \begin{bmatrix} u_1^T \\ u_2^T \end{bmatrix}$, where u_1^T and u_2^T are the row vectors. Consider the following statements :

Statement I : $u_1^T v_1 = 1$ and $u_2^T v_2 = 1$

Statement II : $u_1^T v_2 = 0$ and $u_2^T v_1 = 0$

- (a) Statement 1 is true and statement 2 is false
(b) Both the statements are false
(c) Statement 2 is true and statement 1 false
(d) Both the statements are true.

Ans. (4)

Sol. Let $M = \begin{bmatrix} a & b \\ c & d \end{bmatrix} = [V_1 \ V_2]$,

$$V_1 = \begin{bmatrix} a \\ c \end{bmatrix}, V_2 = \begin{bmatrix} b \\ d \end{bmatrix}$$

$$M^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix} = \begin{bmatrix} U_1^T \\ U_2^T \end{bmatrix}$$

$$U_1^T = \begin{bmatrix} d & -b \\ ad-bc & ad-bc \end{bmatrix}$$

$$U_2^T = \begin{bmatrix} -c & a \\ ad-bc & ad-bc \end{bmatrix}$$

Checking given statement

Statement-I:

$$\begin{aligned} U_1^T V_1 &= \begin{bmatrix} d & -b \\ ad-bc & ad-bc \end{bmatrix} \begin{bmatrix} a \\ c \end{bmatrix} = 1 \\ &= \frac{ad-bc}{ad-bc} = 1 \end{aligned}$$

$$\begin{aligned} U_2^T V_2 &= \begin{bmatrix} -c & a \\ ad-bc & ad-bc \end{bmatrix} \begin{bmatrix} b \\ d \end{bmatrix} \\ &= \frac{-bc+ad}{ad-bc} = 1 \end{aligned}$$

So, statement 1 true.

Statement-II:

$$\begin{aligned} U_1^T V_2 &= \begin{bmatrix} d & -b \\ ad-bc & ad-bc \end{bmatrix} \begin{bmatrix} b \\ d \end{bmatrix} \\ &= \frac{bd}{ad-bc} - \frac{bd}{ad-bc} = 0 \end{aligned}$$

$$\begin{aligned} U_2^T V_1 &= \begin{bmatrix} -c & a \\ ad-bc & ad-bc \end{bmatrix} \begin{bmatrix} a \\ c \end{bmatrix} \\ &= \frac{-ac}{ad-bc} + \frac{ac}{ad-bc} = 0 \end{aligned}$$

Statement-II true.

34. The transfer function of a phase lead compensator is given by

$$D(s) = \frac{3\left(s + \frac{1}{3T}\right)}{\left(s + \frac{1}{T}\right)}$$

The frequency (in rad/sec), at which $\angle D(j\omega)$ is maximum is

- (a) $\sqrt{\frac{1}{3T^2}}$ (b) $\sqrt{3T}$
(c) $\sqrt{\frac{3}{T^2}}$ (d) $\sqrt{3T^3}$

Ans. (a)

Sol. Given phase lead compensator transfer function

$$D(s) = \frac{3\left(s + \frac{1}{3T}\right)}{\left(s + \frac{1}{T}\right)}$$

The Frequency (in rad/sec) at which $\angle D(j\omega)|_{\max}$

$$\omega_m = \sqrt{\text{zero} \times \text{pole}}$$

$$\omega_n = \sqrt{\left(\frac{-1}{3T}\right) \times \left(\frac{-1}{T}\right)} = \sqrt{\frac{1}{3T^2}}$$

$$\omega_m = \sqrt{\frac{1}{3T^2}}$$

35. A single-phase controlled thyristor converter is used to obtain an average voltage of 180 V with 10A constant current to feed a DC load. It is fed from single-phase AC supply of 230V, 50 Hz. Neglect the source impedance. The power factor (round off to two decimal places) of AC main is _____.

Ans. (0.7826)

Sol. Given:

Single phase full controlled converter

$V_0 = 180$ volt = average output voltage

$V_{ac_{rms}} = 230$ volt

$$\text{Input power factor} = \frac{V_0 I_0}{V_{sr} I_{sr}} = \frac{180 \times 10}{230 \times 10}$$


$$\text{IPF} = \left(\frac{180}{230}\right) = 0.7826$$

36. The line currents of a three-phase four wire system are square waves with amplitude of 100 A. These three currents are phase shifted by 120° with respect to each other. The rms value of neutral current is

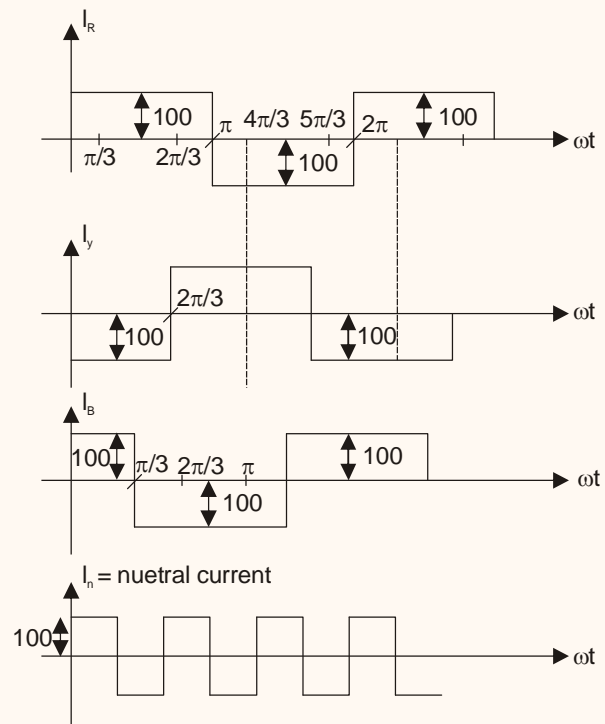- (a) 300 A (b) 0 A
(c) $\frac{100}{\sqrt{3}}$ A (d) 100 A

Ans. (d)

Sol. Line current of a $3\phi - 4$ wire system are square wave and phase shifted by 120° with respect to each other



We get neutral current a square wave form of time period $\frac{2\pi}{3}$.

The neutral current can be expressed at

$$i_n = \begin{cases} 100A, & 0 \leq t < \frac{\pi}{3} \\ -100A, & \frac{\pi}{3} \leq t < \frac{2\pi}{3} \end{cases}$$

This square waveform can be split into

$$i_{n1} = 100A; \quad 0 \leq t < \frac{\pi}{3}$$

$$i_{n2} = -100A; \quad \frac{\pi}{3} \leq t < \frac{2\pi}{3}$$

For rms value,

$$i_{n1}|_{rms} = 100 \sqrt{\frac{t_1}{T}}$$

$$i_{n2}|_{rms} = \left(\frac{1}{T} \int_{t_1}^T (-100)^2 \cdot d(\omega t) \right)^{1/2}$$

$$= 100 \sqrt{\frac{T - t_1}{T}}$$

where, $t_1 = \frac{\pi}{3}$ and $T = \frac{2\pi}{3}$

$$\text{Now, } i_{n1}|_{rms} = 100 \sqrt{\frac{\pi/3}{2\pi/3}} = \frac{100}{\sqrt{2}}$$


$$i_{n2}|_{rms} = 100 \sqrt{\frac{\pi/3}{2\pi/3}} = \frac{100}{\sqrt{2}}$$

$$\text{Now, } i_{n}|_{rms} = \sqrt{(i_{n1}|_{rms})^2 + (i_{n2}|_{rms})^2}$$

$$= \sqrt{\frac{100^2}{2} + \frac{100^2}{2}}$$

$$= 100 \text{ A}$$

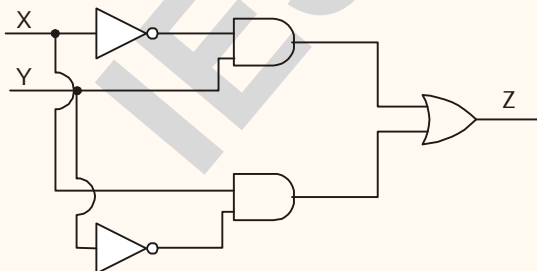
37. In the circuit shown below, X and Y are digital inputs, and Z is a digital output. The equivalent circuit is a



- (a) XOR gate (b) NOR gate
(c) NAND gate (d) XNOR gate

Ans. (a)

Sol:

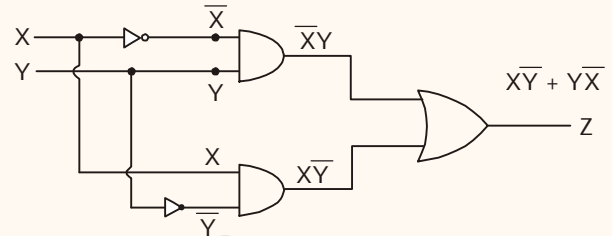

$$Z = \bar{X}Y + X\bar{Y}$$

$$\boxed{Z = X \oplus Y}$$

It is an XOR gate.

38. A moving coil instrument having a resistance of 10Ω gives a full scale deflection when the current is 10 mA. What should be the value of the series resistance, so that it can be used as voltmeter for measuring potential difference up to 100 V ?

- (a) 990Ω (b) 9990Ω
(c) 99Ω (d) 9Ω

Ans. (b)


Sol. Given:

PMMC instrument

$$I_{fs} = 10\text{mA}$$

$$R_{in} = 10\Omega$$

$$10\Omega, 10\text{mA}$$

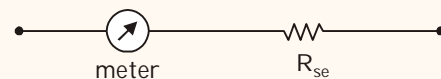

Hence, $100 = 10 \times 10^{-3} \times (10 + R_{se})$

$$\Rightarrow 10 + R_{se} = \frac{100}{10^{-2}} = 10000$$

$$\Rightarrow R_{se} = 10000 - 10 = 9990\Omega$$

i.e. series resistance = 9990Ω

39. A 30 kV, 50 Hz, 50 MVA generator has the positive, negative, and zero sequence reactances of



IES MASTER .org

Institute for Engineers (IES/GATE/PSUs)

Railway Recruitment Board Junior Engineers (RRB-JE)



IES Master Announces

Classroom Course and Online Test Series

RRB-JE 2019

1st stage CBT

Batches starts from **18th Feb**

Classroom Course

Subjects Covered:

- Mathematics
- General Intelligence & Reasoning
- General Awareness
- General Science

Online Test Series **FREE** with Classroom Course

Starts from **23rd Feb**

Online Test Series

- 12 Topic-wise
- 4 Subject-wise
- 8 Mixed Subjects Tests
- 6 Full Length Tests

Total: **30 Tests**

Classroom Program and Online Test Series for RRB-JE 2nd Stage CBT to be announced soon.

Enroll Now



For further details and updated information, visit iesmaster.org
or contact us at 8010009955, 971185 3908

0.25 pu, 0.15 pu, and 0.05 pu, respectively. The neutral of the generator is grounded with a reactance so that the fault current for a bolted LG fault and that of a bolted three-phase fault at the generator terminal are equal. The value of grounding reactance in ohms (round off to one decimal place) is ____.

Ans. (1.8)

Sol: Fault current for single line to ground fault

$$I_{FLG} = \frac{3V}{(x_0 + x_1 + x_2 + 3x_n)} \dots (i)$$

x_0 = Zero sequence reactance

x_1 = Positive sequence reactance

x_2 = Negative sequence reactance

x_n = Neutral reactance of generator

Fault current for 3 ϕ fault

$$I_{f3\phi} = \frac{V}{x_1}$$

Given, $I_{fLG} = I_{f3\phi}$

$$\text{So, } \frac{3V}{x_0 + x_1 + x_2 + 3x_n} = \frac{V}{x_1}$$

$$3x_1 = x_0 + x_1 + x_2 + 3x_n$$

$$x_n = \frac{2x_1 - x_0 - x_2}{3}$$


$$x_n = \frac{2(0.25) - 0.05 - 0.15}{3}$$

$$x_n = 0.1 \text{ pu}$$

$$x_n (\text{in } \Omega) = (0.1) \times \left(\frac{(30)^2}{50} \right)$$

$$x_n (\text{in } \Omega) = 1.8 \Omega$$

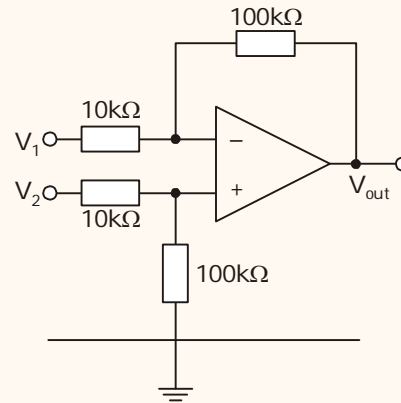
40. In the circuit below, the operational amplifier is ideal. If $V_1 = 10 \text{ mV}$ and $V_2 = 50 \text{ mV}$, the output voltage (V_{out}) is



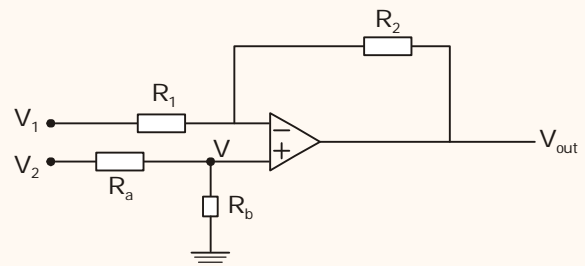- (a) 100 mV (b) 600 mV
(c) 400 mV (d) 500 mV

Ans. (c)

Sol: Sources are connected on both terminals, so we applied Superposition theorem,



$$V_{out} = \left(-\frac{R_2}{R_1} \right) V_1 + \left(1 + \frac{R_2}{R_1} \right) V$$

$$\begin{cases} R_1 = 10 \text{ k}\Omega \\ R_2 = 100 \text{ k}\Omega \\ R_a = 10 \text{ k}\Omega \\ R_b = 100 \text{ k}\Omega \end{cases}$$


and $V = \left(\frac{R_b}{R_a + R_b} \right) V_2$

$$\text{So, } V_{out} = \left(-\frac{R_2}{R_1} \right) V_1 + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_b}{R_a + R_b} \right) V_2$$

$$V_{out} = \left(-\frac{100}{10} \right) (10) + \left(1 + \frac{100}{10} \right) \left(\frac{100}{10+100} \right) (50)$$

$$V_{out} = 400 \text{ mV}$$

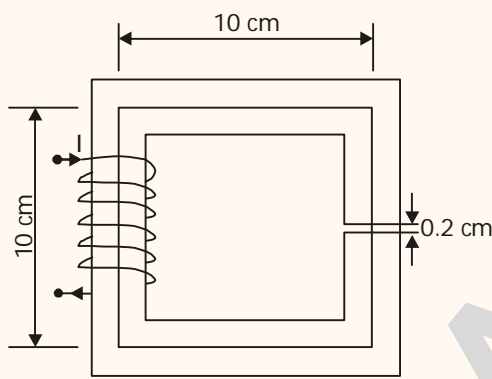41. The magnitude circuit shown below has uniform cross-sectional area and air gap of 0.2 cm. The mean path length of the core is 40 cm. Assume that leakage and fringing fluxes are negligible. When the core relative permeability is assumed to be infinite, the magnetic flux density computed in the air gap is 1 tesla. With same Ampere-turns, if the core relative permeability is assumed to be 1000 (linear), the flux density in tesla (round off to three decimal places) calculated in the air gap is ____.




Ans. (0.834)

Sol.

$$l_{\text{core}} = 40 - 0.2 = 39.8 \text{ cm}$$

$$l_{\text{air}} = 0.2 \text{ cm}$$

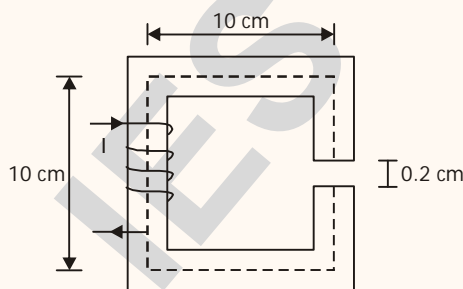

Let a = uniform x-sectional area

We know that

$$\phi = \text{flux} = \frac{\text{MMF}}{\text{Total reluctance}} = \frac{NI}{S_T}$$

$$S_T = S_{\text{airgap}} + S_{\text{core}}$$

$$= \left[\frac{l_{\text{air}}}{\mu_0 (1) a} + \frac{l_{\text{core}}}{\mu_0 \cdot \mu_r \cdot a} \right]$$

$$S_T = \frac{1}{\mu_0 a} \left[l_{\text{air}} + \frac{l_{\text{core}}}{\mu_r} \right]$$

Case 1 : When $\mu_{r \text{ core}} \rightarrow \infty$, $B = 1 \text{ T}$

$$\Rightarrow \text{MMF} = NI = B_1(a) \left[l_{\text{air}} + \frac{l_{\text{core}}}{\mu_r \rightarrow \infty} \right] \frac{1}{\mu_0 a}$$

$$\Rightarrow NI = 1(a) \left[l_{\text{air}} + 0 \right] \times \frac{1}{\mu_0 a} = \frac{l_{\text{air}}}{\mu_0}$$

$$\Rightarrow NI_1 = \frac{l_{\text{air}}}{\mu_0} \quad \dots(i)$$

Case 2 :

$$\mu_r = 1000$$

mmf = same as in Case-1

$$\Rightarrow \text{mmf} = NI_1 = B_2(a) \left[l_{\text{air}} + \frac{l_{\text{core}}}{\mu_r} \right] \times \frac{1}{\mu_0 a}$$

Put NI_1 value from equation (i)

$$\Rightarrow \frac{l_{\text{air}}}{\mu_0} = B_2 \frac{1}{\mu_0} \left[l_{\text{air}} + \frac{l_{\text{core}}}{1000} \right]$$

$$\Rightarrow 0.2 = B_2 \left[0.2 + \frac{39.8}{1000} \right]$$

$$\Rightarrow B_2 = \frac{0.2}{0.2 + 0.0398} = \frac{0.2}{0.2398}$$

$$\Rightarrow B_2 = 0.834 \text{ Tesla}$$

42. A $0.1 \mu\text{F}$ capacitor charged to 100 V is discharged through a $1 \text{ k}\Omega$ resistor. The time in ms (round off to two decimal places) required for the voltage across the capacitor to drop to 1 V is ____.

Ans. (0.46)

Sol. Initially, $V(0) = 100 \text{ V}$

$$C = 0.1 \mu\text{F}$$

$$R = 1 \text{ k}\Omega$$

So, $V(t) = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}$

Here, $V(\infty) = 0$

and $\tau = RC$

$\tau = 1000 \times 0.1 \times 10^{-6}$

$\tau = 10^{-4}$ sec

So, $V(t) = 0 + [100 - 0]e^{-t/10^{-4}}$

$V(t) = 100 e^{-t/10^{-4}}$

Now, voltage drops to 1V,

$100 e^{-t/10^{-4}} = 1$


$e^{t/10^{-4}} = 100$

Taking log on both side

$\frac{t}{10^{-4}} = \ln(100)$
 $t = 4.6 \times 10^{-4}$ sec


$t = 0.46$ msec

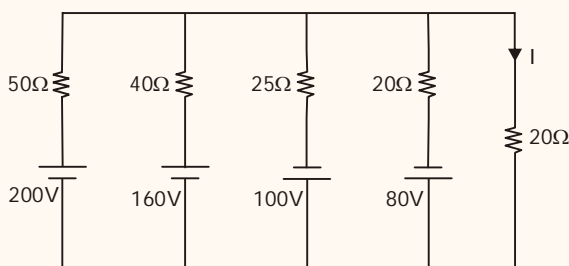43. The current I flowing in the circuit shown below in amperes is _____.



Ans. (0A)

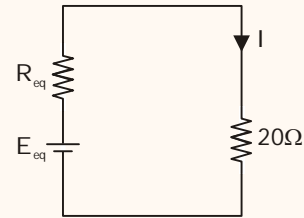Sol: According to Milliman's Theorem, the equivalent circuit of the given circuit is



Where, $E_{eq} = \frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3} + \frac{E_4}{R_4}$

$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

$$= \frac{200}{50} + \frac{160}{40} + \left(\frac{-100}{25}\right) + \left(\frac{-80}{20}\right)$$

$$= \frac{\frac{1}{50} + \frac{1}{40} + \frac{1}{25} + \frac{1}{20}}{\frac{1}{50} + \frac{1}{40} + \frac{1}{25} + \frac{1}{20}}$$

$$= \frac{4 + 4 - 4 - 4}{\left(\frac{1}{50} + \frac{1}{40} + \frac{1}{25} + \frac{1}{20}\right)}$$

$$= 0V$$

So, the current ' I ' flowing in the circuit is 0A.

44. A single-phase transformer of rating 25 kVA, supplies a 12 kW load at power factor of 0.6 lagging. The additional load at unity power factor in kW (round off to two decimal places) that may be added before this transformer exceeds its rated kVA is _____.

Ans. (7.20 kW)

Sol: 12 kW load at 0.6 pf

So, $S_{Load} = 12 + j16$

Now, P is added extra

$S_{Load} = (P + 12) + j16$

$|S_{Load}| = \sqrt{(P+12)^2 + (16)^2}$

$|S_{Load}| = 25$

$$\sqrt{(P+12)^2 + (16)^2} = 25$$

$$(P + 12)^2 + 16^2 = 625$$

$$(P + 12) = \pm 19.2$$

$$P = 7.2, -31.2$$

P is positive value

So, 7.20 kW extra load at unity pf can be added.

45. If $A = 2xi + 3yj + 4zk$ and $u = x^2 + y^2 + z^2$, then $\text{div}(uA)$ at $(1, 1, 1)$ is _____

Ans. (45)

Sol. $uA = (2x^3 + 2xy^2 + 2xz^2)\hat{i} + (3x^2y + 3y^3$

$$+ 3yz^2)\hat{j} + (4x^2z + 4y^2z + 4z^3)\hat{k}$$

$$\text{div}(uA) = \frac{d}{dx}(2x^3 + 2xy^2 + 2xz^2) + \frac{d}{dy}$$

$$(3x^2y + 3y^3 + 3yz^2) + \frac{d}{dz}(4x^2z + 4y^2z + 4z^3)$$

$$\text{div}(uA) = (6x^2 + 2y^2 + 2z^2) + (3x^2 + 9y^2 + 3z^2)$$

$$+ (4x^2 + 4y^2 + 12z^2); \text{ At } (1, 1, 1)$$

$$\text{div}(uA) = (6 + 2 + 2) + (3 + 9 + 3) + (4 + 4 + 12)$$

$$\boxed{\text{div}(uA) = 45}$$

46. A periodic function $f(t)$, with a period of 2π , is represented as its Fourier series,

$$f(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos nt + \sum_{n=1}^{\infty} b_n \sin nt$$

$$f(t) = \begin{cases} A \sin t, & 0 \leq t \leq \pi \\ 0, & \pi < t < 2\pi \end{cases}$$


the Fourier series coefficients a_1 and b_1 of $f(t)$ are

(a) $a_1 = 0; b_1 = \frac{A}{2}$ (b) $a_1 = \frac{A}{2}; b_1 = 0$

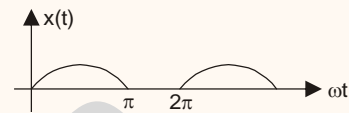(c) $a_1 = \frac{A}{\pi}; b_1 = 0$ (d) $a_1 = 0; b_1 = \frac{A}{\pi}$

Ans. (a)

Sol. $T = 2\pi \quad \omega = \frac{(2\pi)}{T} = 1$



$$a_n = \frac{2}{T} \int_0^T x(t) \cos n \omega t d(\omega t)$$

$$a_1 \Big|_{\omega=1}^{T=2\pi} = \frac{2}{2\pi} \int_0^{2\pi} A \sin t \cos t dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \sin t \cdot \cos t dt$$

$$a_1 = \frac{A}{\pi} \int_0^{\pi} \frac{\sin 2t}{2} = \frac{A}{2\pi} \left[\frac{-\cos 2t}{2} \right]_0^{\pi}$$

$$a_1 = \frac{A}{4\pi} [\cos 0 - \cos 2\pi] = 0$$

$$\boxed{a_1 = 0}$$

& $b_n = \frac{2}{T} \int_0^T x(t) \sin n \omega t d(\omega t)$

$$b_1 = \frac{2}{2\pi} \int_0^{\pi} A \sin t \cdot \sin t dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \sin^2 t dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \frac{(1 - \cos 2t)}{2} dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \left[\frac{1}{2} - \frac{\cos 2t}{2} \right] dt$$

$$= \frac{A}{\pi} \left[\frac{1}{2}(t) - \frac{\sin 2t}{4} \Big|_0^{\pi} \right]$$



IES MASTER

Institute for Engineers (IES/GATE/PSUs)

General Awareness Classroom Course for

SSC-JE 2019

Branches **CE** **ME** **EE**

- Classes by expert faculty in respective domains
- Well-structured study curriculum
- Test Series (online/offline) to determine level of preparation
- Learn how to read, decode, and deduce an answer
- Get rub-off with the best minds aspiring for SSC-JE
- Also, useful for State Engg Services/ PSUs/ State PSUs/ DMRC/ LMRC, etc.

Batch starting from

18th Feb, 2019

Course Duration

140-150 Hrs
(3-4 Hrs a day Monday to Friday)

Timing

05:30 to 08:30

Fee

₹ 6,800 + GST (18%)

Program includes

- All General Awareness topics as per SSC-JE syllabus
- 3 Full-length tests (Online/ Offline)


ENROLL NOW

F-126, Katwaria Sarai, **New Delhi**-110016 | Call +91 801 00 09955
Email: info@iesmaster.org

B-23 A, 5th Floor, Gaurav Deep Heights, Near Fortis Hospital
Sector 62, **Noida** - 201305 | Call 0120 415 1100
Email: info.noida@iesmaster.org | Website: iesmaster.org

$$b_1 = \frac{A}{\pi} \times \frac{\pi}{2} = \frac{A}{2}$$

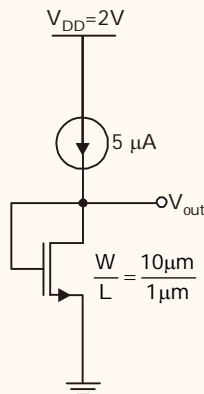47. The enhancement type MOSFET in the circuit below operates according to the square law, $\mu_n C_{ox} = 100 \mu A/V^2$, the threshold voltage (V_T) is 500 mV. Ignore channel length modulation. The output voltage V_{out} is



- (a) 500 mV (b) 2 V
(c) 100 mV (d) 600 mV

Ans. (d)

Sol. $I_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) [V_{gs} - V_T]^2$

$$5 \times 10^{-6} = \left(\frac{1}{2} \right) (100 \times 10^{-6}) (10) [V_{out} - 0.5]^2$$

$$[V_{out} - 0.5]^2 = 0.01$$

$$V_{out} - 0.5 = \pm 0.1$$


$$V_{out} = 0.6V \text{ and } 0.4 \text{ Volts}$$

So, $V_{out} = 600 \text{ mV}$

Option (d) is correct

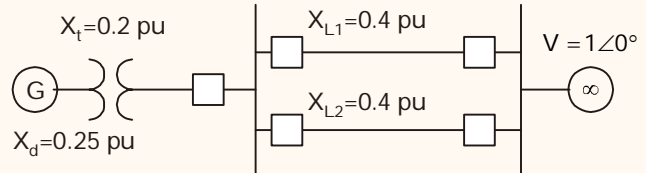
48. In the single machine infinite bus system shown below, the generator is delivering the real power of 0.8 pu and 0.8 power factor lagging to the

infinite bus. The power angle of the generator in degree (round off to one decimal place) is _____.



Ans. (20.51°)

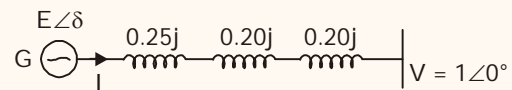Sol: Equivalent circuit of the network can be drawn as



Given, $P = 0.8 \text{ pu}$
 $\text{pf} = 0.8 \text{ pu (lagging)}$
 $V = 1 \text{ pu}$
 $P = VI \cos \phi$
 $0.8 = 1 \times I \times 0.8$

so, $I = 1 \text{ pu}$

$$I = 1 \angle -\cos^{-1}(0.8) \text{ pu}$$

Applying KVL to determine $E \angle \delta$ (generator voltage)

$$\bar{E} = \bar{V} + \bar{I} \bar{X}_{eq}$$

$$E \angle \delta = 1 \angle 0^\circ + [(0.25 + 0.2 + 0.2) \angle 90^\circ] [1 \angle -\cos^{-1}(0.8)]$$

$$E \angle \delta = 1 + 0.65 \angle 53.13^\circ$$

$$\Rightarrow E \angle \delta = 1.484 \angle 20.51^\circ$$

So, $\delta = 20.51^\circ$

49. The output expression for the Karnaugh map shown below is

	PQ			
	00	01	11	10
RS				
00	0	1	1	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

- (a) $Q\bar{R} + \bar{S}$ (b) $Q\bar{R} + S$
(c) $QR + \bar{S}$ (d) $QR + S$

Ans. (b)

Sol:


	PQ			
	00	01	11	10
RS				
00	0	1	1	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

$$f(P,Q,R,S) = S + Q\bar{R}$$

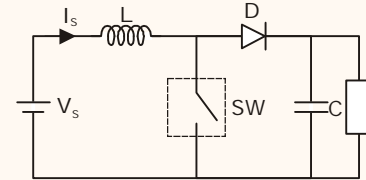50. In a DC-DC boost converter, the duty ratio is controlled to regulate the output voltage at 48V. The input DC voltage is 24 V. The output power is 120 W. The switching frequency is 50 kHz. Assume ideal components and a very large output filter capacitor. The converter operates at the boundary between continuous and discontinuous conduction mode. The value of the boost inductor (in μH) is _____

Ans. (24)

Sol. Given Boost converter
Output voltage
 $V_0 = 48 \text{ Volt}$
Input DC voltage
 $V_s = 24 \text{ volt}$
Output power
 $P_0 = 120 \text{ watt}$



(a)

$$(1 - \alpha) = \frac{V_s}{V_0} = \frac{24}{48} = \frac{1}{2}$$

$$\alpha = \frac{1}{2} = \text{Duty ratio}$$

Assuming losses switch/converter.

$$P_{in} = P_0$$

$$V_s I_s = 120$$

$$I_s = 120/24 = 5 \text{ Amp}$$

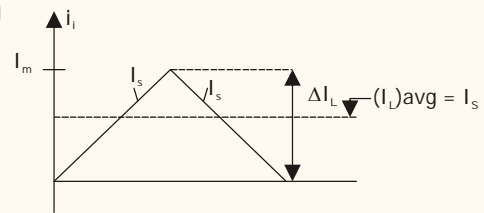


Fig. (b): Inductor current waveform.

At the boundary between continuous and discontinuous conduction mode.

$$I_{mn} = 0$$

$$I_{mn} = 0$$

$$I_{L_{avg}} = \frac{\Delta I_L}{2} = I_s$$

$$\Delta I_L = 2 \times 5 = 10 \text{ Amp}$$

During T_{ON} :-

$$V_s = V_L = L \frac{\Delta I_L}{T_{on}}$$

$$\Delta I_L = \frac{\alpha V_s}{f_{LC}}$$

$$L_C = \frac{\alpha V_s}{f \Delta I_L}$$

By putting all value

$$L_c = \frac{\frac{1}{2} \times 24}{50 \times 10^3 \times 10} = 24 \times 10^{-6} \text{ H}$$


$$L_c = 24 \mu\text{H}$$

Hence, value of the boost inductor is 24 μH

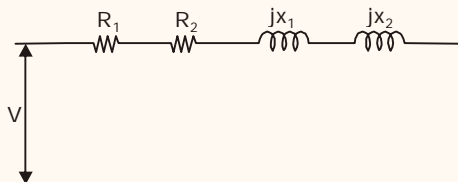51. A delta-connected, 3.7 kW, 400 V (line), 1 three-phase, 4-pole, 50-Hz squirrel-cage induction motor has the following equivalent circuit parameters per phase referred to the stator: $R_1 = 5.39 \Omega$, $R_2 = 5.72 \Omega$, $X_1 = X_2 = 8.22 \Omega$. Neglect shunt branch in the equivalent circuit. The starting line current in amperes (round off to two decimal places) when it is connected to a 100V (line), 10 Hz, three-phase AC source is _____.

Ans. (14.95)

- Sol.** A delta connected 3.1 KW, 400 V
For 50 Hz, 400V (line); given parameters are:
 $R_1 = 5.39 \Omega$, $R_2 = 5.72 \Omega$, $X_1 = X_2 = 8.22 \Omega$



At starting $V = 100\text{V}$, $f = 10 \text{ Hz}$

So, X_1 and X_2 changes due to frequency change

$$X_{1\text{new}} = X_{2\text{new}} = \left(\frac{10}{50}\right)(8.22)$$

$$X_{1\text{new}} = X_{2\text{new}} = 1.644 \Omega$$

So,
$$I_{\text{ph}} = \frac{V_{\text{ph}}}{Z}$$

$$I_{\text{ph}} = \frac{100}{(5.39 + 5.72) + j(1.644 + 1.644)}$$

$$I_{\text{ph}} = \frac{100}{(11.11 + j3.288)}$$

$$|I_{\text{ph}}| = 8.63 \text{ Amp}$$

But line to line current, $I_{L-L} = \sqrt{3} \times 8.63$
 $= 14.95 \text{ Amp}$

52. A three-phase 50 Hz, 400 kV transmission line is 300 km long. The line inductance is 1 mH/km per phase and the capacitance is 0.01 μF/km per phase. The line is under open circuit condition at the receiving end and energized with 400 kV at the sending end, the receiving end line voltage in kV (roundoff to two decimal places) will be _____.

Ans. (418.59)

Sol. Given,

3-phase, 50 Hz, 400 kV, 300 km long line

$$L = 1 \text{ mH/Km per phase}$$

$$C = 0.01 \mu\text{F / Km per phase}$$

Hence, $Z = j\omega L = j(2\pi \times 50 \times 10^{-3} \times 300)$

$$= j(30\pi)\Omega$$

and $Y = j\omega C$

$$= j(2\pi \times 50 \times 0.01 \times 10^{-6} \times 300)$$

$$= j(3\pi \times 10^{-4}) \text{ s}$$

Approximate ABCD parameters,

$$A = D = 1 + \frac{YZ}{2}, \quad B = Z \left[1 + \frac{YZ}{6} \right]$$

$$C = Y \left[1 + \frac{YZ}{6} \right]$$

$$\therefore V_s = AV_r + BI_r$$

for open circuit, $I_r = 0$

$$\Rightarrow V_{r0} = \frac{V_s}{A}$$

$$\Rightarrow V_{r0} = \frac{400}{1 + \frac{YZ}{2}} = \frac{400}{1 + \frac{(j30\pi)(j3\pi \times 10^{-4})}{2}}$$

$$= \frac{400}{1 - 0.044}$$

$$= \frac{400}{0.956} = 418.59 \text{ kV}$$

53. In a 132 kV system, the series inductance up to the point of circuit breaker location is 50 mH. The shunt capacitance at the circuit breaker terminal is $0.05 \mu\text{F}$. The critical value of the resistance in ohms required to be connected across the circuit breaker contacts which will give no transistor oscillation is _____.

Ans. (500)

Sol: Given data,

$$L = 50\text{mH}, C = 0.05\mu\text{F}$$

now, the critical resistance to avoid current chopping or transient oscillations will be given as,

$$R = \frac{1}{2} \sqrt{L/C}$$

$$R = \frac{1}{2} \sqrt{\frac{50 \times 10^{-3}}{0.05 \times 10^{-6}}}$$


$$= 500 \Omega$$

54. A 220 V DC shunt motor takes 3 A at no-load. It draws 25 A when running at full-load at 1500 rpm. The armature and shunt resistances are 0.5Ω and 220Ω , respectively. The no-load speeding rpm (round off to two decimal places) is _____.

Ans. (1579.33)

Sol. DC shunt motor
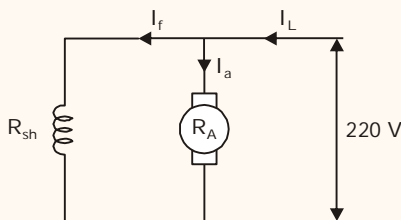
$$V_{dc} = 220 \text{ V}, R_a = 0.5 \Omega, R_{sh} = 220 \Omega$$



I_f = Field current

$$I_f = \frac{V_{dc}}{R_{sh}} = \frac{220}{220} = 1 \Omega$$

Case 1 : At No-load

$$I_L = 3\text{A}, I_f = 1\text{A}$$

$$I_{a0} = I_L - I_f = 2\text{A}$$

ϵ_{b0} = back emf at No-load

$$= V_{dc} - I_{a0} \cdot r_a$$

$$\epsilon_{b0} = 220 - (2 \times 0.5) = 219 \text{ V}$$

Case 2 : At Full-load

$$I_L = 25\text{A}, I_f = 1\text{A}, N_f = 1500 \text{ rpm}$$

$$I_{af} = 25 - 1 = 24 \text{ A}$$

$$\epsilon_{bf} = V_{dc} - I_{af} r_a = 220 - (24 \times 0.5)$$

$$\epsilon_{bf} = 208 \text{ V}$$

As we know, $\epsilon_b \propto N \phi \propto N$

[ϕ is constant, as V is constant]

$$\text{So, } \frac{N_0}{N_f} = \frac{\epsilon_{b0}}{\epsilon_{bf}}$$

$$N_0 = \text{No load speed} = 1500 \times \frac{219}{208}$$

$$N_0 = 1579.33 \text{ rpm}$$

55. Consider a state-variable model of a system

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\alpha & -2\beta \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \alpha \end{bmatrix} r$$

$$y = [1 \quad 0] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

where y is the output, and r is the input. The damping ratio ξ and the undamped natural frequency ω_n (rad/sec) of the system are given by

(a) $\xi = \sqrt{\beta}; \omega_n = \sqrt{\alpha}$

(b) $\xi = \frac{\sqrt{\alpha}}{\beta}; \omega_n = \sqrt{\beta}$

(c) $\xi = \frac{\beta}{\sqrt{\alpha}}; \omega_n = \sqrt{\alpha}$

(d) $\xi = \sqrt{\alpha}; \omega_n = \frac{\beta}{\sqrt{\alpha}}$



IES MASTER

Institute for Engineers (IES/GATE/PSUs)

Our Star Performers - UPSC ESE 2018

"Consistent Quality, Outstanding Results"

CONGRATULATIONS TO ALL

Civil Engineering

AIR 1 Vinay Prakash Sharma	AIR 2 Punit Singh	AIR 3 Praveen Kumar	AIR 4 Abhishek Bagla	AIR 5 Rishabh Dutt	AIR 6 Adarsh Sapre	AIR 7 Rohit Kumar Rajput	AIR 8 Vijaya Nandan Panjoly	AIR 9 Roopesh Mittal	AIR 10 Srichand Pooniya	AIR 11 Ashish Gupta	AIR 13 Ankur Gupta	AIR 14 Singh Jayadevdeep	AIR 15 Shashank Shekhar	AIR 16 Souvik Saha	AIR 17 Reema Agarwal	AIR 18 Arjun Dange			
AIR 19 Shubham Hebbath Nikam	AIR 20 Archit Jain	AIR 21 Prashant Kumar	AIR 22 Seema Shrivastava	AIR 23 Rajat Thenuka	AIR 24 Arun Kumar Sharma	AIR 25 Yadagni Shashank	AIR 27 Priyanshu Shukla	AIR 29 Pranjal Koshariwari	AIR 30 Suryash Dewvedi	AIR 31 Nikhil Virshi	AIR 32 Vishnu Kumar Maurya	AIR 33 Anshul Agarwal	AIR 34 Prakash Katiyar	AIR 35 Nitesh Goyal	AIR 36 Keshav Yemshi Krishna Reddy	AIR 37 Anadi Mittal	AIR 38 Ashish Rawat	AIR 39 Umesh Kumar	AIR 40 Shyam Singh
AIR 41 Saranish Sharma	AIR 42 Ajay Shrivastava	AIR 43 Yogita Meena	AIR 44 Prabok Kumar	AIR 47 Sanjay Unawat	AIR 48 Rajat	AIR 49 Shivan Tyagi	AIR 50 Yashu Chohan Dabohau	AIR 51 Anil Kumar Gupta	AIR 52 Ambareesh Singh	AIR 53 Atul Dwivedi	AIR 55 Yogesh Kumar Gupta	AIR 56 Chetan Kumawat	AIR 57 Sandeep	AIR 58 Unkash Shukla	AIR 60 Vikram Garg	AIR 61 Abuzar Gaffari	AIR 62 Madhukant Goyal	AIR 63 Bansid Hemditya	AIR 64 Sagar Ramesh
AIR 65 Vishal Anand	AIR 66 Salunavath Nath	AIR 67 Divyansh Singh	AIR 68 Sunil Sagotra	AIR 71 Ramesh Vikram Singh	AIR 72 Vidit Singh	AIR 73 Rishabh Vijayvergiya	AIR 74 Lovya Agarwal	AIR 75 Anshul Goyal	AIR 76 Md Arsal Nayaz	AIR 77 Tarun Singh	AIR 78 Rajesh Kumawat	AIR 79 Gaurav Tiwari	AIR 80 Suraj Jatwal	AIR 81 Pankaj Kumar	AIR 82 Rakesh Ranjan	AIR 83 Dharmendra Chaurhan	AIR 84 Chandra Sakhar	AIR 85 Prabok Kumar Meena	AIR 87 Vivak Kumar
AIR 88 Hemant Kumar	AIR 89 Ashish Dubey	AIR 90 Gaurav Agarwal	AIR 91 Rohit Mehta	AIR 92 Kunwar Shubham Patel	AIR 94 Suman Kumar	AIR 95 Saurabh Kumar	AIR 96 Akshat Prabh Soni	AIR 97 Gaurav Joshi	AIR 98 Dhawal Kataria	AIR 99 Abhinav Kumar	AIR 100 Anjali Kumar Maurya	AIR 101 Varid Gupta	AIR 102 Rajesh Kumar	AIR 103 Sajal Mittal	AIR 104 Lalit Meena	AIR 105 Premraj Singh	AIR 106 Aman Hasdika	AIR 107 Prasant Kumar	
AIR 108 Abhishek Meena	AIR 109 Pranjal Gupta	AIR 110 Vaishali Yadav	AIR 111 Swami Prashant Rastogi	AIR 113 Abhimanyu	AIR 114 Sangani Prithvi	AIR 115 Khem Chand Goyal	AIR 116 Reena Panwar	AIR 117 Ashok Jangid	AIR 118 Kathe Sai Charan	AIR 122 Shubhashu Chaurasiya	AIR 123 Rahul Priyadarshi	AIR 124 Rajeev Choudhary	AIR 125 Anil Kumar Kuzhawa	AIR 126 Puspendra Kumar Khattara	AIR 128 Ashok Kumar	AIR 129 Bharat Anand	AIR 130 Lakshendu Bodayher Jena	AIR 131 Yogendra Meena	
AIR 134 Dharmar	AIR 135 Champakpotti Rajbangshi	AIR 136 Surentra Kumar Meena	AIR 139 Gaurav Kumar	AIR 140 Rohit Raj	AIR 142 Sandeep Bhaskar	AIR 143 Shashank Kumar Maurya	AIR 144 Nisha Singh	AIR 145 Pushpendra Singh	AIR 148 Vivik Kumar Shukla	AIR 149 Sagar Singh	AIR 150 Divyanshu Rao	AIR 151 Nareesh Baniwa	AIR 152 Pankaj Prasad	AIR 153 Lokendra Kumar Singh	AIR 155 Umash Kumar	AIR 156 Anika Anand Upadhyay	AIR 157 Pradeep Singh	AIR 159 Aksh Kumar	

Mechanical Engineering

AIR 2 ME Chirag Singla	AIR 15 Shubham Tyagi	AIR 18 Vikash Shukla	AIR 21 Shubham Pachauri	AIR 24 Gaurav Jindal	AIR 29 Jayant Raj Saurav	AIR 39 Pradeep Kumar Singh	AIR 51 Patil Ketan Rajendra	AIR 52 Atulya Jyoti	AIR 54 Arpit	AIR 56 Priyam Agarwal	AIR 60 Saurabh Kumar	AIR 62 Saurabh Dubey	AIR 63 Ashutosh Kumar	
AIR 65 Chandan Kumar	AIR 66 Mithun Kumar	AIR 74 Shallendra Kumar Mishra	AIR 78 Shivam Gupta	AIR 82 Piyush Lawania	AIR 90 Rohit Singh	AIR 93 Krishnaveer Sharma	AIR 96 Dhirendra Choudhary	AIR 98 Niranjan Naghnath Ubale	AIR 104 Sanjay Bapat	AIR 107 Rishabh Dev Tiwari	AIR 108 Rajat Kumar	AIR 118 Shashank Singh	AIR 123 Padigata Ranga Vinod	AIR 128 Sumit Katoch

Electrical Engineering

AIR 3 EE Srijan Varma	AIR 8 Manne Ravi Teja	AIR 9 Souvik Deb Roy	AIR 10 Milan Krishna	AIR 12 Kishna Kumar Gupta	AIR 13 Prakash Tiwari	AIR 16 Pradhuman Deola	AIR 17 Deepak Singh Chauhan	AIR 19 Piyush Kumar Gupta	AIR 26 Pawan Kumar	AIR 36 Ankit Tayal	AIR 37 Anil Shivastava	AIR 38 Prakash Chandrakar	AIR 43 Deependra Marwar	AIR 72 Prince Yadav	AIR 82 Shobha Devi	AIR 96 Jitendra Khatri	AIR 101 Munesh Chand Meena	AIR 108 Disha Agarwal
---------------------------------	---------------------------------	--------------------------------	--------------------------------	-------------------------------------	---------------------------------	----------------------------------	---------------------------------------	-------------------------------------	------------------------------	------------------------------	----------------------------------	-------------------------------------	-----------------------------------	-------------------------------	------------------------------	----------------------------------	--------------------------------------	---------------------------------

Electronics & Telecommunication Engineering

AIR 4 Shashank Shekhar	AIR 5 Jagjit Singh	AIR 12 Narendra Kumar Gupta	AIR 38 Varsha Sharma	AIR 39 Satish Singh	AIR 41 Sutirtho Borral	AIR 44 Aishwary Anand	AIR 46 Patil Rohan Ramraj	AIR 48 Prabhat Panjoly	AIR 48 Danish Aggarwal	AIR 56 Priyanka Somani	AIR 69 Kavya Palfwal	AIR 73 T.Thubasidhar	AIR 76 Rishabh Kumar Dhaivat	AIR 94 Madhu Timan	AIR 104 Ranjan Kumar
----------------------------------	------------------------------	---------------------------------------	--------------------------------	-------------------------------	----------------------------------	---------------------------------	-------------------------------------	----------------------------------	----------------------------------	----------------------------------	--------------------------------	--------------------------------	--	------------------------------	--------------------------------





Ans. (c)

Sol.

Given data,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\alpha & 2\beta \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \alpha \end{bmatrix} r$$

$$y = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

Comparing these state equation with

$$\dot{x} = Ax + Bu$$

$$y = Cx + Du$$

One gets,

$$A = \begin{bmatrix} 0 & 1 \\ -\alpha & -2\beta \end{bmatrix}, B = \begin{bmatrix} 0 \\ \alpha \end{bmatrix}$$

$$C = \begin{bmatrix} 1 & 0 \end{bmatrix}, D = 0$$

Now transfer function is given as,

$$T.F = C[SI - A]^{-1} B + D$$

$$\therefore [SI - A] = \begin{bmatrix} s & -1 \\ \alpha & s+2\beta \end{bmatrix}$$

$$\therefore [SI - A]^{-1} = \frac{1}{(s^2 + 2\beta s + \alpha)} \begin{bmatrix} s+2\beta & 1 \\ -\alpha & s \end{bmatrix}$$

Now,

$$C[SI - A]^{-1} \cdot B$$

$$= \begin{bmatrix} 1 & 0 \end{bmatrix} \times \frac{1}{(s^2 + 2\beta s + \alpha)} \begin{bmatrix} s+2\beta & 1 \\ -\alpha & s \end{bmatrix} \times \begin{bmatrix} 0 \\ \alpha \end{bmatrix}$$

$$= \frac{\alpha}{s^2 + 2\beta s + \alpha}$$

Hence, characteristics equation is,

$$s^2 + 2\beta s + \alpha = 0$$

Comparing the characteristics equation with

$$s^2 + 2\xi\omega_n s + \omega_n^2 = 0$$

One gets,

$$\omega_n = \sqrt{\alpha}, 2\xi\omega_n = 2\beta$$

$$\Rightarrow \xi = \frac{\beta}{\sqrt{\alpha}}$$