

ANSWERS

1. 1 (c) 1. 2 (d) 1. 3 (d) 1. 4 (b) 1. 5 (c) 1. 6 (d) 1. 7 (c) 1. 8 (b) 1. 9 (c) 1. 10 (a)
 1. 11 (b) 1. 12 (d) 1. 13 (c) 1. 14 (d) 1. 15 (a) 1. 16 (c) 1. 17 (b) 1. 18 (c) 1. 19 (a)

EXPLANATIONS


1.3 Voltage across the capacitor

$$= \frac{200}{\sqrt{R^2 + (X_L - X_C)^2}} \times (-jX_C)$$

$$= \frac{200}{\sqrt{100 + (20 - 20)^2}} \times (-j20)$$

$$= -j400$$

$$= 400 \angle -90^\circ \text{ V}$$

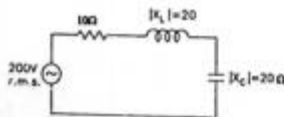

1.4 In the Laplace domain,

$$V_o(s) = \frac{V_i(s)}{R + \frac{1}{Cs}} \times R$$

$$= \frac{V_i(s) RCs}{RCs + 1}$$


$$V_i(t) = 100t u(t)$$

and $V_i(s) = \frac{100}{s^2}$

Hence, $V_o(s) = \frac{100}{s^2} \left[\frac{5 \times 10^{-3} \times 10^{-6} s}{5 \times 10^{-3} \times 4 \times 10^{-6} s + 1} \right]$

$$= \frac{2}{s(2 \times 10^{-2}s + 1)} \approx \frac{2}{s}$$

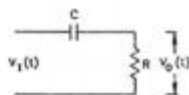$V_o(t) = 2u(t)$
 \therefore Maximum voltage = 2 V



1.5 $H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

$$H(j\omega) = \frac{\omega_n^2}{-\omega^2 + 2\zeta\omega_n j\omega + \omega_n^2}$$

$$|H(j\omega)| = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + (2\zeta\omega_n\omega)^2}}$$

$$|H(j0)| = 1$$

If ω_c is the 3-dB frequency, then

$$|H(j\omega_c)| = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega_c^2)^2 + (2\zeta\omega_n\omega_c)^2}} = 0.707$$