



STANDARD	SUBJECT: PHYSICS	MEDIUM: ENGLISH	DATE: 4/11/2020
10	MOTION	WORKSHEET NO : 3.13	https://www.youtube.com/watch?v=IzNRMHMttag

1. Correct any of the following statements regarding the household electrification circuit.
 - i. The power line to the house is first connected to the main switch and then to the electrical equipment through the watt hour meter and fuse.
 - ii. Even if the main fuse in a household circuit melts, there will still be current flowing to the main switch.
 - iii. Safety fuses are installed in household circuits on phase lines
2. What are the standard color code to use for phase, Neutral, and Earth lines in a household electrical circuit.
3.
 - I. In what way should electrical appliances be included in household electrification circuits? Series / parallel
 - ii. What is the voltage experienced to such electrical appliances in according to the present electricity distribution system?
 - iii. Three bulbs with different power ratings are included in such a household circuit. In the event of a bulb failure with high power rating Will the other two bulbs light up when the switch is turned on?
4. Which of the following is the use of a watt hour meter?
 - a) Measure the current through the mains
 - b) Measure the energy loss of electrical equipment
 - c) Measure total power in the circuit
 - d) Estimate household energy consumption
5. Fuses, MCB, ELCB etc. are used to ensure safety in the home circuit.
 - I) What are the differences between a safety fuse and an MCB?
 - ii) What are the advantages of MCB over Fuse?
 - iii) Complete MCB, ELCB, RCCB