

**CHAPTER 7****ALTERNATING CURRENT**

(Prepared By Ayyappan C, HSST, GMRHSS Kasaragod)

**AC Voltage and AC Current**


- A voltage that varies like a sine function with time is called *alternating voltage (ac voltage)*.
- The electric current whose magnitude changes with time and direction reverses periodically is called the *alternating current (ac current)*.

**Advantages of AC:**

- Easily stepped up or stepped down using transformer
- Can be regulated using choke coil without loss of energy
- Easily converted in to dc using rectifier (Pn - diode)
- Can be transmitted over distant places
- Production of ac is more economical

**Disadvantages of ac**

- Cannot used for electroplating - Polarity of ac changes
- ac is more dangerous
- It can't store for longer time

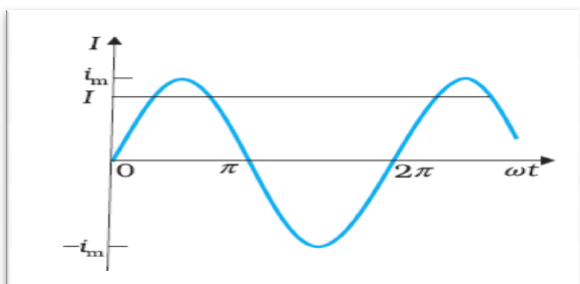**Representation of ac**

- An ac voltage can be represented as

$$v = v_m \sin \omega t$$

- v- instantaneous value of voltage ,  
v<sub>m</sub>- peak value of voltage, ω - Angular frequency.

**RMS Value (effective current)**

- r.m.s. value of a.c. is the d.c. equivalent which produces the same amount of heat energy in same time as that of an a.c.
- It is denoted by I<sub>rms</sub> or I.
- Relation between r.m.s. value and peak value is


$$I_{rms} = \frac{i_m}{\sqrt{2}}$$

- The r.m.s voltage is given by


$$V_{rms} = \frac{v_m}{\sqrt{2}}$$

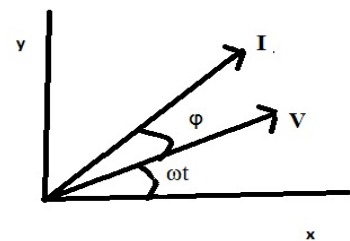**Phasors**

- A phasor is a vector which rotates about the origin with angular speed ω.
- The vertical components of phasors V and I represent the sinusoidally varying quantities v and i.
- The magnitudes of phasors V and I represent the peak values v<sub>m</sub> and i<sub>m</sub>



- The diagram representing alternating voltage and current (phasors) as the rotating vectors along with the phase angle between them is called phasor diagram.

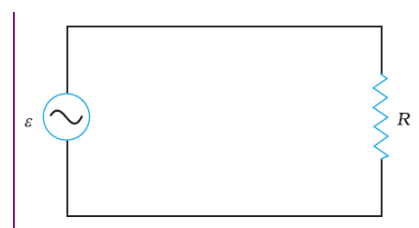**AC Voltage applied to a Resistor**

www.rvgirls.com

- The ac voltage applied to the resistor is

$$v = v_m \sin \omega t$$

- Applying Kirchoff's loop rule

$$v_m \sin \omega t = iR$$

$$i = \frac{v_m}{R} \sin \omega t$$




- Since R is a constant, we can write this equation as

$$i = i_m \sin \omega t$$


- Where peak value of current is

$$i_m = \frac{v_m}{R}$$

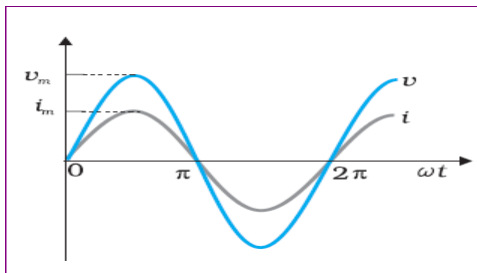- Thus when ac is passed through a resistor the voltage and current are in phase with each other.



Phasor diagram

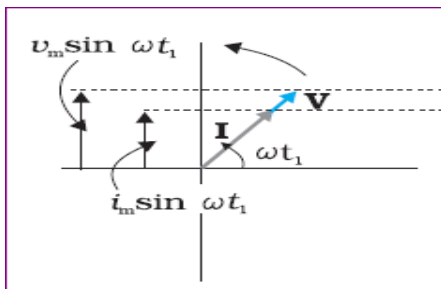

Instantaneous power

- The instantaneous power dissipated in the resistor is

$$p = i^2 R = i_m^2 R \sin^2 \omega t$$

Average power

- The average value of p over a cycle is

$$\bar{p} = \langle i^2 R \rangle = \langle i_m^2 R \sin^2 \omega t \rangle$$

or

$$\bar{p} = i_m^2 R \langle \sin^2 \omega t \rangle$$

- Using the trigonometric identity,

$$\sin^2 \omega t = 1/2 (1 - \cos 2\omega t)$$

$$\langle \sin^2 \omega t \rangle = (1/2) (1 - \langle \cos 2\omega t \rangle)$$

- Since  $\langle \cos 2\omega t \rangle = 0$

$$\langle \sin^2 \omega t \rangle = \frac{1}{2}$$

- Thus

$$\bar{p} = \frac{1}{2} i_m^2 R$$


- In terms of r.m.s value

$$P = \bar{p} = \frac{1}{2} i_m^2 R = I^2 R$$

- Or

$$P = V^2 / R = IV \quad (\text{since } V = IR)$$

AC VOLTAGE APPLIED TO AN INDUCTOR

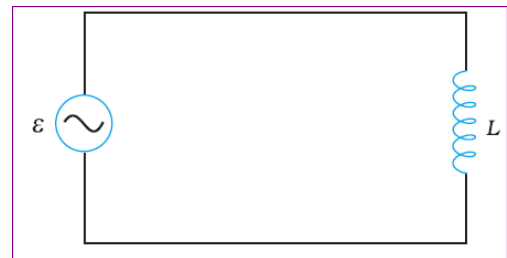

- Let the voltage across the source be

$$v = v_m \sin \omega t$$

- Using the Kirchoff's loop rule

$$v - L \frac{di}{dt} = 0$$

- Where L is the self-inductance

- Thus

$$\frac{di}{dt} = \frac{v}{L} = \frac{v_m}{L} \sin \omega t$$

- Integrating

$$\int \frac{di}{dt} dt = \frac{v_m}{L} \int \sin(\omega t) dt$$

$$i = -\frac{v_m}{\omega L} \cos(\omega t) + \text{constant}$$

- Since the current is oscillating, the constant of integration is zero.
- Using

$$-\cos(\omega t) = \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$i = i_m \sin\left(\omega t - \frac{\pi}{2}\right)$$

- Where

$$i_m = \frac{v_m}{\omega L}$$

- Or

$$i_m = \frac{v_m}{X_L}$$

- Where  $X_L$ - inductive reactance

### Inductive reactance ( $X_L$ )

- The resistance offered by the inductor to an ac through it is called inductive reactance.
- It is given by

$$X_L = \omega L$$

- The dimension of inductive reactance is the same as that of resistance and its SI unit is ohm ( $\Omega$ ).
- The inductive reactance is directly proportional to the inductance and to the frequency of the current.

### Phasor Diagram


- We have the source voltage

$$v = v_m \sin \omega t$$

- The current

$$i = i_m \sin\left(\omega t - \frac{\pi}{2}\right)$$

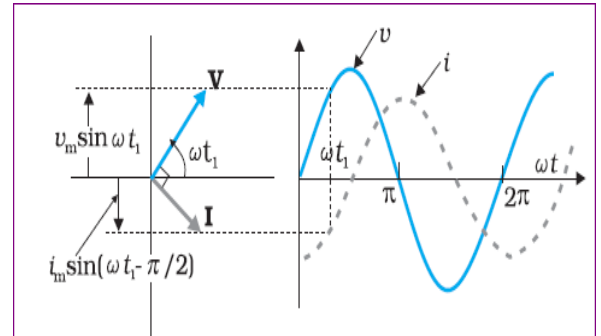- Thus a comparison of equations for the source voltage and the current in an inductor shows that the current lags the voltage by  $\pi/2$  or one-quarter (1/4) cycle.



### Instantaneous power

- The instantaneous power supplied to the inductor is

$$\begin{aligned} p_L &= i v = i_m \sin\left(\omega t - \frac{\pi}{2}\right) \times v_m \sin(\omega t) \\ &= -i_m v_m \cos(\omega t) \sin(\omega t) \\ &= -\frac{i_m v_m}{2} \sin(2\omega t) \end{aligned}$$

### Average power


- The average power over a complete cycle in an inductor is

$$\begin{aligned} P_L &= \left\langle -\frac{i_m v_m}{2} \sin(2\omega t) \right\rangle \\ &= -\frac{i_m v_m}{2} \langle \sin(2\omega t) \rangle = 0, \end{aligned}$$

- since the average of  $\sin(2\omega t)$  over a complete cycle is zero.
- Thus, the *average power supplied to an inductor over one complete cycle is zero.*



**AC VOLTAGE APPLIED TO A CAPACITOR**

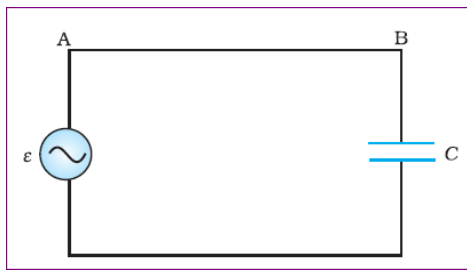

- A capacitor in a dc circuit will limit or oppose the current as it charges.
- When the capacitor is connected to an ac source, it limits or regulates the current, but does not completely prevent the flow of charge.
- Let the applied voltage be

$$v = v_m \sin \omega t$$

- The instantaneous voltage  $v$  across the capacitor is

$$v = \frac{q}{C}$$

- Where  $q$  is the charge on the capacitor.
- Using the Kirchhoff's loop rule

$$v_m \sin \omega t = \frac{q}{C}$$

- Therefore

$$i = \frac{d}{dt}(v_m C \sin \omega t) = \omega C v_m \cos(\omega t)$$

- Using the relation

$$\cos(\omega t) = \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$i = i_m \sin\left(\omega t + \frac{\pi}{2}\right)$$

- Where

$$i_m = \frac{v_m}{(1 / \omega C)}$$

- Or

$$i_m = \frac{v_m}{X_C}$$

- Where  $X_C$  – capacitive reactance

**Capacitive Reactance**

- It is the resistance offered by the capacitor to an ac current through it.
- The dimension of capacitive reactance is the same as that of resistance and its SI unit is ohm ( $\Omega$ ).

**Phasor Diagram**


- The applied voltage is

$$v = v_m \sin \omega t$$

- The current is

$$i = i_m \sin\left(\omega t + \frac{\pi}{2}\right)$$

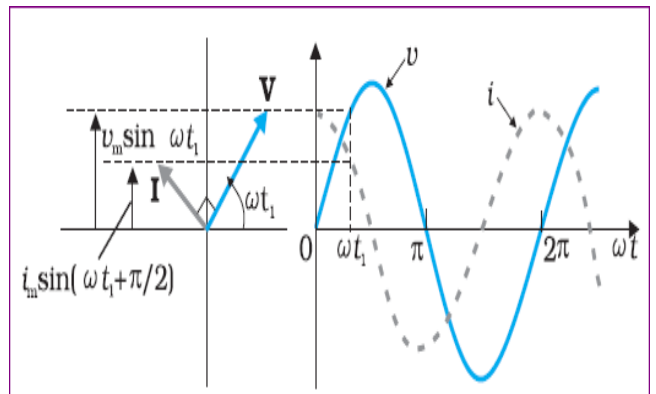- Thus the current leads voltage by  $\pi/2$ .



**Instantaneous power**

- The instantaneous power supplied to the capacitor is

$$\begin{aligned} p_c &= i v = i_m \cos(\omega t) v_m \sin(\omega t) \\ &= i_m v_m \cos(\omega t) \sin(\omega t) \\ &= \frac{i_m v_m}{2} \sin(2\omega t) \end{aligned}$$

**Average power**

- The average power is given by



$$P_C = \left\langle \frac{i_m v_m}{2} \sin(2\omega t) \right\rangle = \frac{i_m v_m}{2} \langle \sin(2\omega t) \rangle = 0$$


- Thus the average power over a cycle when an ac passed through a capacitor is zero.

### TRANSFORMER

- It is a device used to change alternating voltage.
- It works using the principle of mutual induction.
- Works only in ac
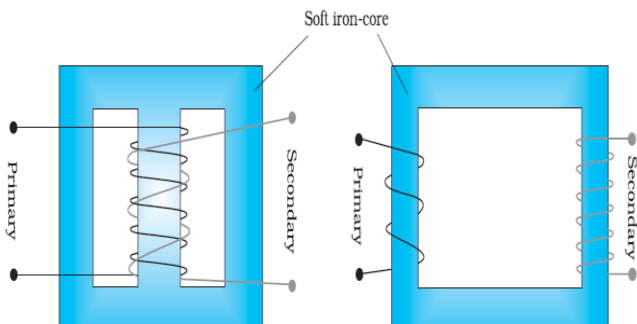
### Construction

- A transformer consists of two sets of coils, insulated from each other.
- They are wound on a soft-iron core, either one on top of the other.
- One of the coils called the **primary coil** has  $N_p$  turns.
- The other coil is called the **secondary coil**; it has  $N_s$  turns.
- The primary coil is the **input coil** and the secondary coil is the **output coil** of the transformer.



### Theory / Transformer Equation

- Let  $\phi$  be the flux in each turn in the core at time  $t$  due to current in the primary when a voltage  $v_p$  is applied to it.
- The induced emf or voltage  $\varepsilon_s$  in the secondary with  $N_s$  turns is

$$\varepsilon_s = -N_s \frac{d\phi}{dt}$$

- The alternating flux  $\phi$  also induces an emf, called back emf in the primary.

$$\varepsilon_p = -N_p \frac{d\phi}{dt}$$

- Assuming

$$\varepsilon_p = v_p \quad \text{and} \quad \varepsilon_s = v_s$$

- Therefore

$$v_s = -N_s \frac{d\phi}{dt}$$

$$v_p = -N_p \frac{d\phi}{dt}$$

- Thus

$$\frac{v_s}{v_p} = \frac{N_s}{N_p}$$

- For an ideal transformer input power and output power are equal, therefore

$$i_p v_p = i_s v_s$$

- Thus

$$\frac{i_p}{i_s} = \frac{v_s}{v_p} = \frac{N_s}{N_p}$$

- This is the transformer equation.


### Types of Transformers

#### Step-up transformer

- We have


$$V_s = \left( \frac{N_s}{N_p} \right) V_p \quad \text{and} \quad I_s = \left( \frac{N_p}{N_s} \right) I_p$$

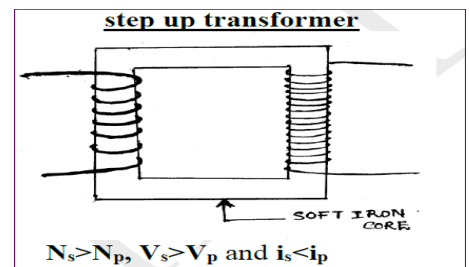- Thus, if the secondary coil has a greater number of turns than the primary ( $N_s > N_p$ ), **the voltage is stepped up** ( $V_s > V_p$ ). This type of arrangement is called a **step-up transformer**.
- In step up transformer, there is less current in the secondary than in the primary ( $I_s < I_p$ )


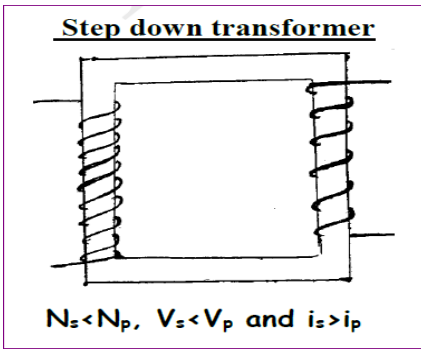
#### Step-down transformer

- In a step-down transformer the secondary coil has less turns than the primary ( $N_s < N_p$ ).
- Here  $V_s < V_p$  and  $I_s > I_p$ . That is, the voltage is stepped down, or reduced, and the current is increased.



**Working**

- When an alternating voltage is applied to the primary, the resulting current produces an alternating magnetic flux which links the secondary and induces an emf in it.
- The value of the emf depends on the number of turns in the secondary.

**Efficiency of a transformer**

- The efficiency of a transformer is given by

$$\text{Efficiency, } \eta = \frac{\text{output power}}{\text{input power}}$$

**Energy loss in transformers**

**Copper Loss**

- As the current flows through the primary and secondary copper wires, electric energy is wasted in the form of heat.
- This is minimised by using thick wire.

**Eddy current Loss (Iron Loss)**

- The eddy currents produced in the soft iron core of the transformer produce heating.
- Thus electric energy is wasted in the form of heat.
- The effect is reduced by having a laminated core.

**Magnetic flux leakage**

- The entire magnetic flux produced by the primary coil may not be available to the secondary coil.
- Thus some energy is wasted.
- It can be reduced by winding the primary and secondary coils one over the other.

**Hysteresis Loss**

- Since the soft iron core is subjected to continuous cycles of magnetization, the core gets heated due to hysteresis.

- Minimised by using a magnetic material which has a low hysteresis loss.

**Uses of a transformer**

- The large scale transmission and distribution of electrical energy over long distances is done with the use of transformers.
- The voltage output of the generator is stepped-up. It is then transmitted over long distances to an area sub-station near the consumers. There the voltage is stepped down.
- It is further stepped down at distributing sub-stations and utility poles before a power supply of 240 V reaches our homes.

\*\*\*\*\*



