

## Ohm's Law II

**AIM:** To verify the laws of combination of Resistances.

**APPARATUS:** Cells, Ammeter, Voltmeter, Rheostat, Key, Resistances, Bread Board, Connecting wires etc

**THEORY:** At constant temperature, the current passing through the conductor is directly proportional to the potential difference across the conductor.


That is  $V \propto I$  or  $\frac{V}{I} = R$  the resistance of the conductor.

When two resistances  $R_1$  and  $R_2$  connected in series, the effective resistance  $R_s = R_1 + R_2$ .

When they are connected in parallel, the effective resistance is

given by  $\frac{1}{R_s} = \frac{1}{R_1} + \frac{1}{R_2}$

or  $R_p = \frac{R_1 R_2}{R_1 + R_2}$

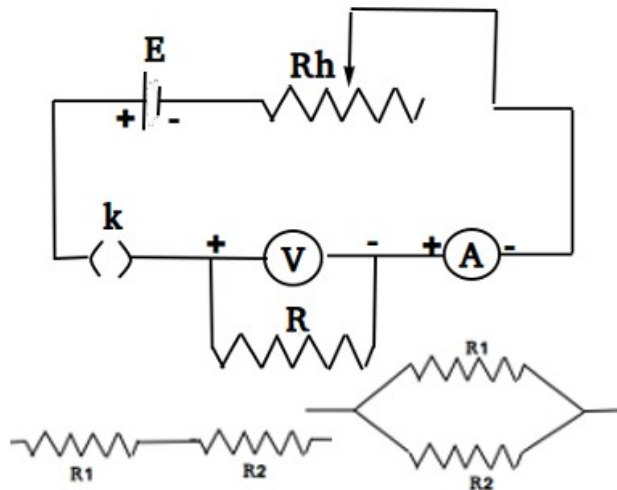

**OBSERVATIONS:**

Least Count of the ammeter =                      A

Least Count of the voltmeter =                      V

Resistance	Trial No	Ammeter Reading (I) Ampere	Voltmeter Reading (V) Volts	$R = \frac{V}{I}$ $\Omega$	Mean R $\Omega$
$R_1$	1				$R_1 =$
	2				
	3				
	4				
$R_2$	1				$R_2 =$
	2				
	3				
	4				
$R_1$ and $R_2$ in Series	1				$R_s =$
	2				
	3				
	4				
$R_1$ and $R_2$ in Parallel	1				$R_p =$
	2				
	3				
	4				

**CALCULATIONS:**

$$R_1 = \quad \quad \quad \Omega$$

$$R_2 = \quad \quad \quad \Omega$$

$$R_s =$$

$$R_s = R_1 + R_2 = \quad \quad \quad = \quad \quad \quad \Omega$$

$$R_p = \quad \quad \quad \Omega$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \quad \quad \quad = \quad \quad \quad \Omega$$

**RESULT:**

The laws of combination of Resistances in Series and Parallel are verified.