

Experiment No:

Date:


## Potentiometer I

**Aim:**

To compare the emf's of two primary cells using Potentiometer

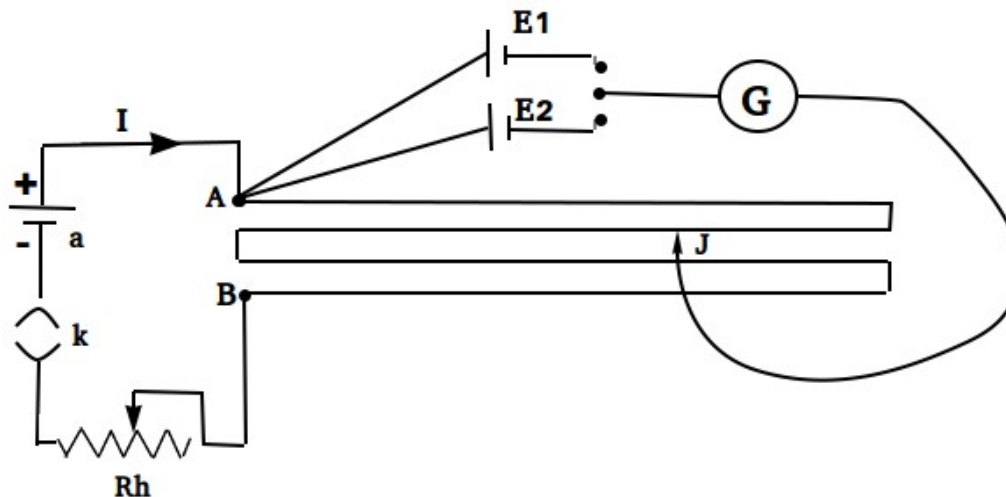**Apparatus:**

Potentiometer, Accumulator, Daniel Cell, Leclanche Cell, Rheostat, Key, Jockey, Connecting wires etc.



**Theory:**

When a steady current flows through a resistance wire, the potential difference developed in the wire is directly proportional to the length of the wire,

If  $E_1$  and  $E_2$  are the emf's of a Daniel Cell and Leclanche Cell and  $l_1$  and  $l_2$  are their respective balancing lengths, then

$$E_1 \propto l_1 \text{ and } E_2 \propto l_2$$

that is  $\frac{E_1}{E_2} = \frac{l_1}{l_2}$

**Observations:**

Sl No	Balancing Length for (cm)		$\frac{E_1}{E_2} = \frac{l_1}{l_2}$
	Daniel Cell ( $E_1$ )	Leclanche Cell	
1			
2			
3			
4			
5			
6			
7			

The Ratio of emf's =

**Result:**

The Ratio of emf's =