

Experiment No:

Date:


## Potentiometer II

**Aim:**

To determine the internal resistance of a primary cells using Potentiometer

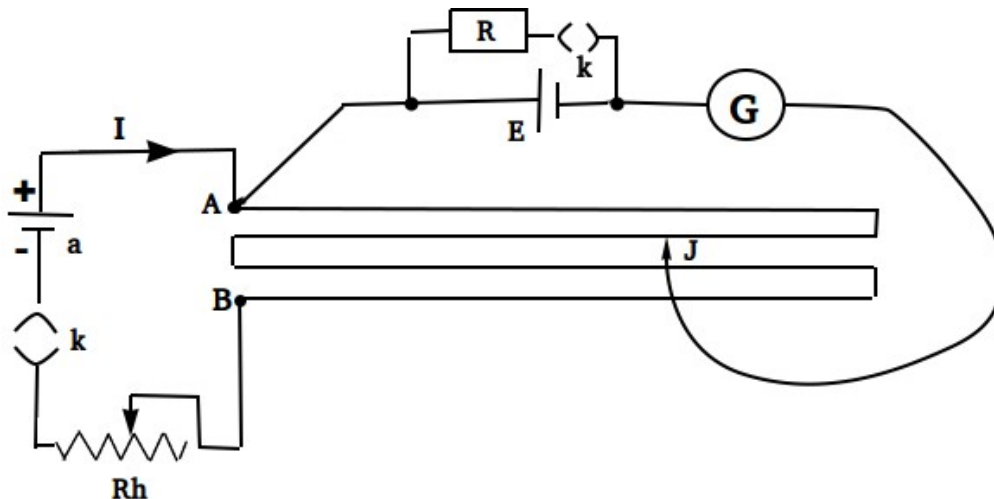**Apparatus:**

Potentiometer, Accumulator, Daniel Cell/Leclanche Cell, Rheostat, Key, Jockey, Connecting wires etc.



**Theory:**

When a steady current flows through a resistance wire, the potential difference developed in the wire is directly proportional to the length of the wire,

For an open circuit, the emf  $E \propto l_1$

If the circuit is closed with a resistance R, the Potential Difference  $V \propto l_2$

That is  $\frac{E}{V} = \frac{l_1}{l_2}$

We have  $E = V + Ir$

Where  $I$  is the current and  $r$  is the internal resistance of the cell.

Then we have internal resistance as  $r = \frac{l_1 - l_2}{l_2} R$

**Observations:**

Sl No	External Resistance (R) $\Omega$	Balancing Length when key (cm)		$r = \frac{l_1 - l_2}{l_2} R \quad \Omega$
		Open ( $l_1$ )	Closed ( $l_2$ )	
1				
2				
3				
4				
5				
6				
7				

**Result:**

The Internal resistance of the cell increases with External Resistance.