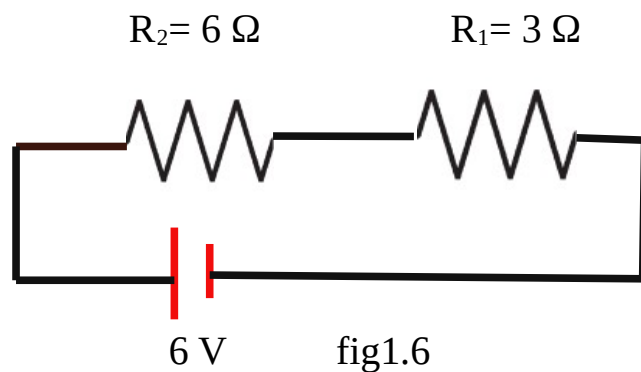


PHYSICS - X-PART-8 CLASS 08

Arrangement of Resistors in Circuits1. Series Connection

When a circuit is completed by connecting the resistors one after the other, it is called series connection.



$$\text{Effective resistance, } R = R_1 + R_2$$

* Effective resistance is the sum of the resistance of all the resistors when they are connected in series.

Ex. 1 (Fig.1.6)

$$R_1 = 3 \Omega$$

$$R_2 = 6 \Omega$$

Effective resistance, $R = R_1 + R_2$

$$R = 3 \Omega + 6 \Omega$$

$$R = 9 \Omega$$

2. If 2Ω , 4Ω , 6Ω resistors are connected in series. Calculate the effective resistance.

$$R_1 = 2 \Omega$$

$$R_2 = 4 \Omega$$

$$R_3 = 6 \Omega$$

Effective resistance, $R = R_1 + R_2 + R_3$

$$R = 2 \Omega + 4 \Omega + 6 \Omega = 12 \Omega$$

When resistors are connected in series,

- * The potential difference gets divided
- * The current through each resistor will be the same.
- * The effective resistance increases.

Assignment

1. What is the current if $4\ \Omega$ and $2\ \Omega$ resistors are connected in series and $6\ \text{V}$ potential difference is applied?