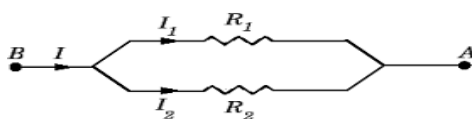


Physics Class Notes

[Click Here To Watch The Video](#)

Parallel Connection

Parallel connection of resistors is shown below



The effective resistance of the parallel combination, $1/R = 1/R_1 + 1/R_2$
or $R = R_1 \cdot R_2 / (R_1 + R_2)$

When 'n' resistors of equal resistance $r \Omega$ are connected in parallel, the effective resistance, $R = r/n$

Features

- Effective resistance decreases with the increase of the number of resistors.
- Large current flows through small resistance and small current through large resistance. (Current is different)
- Same potential difference will be available at all resistors.
- When a number of resistors are connected in parallel, the effective resistance will be less than the least one among them.

Problem

1. It is given $5\Omega, 20\Omega$ resistors and $10V$ battery
 - a. What is the effective resistance of the circuit?
 - b. What is the current in the circuit?


Ans:

a. $R = R_1 \cdot R_2 / (R_1 + R_2) = 5 \times 20 / (5 + 20) = 100/25 = 4\Omega$

b. $I = V/R = 10/4 = 2.5A$

Home Work

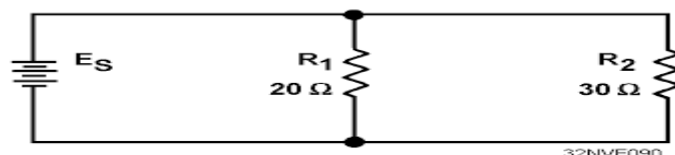1. Calculate the effective resistance of the circuit.



2. 20 resistors of 2Ω each are connected in parallel. Calculate the effective resistance.
3. when a 6Ω and a 3Ω resistors are connected in parallel to a $12V$ battery. Calculate the effective resistance and current in the circuit.