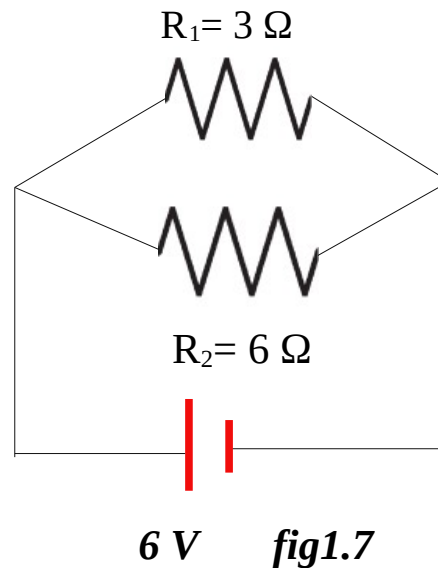


PHYSICS - X-PART-9 CLASS 09

Arrangement of Resistors in Circuits2. Parallel Connection

Effective resistance, $1/R = 1/R_1 + 1/R_2$

$$R = \frac{R_1 \times R_2}{R_1 + R_2}$$



Ex. 1 (Fig.1.7)

$$R_1 = 3 \Omega$$

$$R_2 = 6 \Omega$$

Effective resistance, $R = \frac{R_1 \times R_2}{R_1 + R_2}$

$$R = \frac{3 \Omega \times 6 \Omega}{3 \Omega + 6 \Omega}$$

$$R = 2 \Omega$$

2. If 2 Ω, 4 Ω resistors are connected in parallel. Calculate the effective resistance.

$$R_1 = 2 \Omega$$

$$R_2 = 4 \Omega$$

Effective resistance, $R = \frac{R_1 \times R_2}{R_1 + R_2}$

$$R = \frac{2 \Omega \times 4 \Omega}{2 \Omega + 4 \Omega}$$

$$R = 1.33 \Omega$$

