

CHAPTER 1 EFFECTS OF ELECTRIC CURRENT

(1 Mark Questions)

- Electric bulb: electrical energy \rightarrow light
Induction cooker: electrical energy \rightarrow _____
- Which of the following is connected parallel to a circuit? (ammeter, voltmeter, galvanometer)
- Which of the following is correct?
(a) $Q = \frac{I}{t}$ (b) $I = Q/t$ (c) $Q = It$ (d) $I = Qt$
- Define one volt
- Find the odd one out
(a) I^2R (b) VI (c) V^2/R (d) I^2R
 - LED
 - Fluorescent lamp
 - Bulb
 - LCD
- (a) Induction cooker
(b) soldering iron
(c) safety fuse
(d) LED
- Write any two situations in which over current is flowing through a circuit
- Name any two units of LED and write their uses
- The amperage of a fuse wire used in a circuit that works on 230V is 2.2A. if so the power of the deice is
 - Less than 300W
 - 300W to 500W
 - Between 500W to 510W
 - More than 510W
- How much will be the power of a 220V, 100W electric bulb working at 110V?
i. 100W ii 75W iii 50W iv 25W
- How many resistors of 176Ω should be connected in parallel to get 5A current from 230V supply
(a) 2 (b) 3 (c) 4 (d) 6
- If five 10Ω resistors are connected in parallel then their equivalent/effective resistance is
(a) 10Ω (b) 2Ω (c) $\frac{1}{2}\Omega$ (d) 5Ω
- If five 10Ω resistors are connected in series then their equivalent/effective resistance is
(a) 5Ω (b) 50Ω (c) 10Ω (d) $1/5\Omega$
- Define amperage and what is its unit?
- 1 Calorie = _____ J
- _____ is used as heating coil in heater
- Fuse wire is connected in a circuit in _____(series/parallel)
- Fuse wire is an alloy of _____& _____
- When the current flowing through a conductor is doubled then the heat generated become _____
(a) Twice (b) four times (c) thrice (d) half
- Write the full form of LED
- Write a slogan for energy conservation

21.

(a) Identify the device




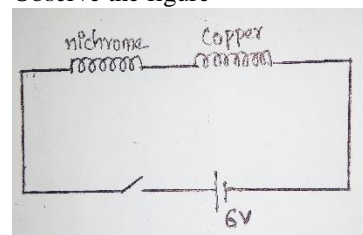(b) Write any two advantages of LED bulb

- Why nitrogen or inert gas is filled in incandescent lamp at low pressure
- Why tungsten is used as filament? also Explain why nichrome is not used as a filament
- Why nichrome is used as heating coil in electric heater?
- Write the differences between series and parallel connection of resistors
- A heating appliance has resistance 115Ω . If 2A current flows through it, what is the power of the appliance
 - If it works for 5 minutes find the heat generated
- Identify (a) and (b) and write their uses




- According to Joule's law $H = I^2Rt$. Will the heat developed increases with increase on resistance without changing the voltage? Explain
- If a bulb is lit after re-joining the parts of a broken filament, what change will occur in the intensity of the light from the lamp? What will be the change in the power of the bulb?
- Observe the figure



- If same length and area of cross section of wires are used which one will produce more heat when key is closed?
 - What happened to the heat produced if they are connected in parallel?
- How fuse wire ensures safety of electric appliances
 - House hold appliances are connected in parallel. Why they are connected in parallel
 - Three resistors of 6Ω are given draw the circuit which will give effective resistance 9Ω and 4Ω

34. Identify the type of connection

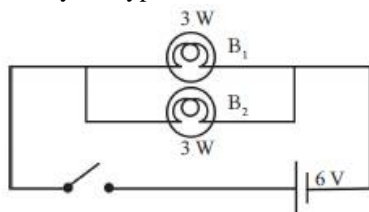

- When key is closed which bulb will glow brightly
- Does current in B_1 and B_2 are same or different
- If B_1 is replaced with a 5W bulb then which bulb will glow brightly

35.

- A girl has many resistors of $2\ \Omega$ each. She needs a circuit of $9\ \Omega$ resistance. For this draw the circuit
- A boy has many resistors of $4\ \Omega$ each. he needs a circuit of $26\ \Omega$ resistance. For this draw the circuit
- A boy has many resistors of $8\ \Omega$ each. he needs a circuit of $2\ \Omega$ resistance. For this draw the circuit

(3 marks questions)

36. Three resistors of $2\ \Omega$, $3\ \Omega$ and $6\ \Omega$ are given in the class.

- What is the highest resistance that can be obtained by them? draw the circuit
- What is the least resistance that can be obtained by them? Draw the circuit.
- Can you make a resistance $4.5\ \Omega$ using them? Draw the circuit

37. 0.5A current flows through an electric heating device connected to 230V supply.

- The quantity of charge that flows through the circuit in 5 minutes is _____
(a) 5C (b) 15C (c) 150C (d) 1500C
- How much is the resistance of the circuit?
- Calculate the quantity of heat generated in 5 minutes
- How much is the power of the device neglect the resistance of wire

38.

a. Complete the following table

Electrical device	Operating voltage(V)	Power (P)	Current (I)
Heater	230V	4370W	-----
Bulb	230V	-----	14.5 A
LED TV	230V	57.5W	-----
Fan	-----	28.75W	0.125A


b. Match the following table

A	B	C
Heater	Voice coil	Lighting effect
Bulb	Heating coil	Electromagnetic induction
Microphone	Armature	Chemical effect
	Filament	Heating effect

39. Correct the underlined statements if it is wrong

- Incandescent lamp having high power will have high resistance in its filament.
- For devices working in same voltage the power is directly proportional to its resistance.
- In an electric device the power is directly proportional to its voltage.

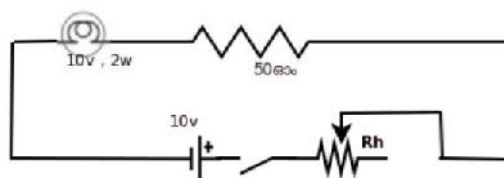40. Observe the figure and answer the following questions




- What is the name and function of the device labelled as R_h
- If the resistance of R_h is $100\ \Omega$ what is the current flowing through the bulb
- Find the power of the bulb

41.


- Write any two disadvantages of filament lamp
- Why tungsten is not used in iron box?
- Write any three factors which affect the heat generated in a current carrying conductor.

42. Observe the figure

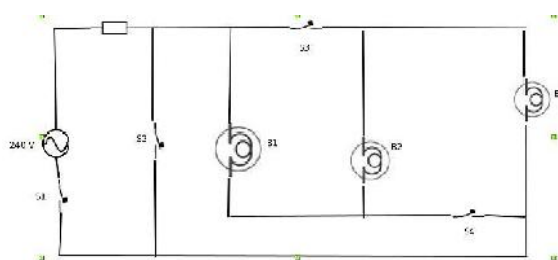

- When switch S_1 is ON which of these bulbs will glow?
- If S_2 and S_3 are getting ON along with S_1 then what will happened to bulb?
- Does this circuit show short circuit and overloading under any case? Explain

43. Observe the figure

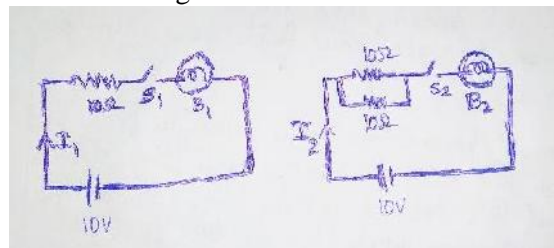

- When the switches are getting ON which bulb will glow with more brightness? Explain.
- Calculate I_1 and I_2 in the above figure