

CODE NO: 07A1EC05 SET NO. 4

## 2008 JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY

IV B.TECH II SEMESTER SUPPLEMENTARY EXAMINATIONS

### NETWORK ANALYSIS

(COMMON TO ELECTRONICS & COMMUNICATION ENGINEERING, ELECTRONICS & INSTRUMENTATION ENGINEERING, BIO-MEDICAL ENGINEERING, ELECTRONICS & CONTROL ENGINEERING, ELECTRONICS & TELEMATICS AND ELECTRONICS & COMPUTER ENGINEERING)

AUG/SEP 2008

Time: 3 hours  
Max Marks: 80

---

**Answer any FIVE Questions**  
**All Questions carry equal marks**

1. Derive an expression to convert a given 3-phase star connected circuit to equivalent delta connection. [16]
2. Derive expression for R.M.S. and average value of a sinusoidal alternating quantity. [16]
3. (a) Explain the phenomenon of resonance. Derive the formula for the resonant frequency of the series resonant circuit.  
(b) Give the quality factor in terms of Bandwidth.  
(c) Find the natural frequency of a series RLC circuit in which  $R = 200$  ohms,  $L = 0.15$  H and  $C = 5$  micro Farads. [8+4+4]
4. Draw the oriented graph, select a tree and obtain the tie-set schedule. [16]
5. Obtain Norton's equivalent across terminals A and B for network [16]
6. Find the Z parameters of the  $\Pi$  network & prove that the circuit is reciprocal. [16]
7. Derive the transient response of RLC series circuit with unit step input. [16]
8. Describe a prototype T section band stop filter. Determine the formula required for designing band stop filter. With suitable sketches explain the advantages of m-derived band stop filter.