

2006 JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY

II B.TECH I SEMESTER SUPPLEMENTARY EXAMINATIONS,
LINEAR & DIGITAL IC APPLICATIONS
 (COMMON TO ELECTRONICS & COMMUNICATION ENGINEERING, ELECTRONICS &
 INSTRUMENTATION ENGINEERING, ELECTRONICS & CONTROL ENGINEERING,
 MECHATRONICS AND ELECTRONICS & TELEMATICS)

NOVEMBER 2006

TIME -3 HOUR
 MARK - 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) What is an OP-AMP? Why it is called so? [4]
- (b) Explain the parameters that should be considered for ac and dc applications of an OP-AMP [6]
- (c) Draw and explain the three open loop OP-AMP configurations with neat circuit diagram [6]
2. (a) Define slew rate and derive the expression for it. List causes of the slew rate and explain its significance in applications [10]
- (b) Explain the difference between slew rate and transient response [6]
3. (a) Draw the schematic diagram of Wien Bridge Oscillator and derive the expression for frequency of oscillation [10]
- (b) What are the conditions to be satisfied by a circuit to produce oscillations? [6]
4. (a) Design a 555 Astable multivibrator to operate at 10 KHz with 40% duty cycle. [8]
- (b) Explain in which the 555 timer can be used as Astable multivibrator [8]
5. (a) Draw the circuit diagram IC 1496 balanced modulator circuit and explain its operations. Sketch the output waveform for the square wave inputs with a phase difference π . [8]
- (b) Draw the circuit of PLL as frequency multiplier and explain its working [8]
6. (a) Explain the term "Frequency Sealing" with suitable example. [6]
- (b) Design a wide band-pass filter with $f_L=200\text{Hz}$, $F_H=1\text{KHz}$ and a pass-band gain=4. Draw the frequency response and calculate 'Q' factor for the filter. [10]

7. (a) Draw the circuit of ECL logic OR/NOR gate and verify the Boolean expression. [8]

(b) List out the major advantages of ECL logic. [4]

(c) Explain the functions of a Tri-state TTL gate

8. (a) Draw the circuit of a Weighted Resistor DAC and obtain expression for n-bits. [8]

(b) Sketch the Analog output voltage for the given digital input code. [4]

(c) What are the major disadvantages in this type?

Educationobserver.com